

Name SOLUTIONS

ECE Box # _____

A	91 - 100
B	76 - 90
C	60 - 75

μ 84.9

σ 13.5

MED 88

Problem	Average Score	Points
1	<u>22.9</u>	25
2	<u>12.7</u>	15
3	<u>21.9</u>	25
4	<u>14.3</u>	20
5	<u>13.1</u>	15

ECE4902 B2015


Analog IC Design

Final Exam
December 15, 2015

- This is a **closed book, closed notes test!** Use of calculators is OK, but **no pre-stored data or formulas allowed!**
- The last page is a notes page that may be detached for convenience and need not be turned in with the exam
- Show **all** your work. Partial credit may be given. If you think you need something that you can't remember, write down what you need and what you'd do if you remembered it.
- **Look for the simple, straightforward way to solve the problem for the level of accuracy required. Don't get entangled in unnecessary algebra.**
- As in real life, some problems may give you more information than you need. Don't assume that all information must be used! It's your job to decide what's relevant to the solution.
- You have one hour and 50 minutes to complete this exam. There are five problems on a total of 13 pages (including notes page).


- This problem is concerned with the op-amp circuit shown in the figure below. This op-amp is intended for single-supply applications, with supply rail voltages of $V_{DD} = +5V$ and $V_{SS} = 0V$ (ground). In this application, a colleague has seen that the 100pF load capacitance at the v_{OUT} node has caused slow op-amp behavior, and proposes increasing the op-amp unity-gain frequency by reducing the compensation capacitor C_{COMP} to 5pF.

 For the purposes of this problem, you may assume the op-amp is connected as a follower with negative feedback so that all MOSFETs are in the saturation (active) region, and input and output node voltages are +2.5V.



For the MOSFET parameters, use the following:

Parameter	N-channel	P-channel	Units
V_{TH}	+0.90	-0.80	V
μC_{ox}	6.0E-5	2.0E-5	A/V ²
λ	0.02	0.05	V ⁻¹

 

a) V_{GS} values from square law:

M_1, M_2

$$20\mu A = \frac{6E-5}{2} \frac{20}{2} (V_{GS1} - 0.9)^2$$

$$V_{GS1} - 0.9V = \sqrt{20\mu A \left(\frac{2}{6E-5}\right) \left(\frac{2}{20}\right)} = \underbrace{0.258}_{V_{OV1} \text{ FOR } 2(a)} \Rightarrow V_{GS1} = 1.158V$$

M_3, M_4

$$20\mu A = \frac{2E-5}{2} \frac{40}{2} (V_{GS3} - (-0.8))^2$$

$$V_{GS3} + 0.8V = \sqrt{20\mu A \left(\frac{2}{2E-5}\right) \left(\frac{2}{40}\right)} = \underbrace{0.316}_{V_{OV5} \text{ FOR } 2(c)} \Rightarrow V_{GS3} = -1.116V$$

M_5 HAS SAME I_D/W RATIO; SAME V_{GS}

M_6, M_7, M_8

$$20\mu A = \frac{6E-5}{2} \frac{10}{2} (V_{GS6} - 0.9)^2$$

$$V_{GS6} - 0.9V = \sqrt{20\mu A \left(\frac{2}{6E-5}\right) \left(\frac{2}{10}\right)} = \underbrace{0.365}_{V_{OV6} \text{ FOR } 2(c)} \Rightarrow V_{GS6} = 1.265V$$

- a) Find the DC operating point (drain current I_D and gate-source voltage V_{GS}) for all MOSFETs. Accuracy for currents $\pm 20\%$; accuracy for voltages $\pm 0.05V$. Use the table below to record your answers.

[15]

MOSFET	Drain current $I_D [\mu A]$	Gate-Source voltage $V_{GS} [V]$
M1	20	1.158
M2	20	1.158
M3	20	-1.116
M4	20	-1.116
M5	400	-1.116
M6	20 μA	1.265
M7	40	1.265
M8	400	1.265

- b) Determine the voltage with respect to ground at each node.

[5]

	Node voltage [V]	
V_1	+2.5 V	
V_2	+2.5 V	
V_{OUT}	+2.5 V	
V_{S1}	+1.34	$V_1 - V_{GS1}$
V_{G3}	+3.88	$V_{DD} + V_{GS3}$
V_{G5}	+3.88	$V_{DD} + V_{GS5}$
V_{G6}	+1.27	V_{GS6}


- c) Determine the value of the resistor R_B . Accuracy $\pm 20\%$.

[5]

$$R_B = 187 \text{ k}\Omega$$

$$\text{OHM'S LAW} \quad \frac{5V - 1.27V}{20\mu A}$$

 2. Continuing with the op-amp circuit from the previous problem, shown again in the figure below.



- a) Assuming the dominant pole model, determine the expected value of the unity gain frequency (gain bandwidth product) f_T for this op-amp. Accuracy $\pm 20\%$.

$$f_T = \underline{4.9 \text{ MHz}} \quad [5]$$

$$\frac{g_{mI}}{2\pi C_C} \leftarrow \frac{2I_{D1}}{V_{ov1}} = \frac{2(20\mu A)}{0.258V} = 154\mu A/V$$

$$\frac{154E-6}{2\pi(5\text{ pF})} = 4.9 \text{ MHz}$$

- b) Determine the slew rate in $V/\mu s$ for this op-amp. Accuracy $\pm 20\%$.

$$SR = \underline{8 V/\mu s} \quad [5]$$

$$\frac{I_{SS}}{C_C} = \frac{40\mu A}{5\text{ pF}} = 8E+6 \frac{V}{\text{sec}}$$


- c) Determine the output voltage swing range: the minimum and maximum output voltages $V_{OUT(MIN)}$ and $V_{OUT(MAX)}$ for all MOSFETs to operate in the saturation (active) region. Accuracy $\pm 0.05V$.

$$V_{OUT(MIN)} = \underline{0.37} \quad V_{OUT(MAX)} = \underline{4.68} \quad [5]$$

$$\underbrace{\quad}_{0V + V_{ov6}} \quad \underbrace{\quad}_{V_{DD} + V_{ov5}}$$

TRIODE CRASH WHEN $V_{DS} = \underbrace{V_{GS} - V_{TH}}_{V_{ov}}$

 3. The simplified small signal model for the op-amp of the previous problem is:



POLE
FREQUENCIES

$$\frac{1}{2\pi R_{oI} C_I} = 490 \text{ Hz}$$

$$45 \text{ kHz}$$

STAGE
DC GAINS

$$A_{vI} = \frac{g_{mI}}{R_{oI}} = \frac{1.54 \text{E-}4 \text{ A/V}}{714 \text{ k}\Omega} = 110$$

$$A_{vII} = \frac{g_{mII}}{R_{oII}} = \frac{2.52 \text{E-}3 \text{ A/V}}{35.7 \text{ k}\Omega} = 90$$

- a) What is the numerical value of the DC open-loop gain A_O ? [5]

$$A_O = 9900 + 80 \text{ dB}$$

- b) Using the graph paper on the following page, **CAREFULLY** sketch the open-loop gain Bode plot (magnitude and phase). Be sure to label your axes and any interesting points on your plot. [6]

- c) If this op-amp is configured with negative feedback for closed-loop gain of unity, what will the phase margin be? Indicate this on your plot from (b). [5]

$$\text{Phase margin} \approx 5^\circ$$

- d) If this op-amp is configured with negative feedback for closed-loop gain of unity, would it be stable, marginally stable, or unstable? (Circle one) [1]

STABLE


MARGINALLY
STABLE

UNSTABLE

Explain! ϕ MARGIN NEEDS TO BE $> 70^\circ$ TO BE STABLE (NO OVERSHOOT) [3]

- e) Why is the value of C_I in the small signal model so much bigger than C_{COMP} ? Explain! [5]

MILLER EFFECT

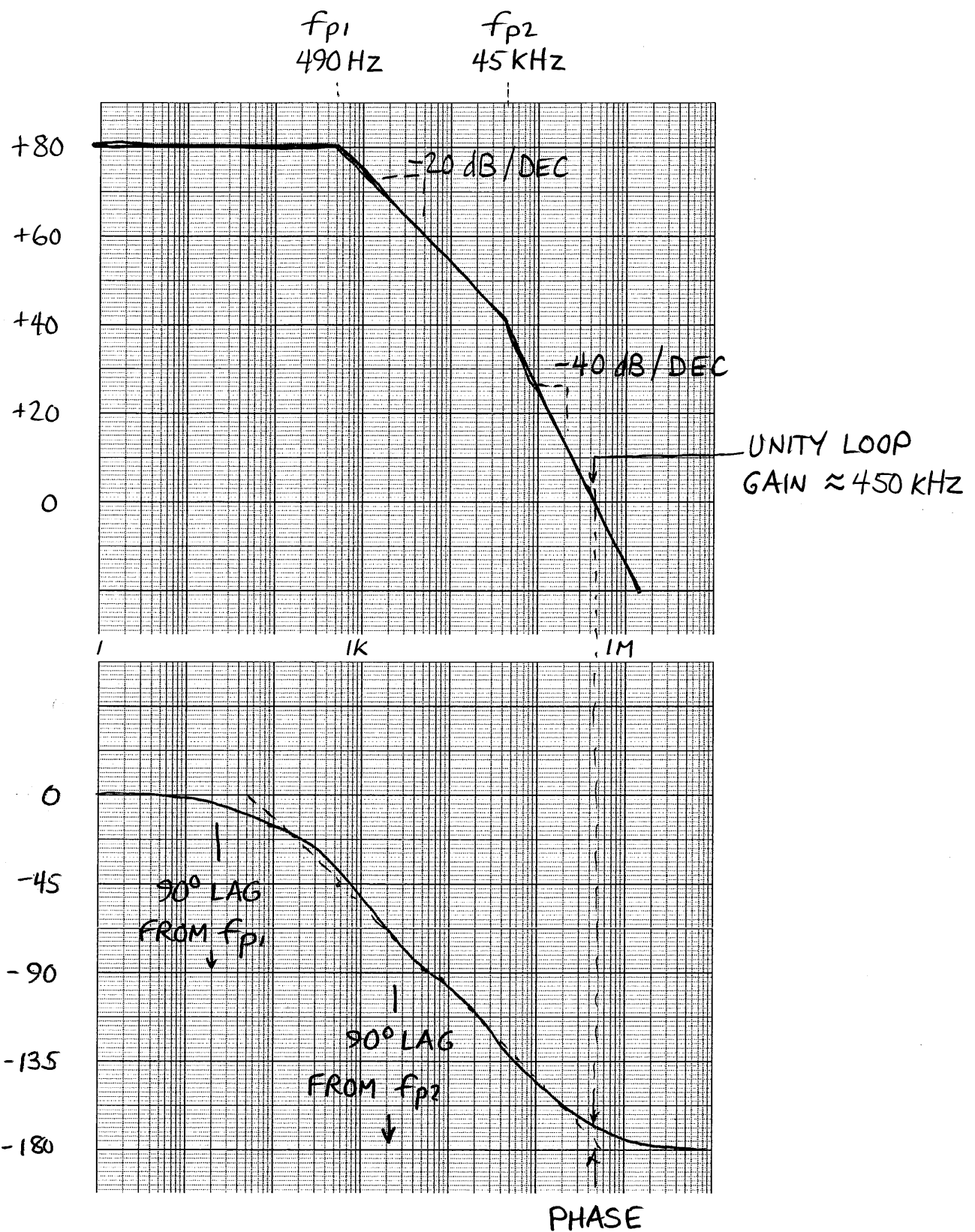

PROBLEM! C_c IS TOO SMALL,
 DOESN'T MOVE f_{p1} TO A LOW
 ENOUGH FREQUENCY; f_{p2} OCCURS
 BEFORE UNITY LOOP GAIN FREQUENCY

4. This problem involves design of a differential amplifier, shown in schematic form on the opposite page. The amplifier is powered by split $\pm 5V$ supply rails. MOSFETs M1 and M2 form the differential pair; these are identical devices with width equal to W1. Bias current of $I_{BIAS} = 200\mu A$ for the differential pair is provided by the current mirror formed by MOSFETs M3 and M4; note the unequal widths $W3 \neq W4$.

For this problem, you may ignore channel length modulation effects and the body effect. For the MOSFET parameters, use the following:

Parameter	N-channel	P-channel	Units
V_{TH}	+0.90	-0.80	V
μC_{ox}	6.0E-5	2.0E-5	A/V ²

- a) Find the value of $R_{D1} = R_{D2} = R_D$ required for a DC bias voltage level of +2.5V at outputs v_{O1} and v_{O2} when $v_{IN} = 0$. Accuracy $\pm 10\%$.

$$R_D = \underline{25k\Omega} \quad \text{DC BIAS CONDITION: } \left(\frac{I_{BIAS}}{2} \right) R_D = 5V - 2.5V \quad [3]$$

- b) Choose R_B so the M3/M4 mirror produces $I_{BIAS} = 200\mu A$. Accuracy $\pm 10\%$.

$$R_B = \underline{176k\Omega} \quad \text{OHM'S LAW} \quad [4]$$

- c) Choose width $W1 = W2 = W$ for M1 and M2 so that the small signal differential voltage gain magnitude is $|v_{od}/v_{in}| = 12$. Accuracy $\pm 10\%$.

$$W = \underline{38} \quad \text{FOR } g_m = \frac{12}{R_D} = 480\mu A/V = \sqrt{2(100\mu A)(6E-5)} \frac{W_1}{2} \quad [4]$$

- d) In the space on the opposite page, sketch the total v_{O1} and v_{O2} that result when the input is a low frequency sine wave with differential amplitude of 0.2V peak. Be sure to indicate any interesting information (such as peak voltage values) on your plot.

[3]

- e) In the space on the opposite page, sketch the total v_{O1} and v_{O2} that result when the input is a low frequency sine wave with differential amplitude of 1.0V peak. Be sure to indicate any interesting information (such as peak voltage values) on your plot.

[3]

- f) A colleague proposes to increase the small signal differential voltage gain magnitude (without affecting the output DC operating point), by doubling the value of W from part (c) while keeping the other design values (I_{BIAS} , R_B , R_D) unchanged. Will this work? Circle one:

YES, IT
WILL WORK


NO, IT
WON'T WORK

[1]


[2]

Explain!: Why or why not?


g_m HIGHER (V_{ov} LOWER)

 

Axes for (d):

 

Axes for (e):

 

5. You are designing analog circuitry on a digital IC being fabricated in a CMOS process with very short gate length ($L=0.13\mu\text{m}$). The I_D vs. V_{GS} plot for a MOSFET in the active region (measured using the circuit shown in Fig. 4a) is shown below. The characteristic exhibits a "short-channel" effect: due to velocity saturation of carriers in the channel, the mobility relationship does not hold and the square law equation does not apply for predicting drain current I_D when $V_{GS} > 0.5\text{V}$



 


Fig. 4a.

 

 It is desired to use this MOSFET in a common-source amplifier configuration shown below, in which the small-signal input v_{sig} rides on a DC bias level V_{BIAS} which is chosen for a DC drain current of 1.2mA.



- a) Find the required DC bias level V_{BIAS} to realize the operating point with DC drain current of 1.2mA. Indicate the operating point on the I_D - V_{GS} plot. [3]

$$V_{BIAS} = \underline{0.75V}$$

- b) Determine the transconductance g_m at this operating point. [3]

$$g_m = \underline{3.0 \text{ E-3}} \quad \text{SLOPE}$$

- c) Determine the value of R_D for an output DC bias level of +1.0V [3]

$$R_D = \underline{1.25 \text{ k}\Omega} \quad \text{OHM'S LAW}$$

- d) Determine the small signal gain $a_v = v_{out}/v_{sig}$ of the circuit with your value of R_D . You may ignore channel length modulation. [3]

$$a_v = \underline{-2.09} \quad -g_m R_D \quad \text{SAME SMALL SIGNAL MODEL FOR COMMON SOURCE}$$

- e) A colleague cites the equation $g_m = 2I_D/(V_{GS} - V_{TH})$ and suggests that the small-signal transconductance g_m for this device can be increased, by increasing V_{BIAS} to operate the MOSFET at a higher value of drain current I_D . Is this correct? Explain your answer! [1]

YES, g_m WILL BE HIGHER
WITH INCREASED I_D

NO, g_m WILL NOT BE HIGHER
WITH INCREASED I_D

Explain! SAME SLOPE! g_m DOES NOT CHANGE
AT HIGHER V_{GS} VALUES! [2]

MOSFET LARGE SIGNAL CHARACTERISTICS

P CHANNEL

N CHANNEL

CIRCUIT SYMBOL		
SATURATION REGION	$I_D = -\frac{\mu_p C_{ox} W}{2L} (V_{GS} - V_{TH})^2 [1 + \lambda V_{DS}]$	$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_{TH})^2 [1 + \lambda V_{DS}]$
I_D - V_{DS} CHARACTERISTIC		
I_D - V_{GS} CHARACTERISTIC (SATURATION REGION)		
TRIODE REGION	$I_D = -\mu_p C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]$	$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]$