

ECE4902 Lecture 6

Quiz 2

Current Mirror

- Diode connected MOSFET
- DC matching
- Small signal models

Common Source with Active Load

- Low-frequency small-signal gain
- Bandwidth
- Gain-bandwidth product

Handouts:

- Lab 5 Review Slides

- Diode Connected MOSFET


- Small signal analysis of ...

 - current mirror

 - CS amplifier with active load


G, D TOGETHER

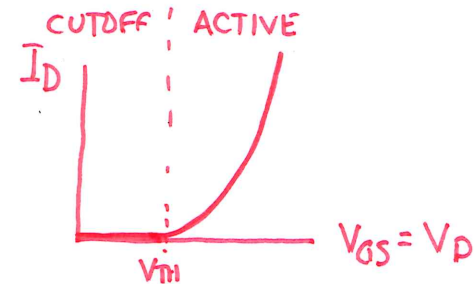Current mirror: Why does diode connected MOSFET have to carry $I_D = I_B$?



CURRENT WE WANT

V_{GS} THAT CORRESPONDS TO I_B INPUT

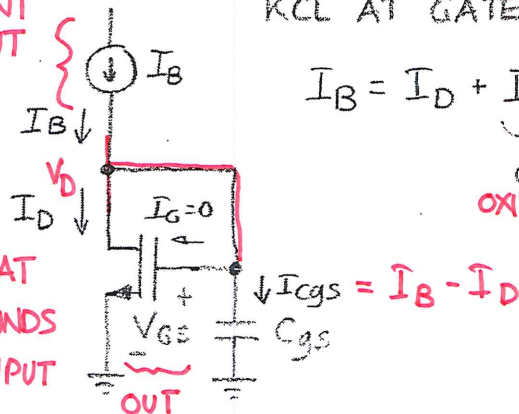

KCL AT GATE NODE

$$I_B = I_D + I_G + I_{cgs}$$

OXIDE

$$I_{cgs} = I_B - I_D$$

SUPPOSE $I_D \neq I_B$


SAY V_{GS} IS TOO SMALL SO $I_D < I_B$

IF $I_D < I_B$, THEN I_{cgs} WILL BE POSITIVE
 $\Rightarrow$ CHARGING UP $C_{gs} \Rightarrow$ INCREASING I_D
 $\Rightarrow$ MOVES I_D CLOSER TO I_B

SIMILARLY, IF $I_D > I_B$, V_{GS} WILL DECREASE

EQUILIBRIUM WHEN $\frac{dV_{GS}}{dt} = 0 \Rightarrow I_{cgs} = 0 \Rightarrow \boxed{I_B = I_D}$

"CURRENT MIRROR"

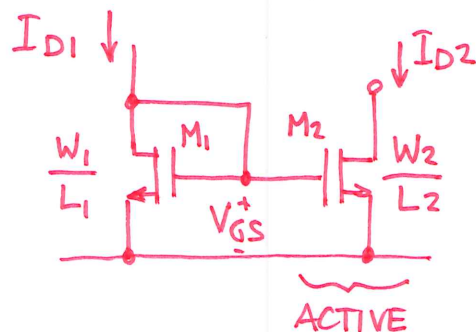

V_{GS} MUST BE SAME FOR BOTH (CONNECTION)

$$I_{D1} = \frac{\mu_1 C_{ox1}}{2} \frac{W_1}{L_1} (V_{GS} - V_{TH1})^2 \Rightarrow V_{GS} = V_{TH1} + \sqrt{\frac{2}{\mu_1 C_{ox1}} I_{D1} \frac{L_1}{W_1}}$$

APPLY THIS V_{GS} TO M_2

$$I_{D2} = \frac{\mu_2 C_{ox2}}{2} \frac{W_2}{L_2} \left(\sqrt{\frac{2}{\mu_1 C_{ox1}} I_{D1} \frac{L_1}{W_1}} + V_{TH1} - V_{TH2} \right)^2$$

ON IC SILICON WAFER: MATCHING: $V_{TH1} = V_{TH2}$

$$\mu_1 C_{ox1} = \mu_2 C_{ox2}$$

$$I_{D2} = \left(\frac{W_2/L_2}{W_1/L_1} \right) I_{D1}$$


SIZE RATIO

CHOOSE $L_1 = L_2$ (BASED ON λ TO GET r_o)


$$I_{D2} = \left(\frac{W_2}{W_1} \right) I_{D1}$$

SCALE RATIO WITH WIDTH FACTOR

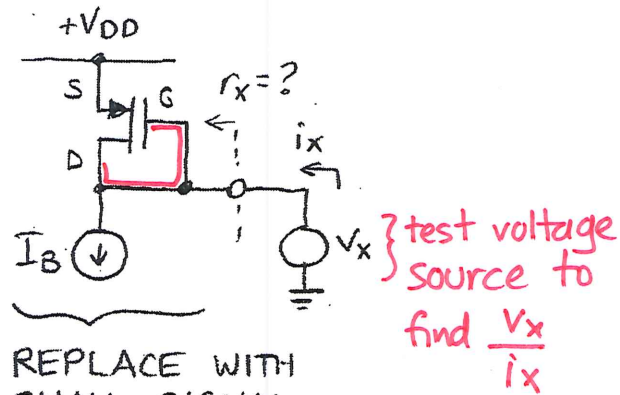small signal resistance of diode connected MOSFET



REPLACE WITH SMALL SIGNAL MODEL

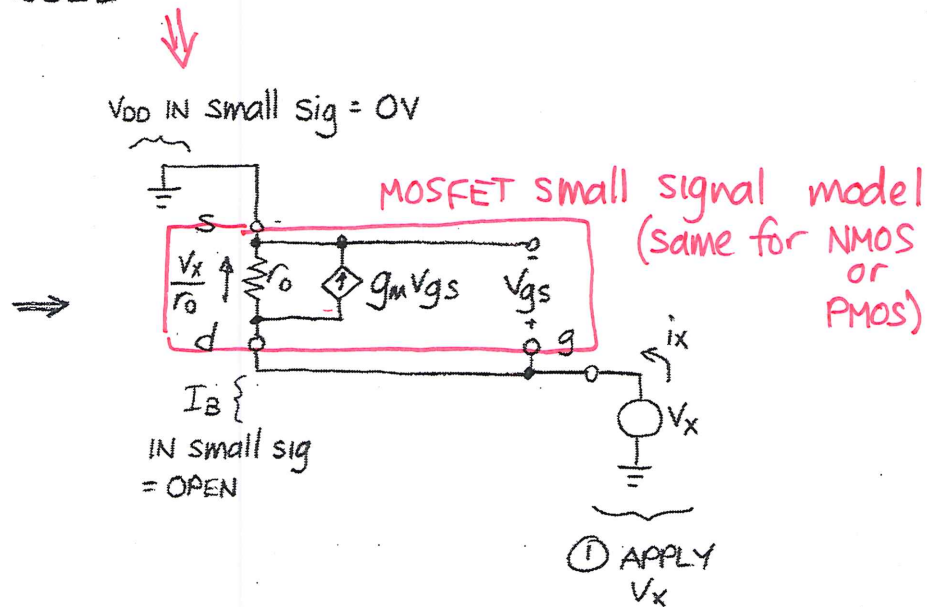

"IMPEDANCE AT A NODE" PROCEDURE

- ① APPLY V_x
- ② CALCULATE i_x
- ③ $r_x = \frac{V_x}{i_x}$

- ② KCL AT GATE

$$i_x = g_m V_{gs} + \frac{V_x}{r_o}$$


$$i_x = g_m V_x + \frac{V_x}{r_o} = V_x \left(g_m + \frac{1}{r_o} \right)$$

KVL AROUND GATE: $V_{gs} = V_x$


- ③ $r_x = \frac{V_x}{i_x} = \frac{1}{g_m + \frac{1}{r_o}} = \left(\frac{1}{g_m} \right) \parallel r_o$ USUALLY $r_o \gg \frac{1}{g_m}$

$$r_x \approx \frac{1}{g_m}$$

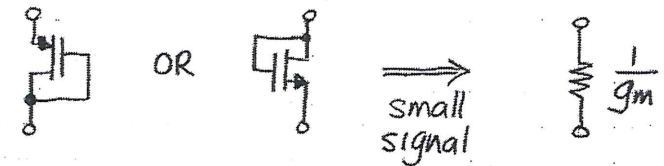SMALL SIGNAL MODEL FOR DIODE CONNECTED MOSFET (NMOS OR PMOS) IS $1/g_m$:



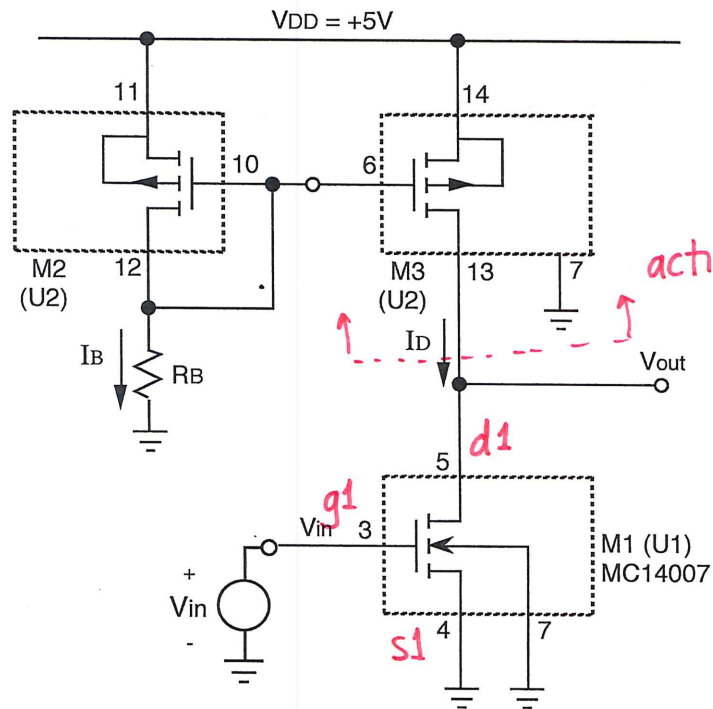small signal model for common source amplifier with active load





FUNCTION GENERATOR

$$R_{out} = r_{o1} || r_{o3} = \frac{1}{\frac{1}{\lambda_1 I_D} + \frac{1}{\lambda_3 I_D}} = \frac{1}{(\lambda_1 + \lambda_3) I_D}$$


$$g_{m1} = \frac{2I_D}{(V_{GS1} - V_{TH1})}$$

NUMBERS
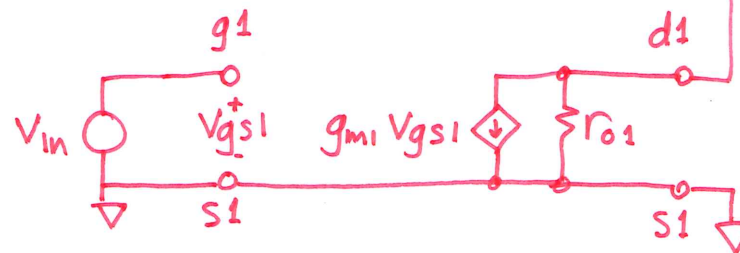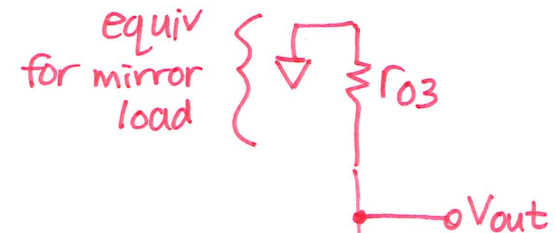
$$\text{CHOOSE } V_{ov} = 0.3 \quad \frac{2}{(0.3V)(0.03+0.05)} = 83 \gg 10$$





r_{o1}, r_{o3} IN PARALLEL: REDRAW

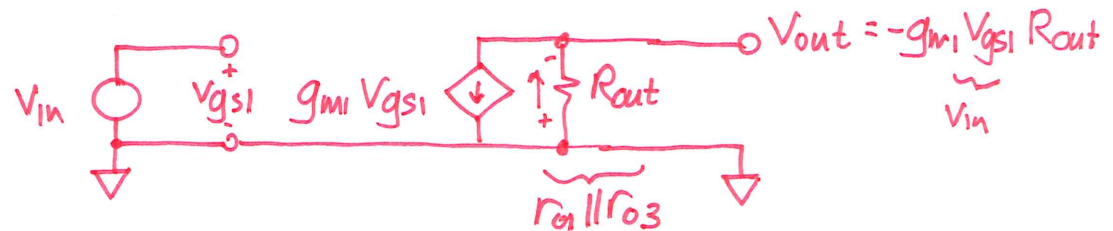

$$\text{Small signal gain } \frac{V_{out}}{V_{in}} = -g_{m1} R_{out} = \frac{2I_D}{(V_{GS1} - V_{TH1})(\lambda_1 + \lambda_3)I_D} = \frac{2}{V_{ov}(\lambda_1 + \lambda_3)}$$

Example process parameters		NMOS	PMOS	Units
Threshold voltage	V_t	+1.50	-1.50	V
Mobility- C_{ox} product	μC_{ox}	7.0 E-6	2.5 E-6	A/V ²
Channel length modulation	λ	0.03	0.05	V ⁻¹

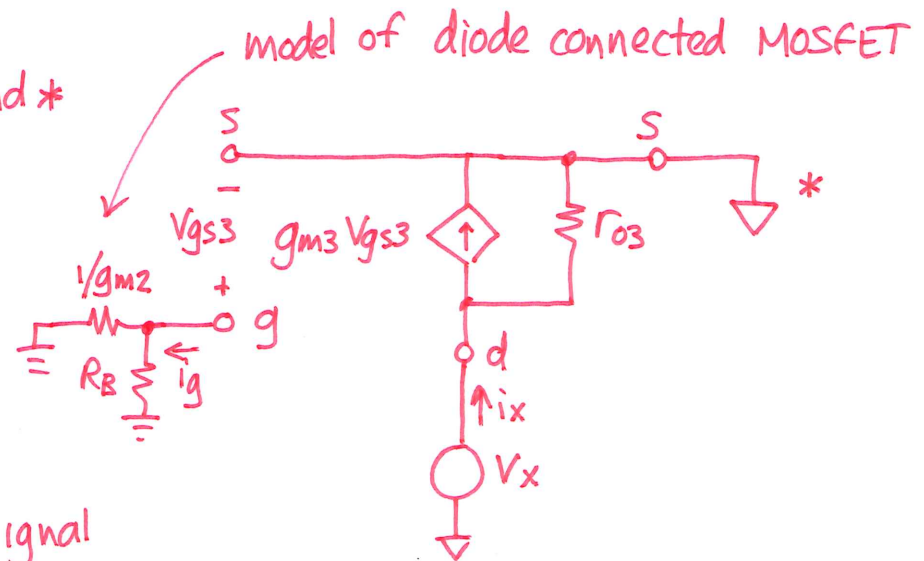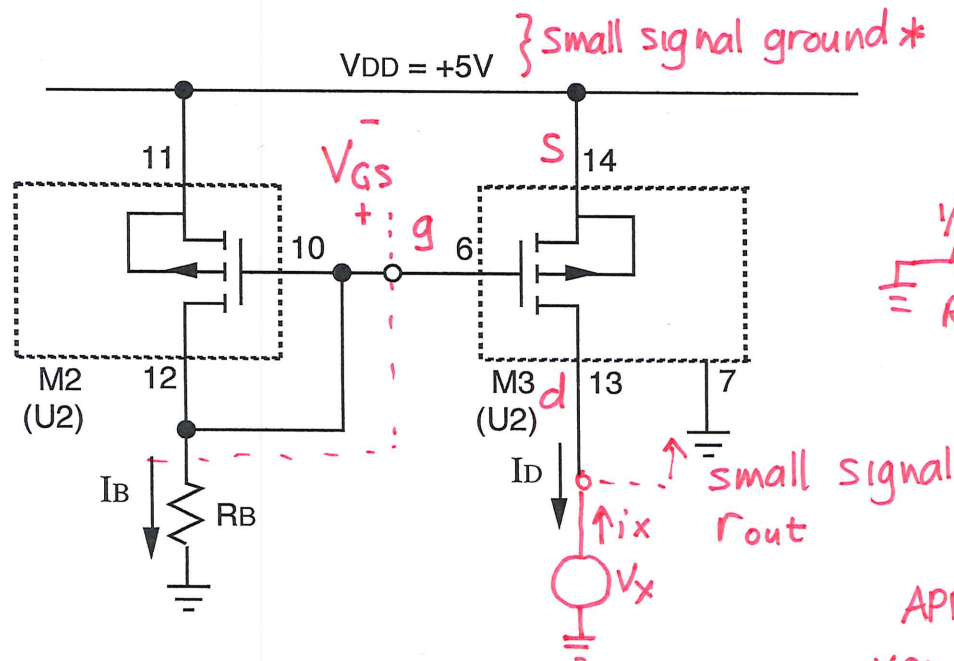small signal resistance "looking into" drain of current mirror:



APPLY V_x , CALCULATE i_x

KCL AT d NODE

$$i_x = g_{m3} V_{gs3} + \frac{V_x}{r_{o3}} \quad [1]$$

KVL LOOP TO FIND V_{gs3}

$$V_{gs3} - i_g \left(R_B \parallel \frac{1}{g_{m2}} \right) = 0 \Rightarrow V_{gs3} = 0 \quad [2]$$


= 0 (GATE OXIDE)

SUB [2] INTO [1]


$$\frac{V_x}{i_x} = r_{o3} \quad \text{HIGH! GOOD FOR HIGH GAIN!}$$

Bandwidth: small signal model for common source amplifier with active load

ASSUME $C_L \gg C_{par}$

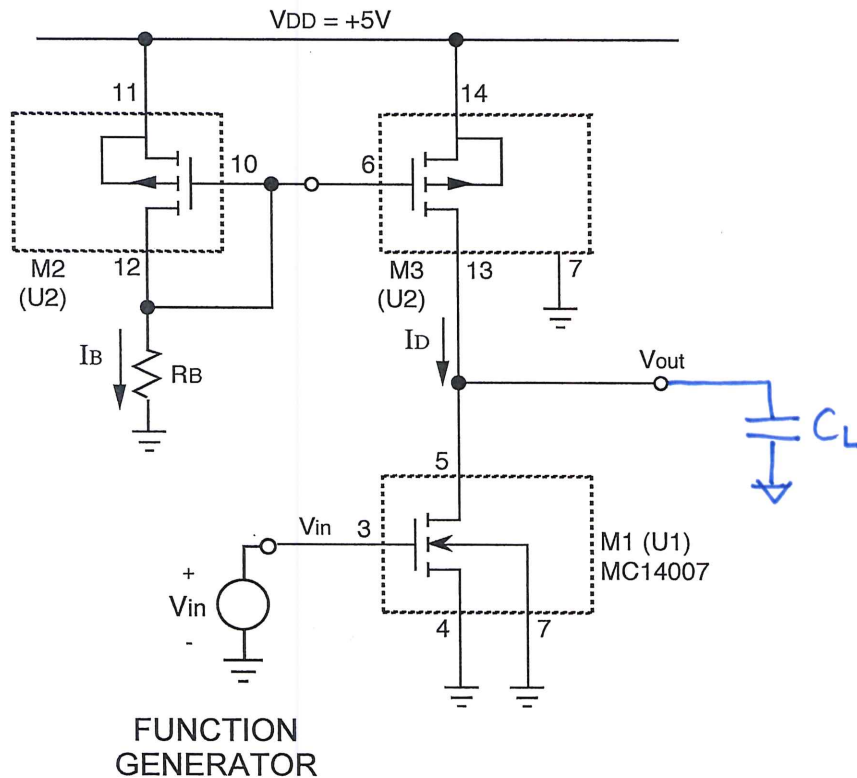

small signal model (low freq)

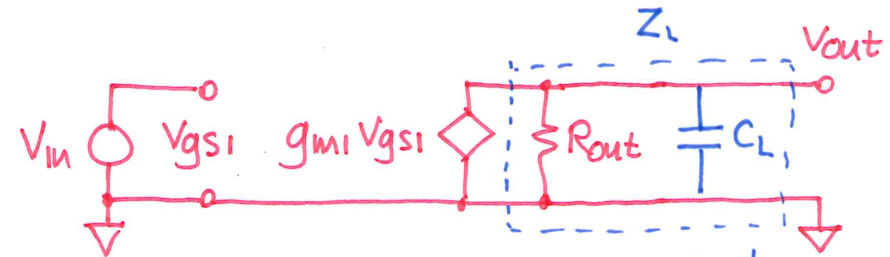

small signal gain

$$\frac{V_{out}}{V_{in}} = -g_{m1} \underbrace{R_{out}}_{Z_L}$$

$$Z_L = R_{out} \parallel \frac{1}{sC_L}$$

$$Z_L = \frac{R_{out}}{1 + sR_{out}C_L}$$

$$\frac{V_{out}}{V_{in}} = -g_{m1} Z_L = \frac{-g_{m1} R_{out}}{1 + sR_{out}C_L}$$

PROBLEM?

R_{out} POORLY CONTROLLED!

GAIN $\times$ BW

$$g_{m1} R_{out} \frac{1}{2\pi R_{out} C_L} = \frac{g_{m1}}{2\pi C_L}$$

DC GAIN $\{ g_{m1} R_{out}$

