

ECE4902 Lecture 7

Common Source with Active Load
Design Example

Bandwidth (6.2)
Miller Effect


Differential Pair

Hand In:
HW 3

Handouts:
Design Example
Transfer Function: Poles & Nodes
Miller Effect
3 Cases of Differential Pair
Bartlett's Bisection Theorem
Lab 7 Differential Pair Circuits

Design example: common source amplifier with active load

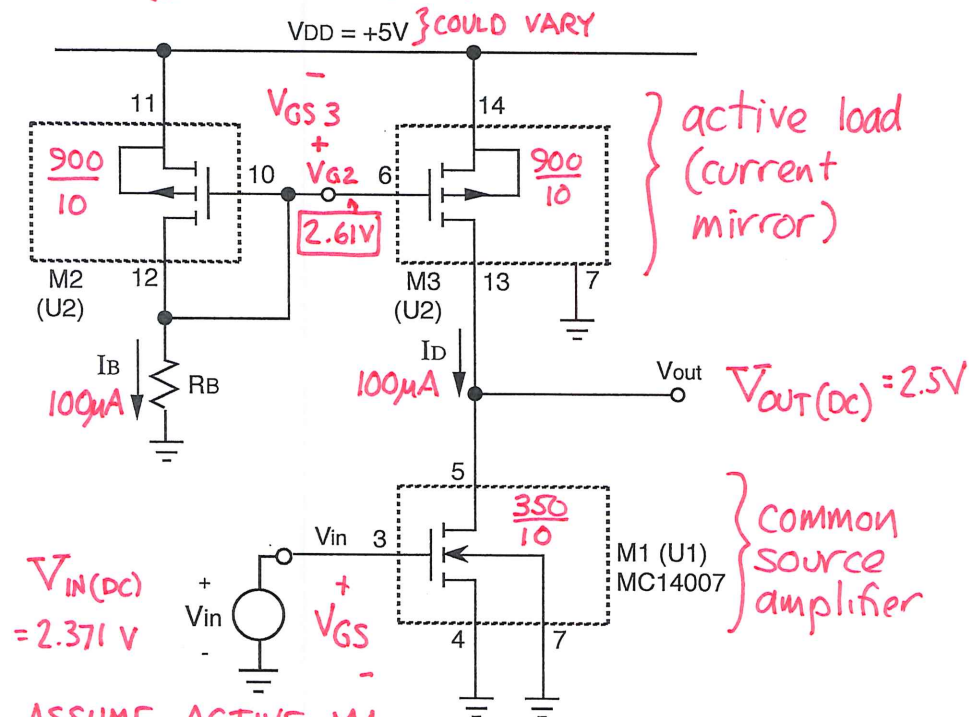Determine input DC bias and value of R_B required for V_{OUT} DC bias of 2.5V and DC drain current of 100 μ A



$$V_{in(DC)} = 2.371V$$

ASSUME ACTIVE M1
SQUARE LAW

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 [1 + \lambda V_{DS}]$$

$$100\mu A = \frac{7E-6}{2} \frac{350}{10} (V_{GS} - 1.5V)^2 [1 + \frac{(0.03)(2.5V)}{0.075}]$$

$$V_{GS} = \sqrt{\frac{100\mu A}{1.075} \frac{2}{7E-6} \frac{10}{350}} + 1.5V = 2.371$$

$$\begin{matrix} +NMOS \\ -PMOS \end{matrix} \quad \pm 0.871 \quad \left. \begin{matrix} V_{GS} - V_{TH} < V_{DS} = 2.5V \\ \checkmark \text{ ACTIVE} \end{matrix} \right\}$$

FOR M3: ASSUME ACTIVE SQ LAW

$$100\mu A = \frac{2.5E-6}{2} \frac{900}{10} (V_{GS3} + 1.5V)^2 [1 + \frac{(0.05)(2.5)}{0.125}]$$

$$V_{GS3} = -1.5V + \sqrt{\frac{100\mu A}{1.125} \frac{2}{2.5E-6} \frac{10}{900}} \pm 0.89V \text{ CHOOSE - FOR PMOS}$$

$$V_{GS3} = -1.5V - 0.89V = -2.39V$$

KVL TO GATES OF MIRROR:

$$V_{DD} + V_{GS3} = V_{G2} = 5V + (-2.39V) = 2.61V$$

$V_{DS2} \neq V_{DS3}$ I_{D2}, I_{D3} A LITTLE DIFFERENT
(CHANNEL LENGTH MOD)


IGNORE FOR NOW: $I_{D2} = I_{D3} = 100\mu A$

$$R_B = \frac{2.61V}{100\mu A} = 26.1K\Omega$$

DISADVANTAGE: I_B SENSITIVE TO V_{DD} CHANGE
(SOLVE WITH BIAS BLOCK, BANDCAP V REF)

Example process parameters		NMOS	PMOS	Units
Threshold voltage	V_t	+1.50	-1.50	V
Mobility- C_{ox} product	μC_{ox}	7.0 E-6	2.5 E-6	A/V ²
Channel length modulation	λ	0.03	0.05	V ⁻¹

small signal gain

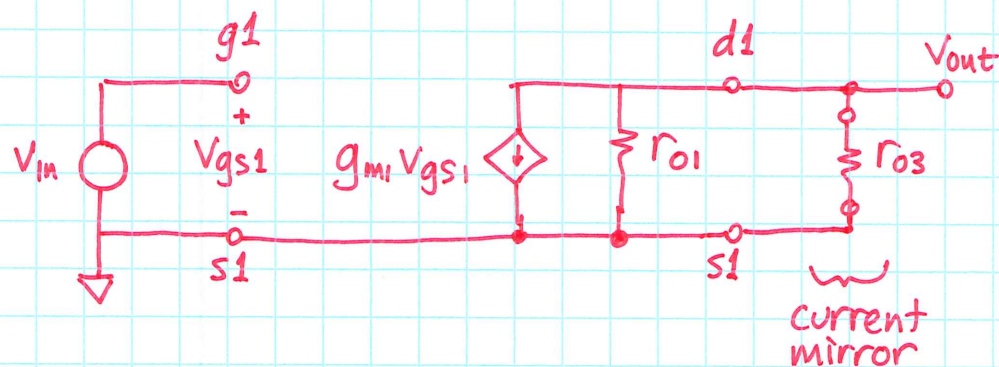

$$g_{m1} = \frac{2I_{D1}}{(V_{GS1} - V_{TH1})}$$

$$= \frac{2(100\mu A)}{0.871}$$

$$= 230\mu A/V$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}}$$

$$= \frac{1}{(0.03)(100\mu A)}$$

$$= 330k\Omega$$

$$r_{o3} = \frac{1}{\lambda_3 I_{D3}}$$

$$= \frac{1}{(0.05)(100\mu A)}$$

$$= 200k\Omega$$

$$R_{out} = r_{o1} || r_{o3} = 125k\Omega$$

$$\frac{V_{out}}{V_{in}} = -g_{m1} R_{out} = -\left(\frac{230\mu A}{V}\right)(125k\Omega) = -29 \Rightarrow -120$$

LARGE
 $V_{GS} - V_{TH}$

FIX: SMALLER
 $(V_{GS} - V_{TH}) \Rightarrow 0.22$

$$\frac{2}{(\lambda_1 + \lambda_3)(V_{GS} - V_{TH})}$$

Transfer function: Poles associated with circuit nodes

Cascade of noninteracting blocks

$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{V_2}\right) \left(\frac{V_2}{V_1}\right) \left(\frac{V_1}{V_{in}}\right)$$

PRODUCT OF INDIVIDUAL
BLOCK TRANSFER FUNCTIONS!

(1)

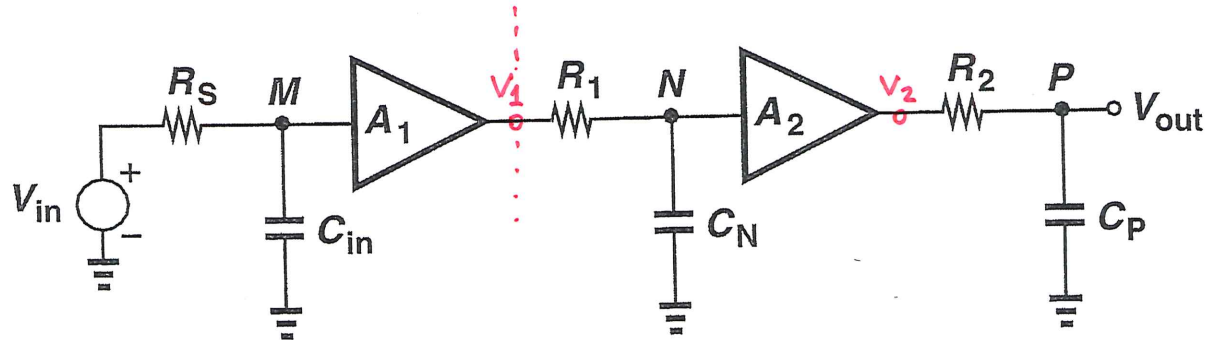


Figure 6.6 Cascade of amplifiers.

$$\frac{V_1}{V_{in}} = \left(\frac{1}{1+sR_SC_{in}}\right) A_1$$

$$\frac{V_2}{V_1} = \left(\frac{1}{1+sR_1C_N}\right) A_2$$

$$\frac{V_{out}}{V_2} = \frac{1}{1+sR_2C_P}$$


$$\frac{V_{out}}{V_{in}} = \frac{A_1 A_2}{(1+sR_SC_{in})(1+sR_1C_N)(1+sR_2C_P)}$$

EACH POLE OF $\frac{V_{out}}{V_{in}}$ TRANSFER FUNCTION

ASSOCIATED WITH NODE IN
THE PHYSICAL CIRCUIT

(2)

$$\left|\frac{V_{out}}{V_{in}}\right|$$


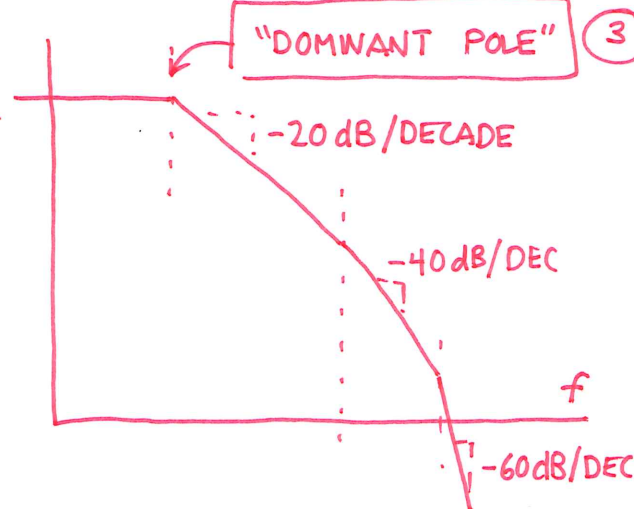


DETERMINES
BANDWIDTH

Miller effect

EE4902 MILLER EFFECT

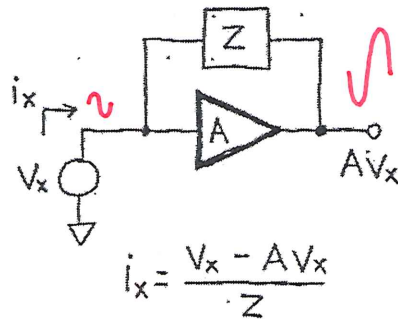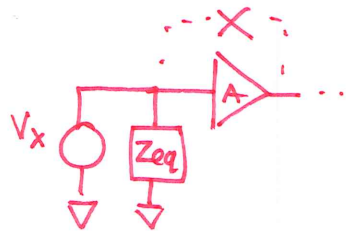
Consider any amplifier (not necessarily an op-amp) with gain A , and some impedance Z from input to output: what impedance does it "look like"?



$$\frac{V_x}{i_x} = \frac{Z}{(1-A)}$$

Impedance is reduced by factor $(1-A)$

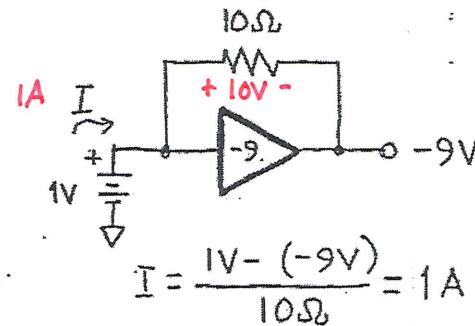EXAMPLE: $Z = 10\Omega$ resistor
 $A = -9$; $V_x = 1V$



Applying 1V causes 1A to flow:
Source "sees" a 1Ω resistor!
 $1\Omega = 10\Omega / (1 - [-9])$


WHEN Z IS A CAPACITANCE: $Z = \frac{1}{j\omega C}$

$$\frac{V_x}{i_x} = \frac{1}{j\omega (1-A)C}$$

APPARENT VALUE OF C MULTIPLIED BY $(1-A)$!


LARGE INCREASE WHEN A IS INVERTING GAIN

Miller effect in common source stage

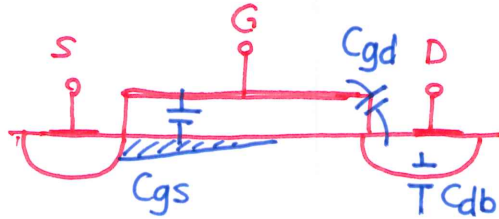


PARASITICS

IF C_{gs} DOMINATES

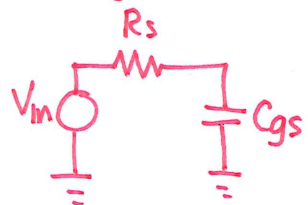

$$BW = \frac{1}{2\pi R_s C_{gs}}$$

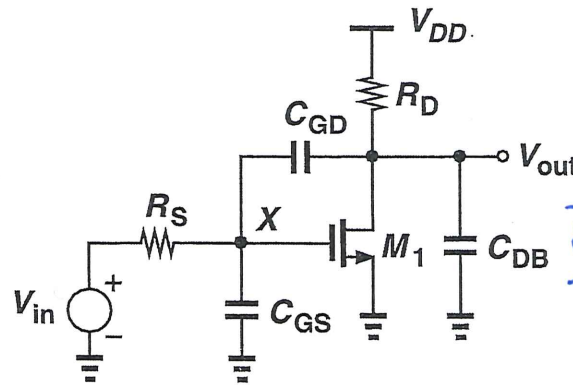


ANY C_L WILL ADD IN PARALLEL

Figure 6.10 High-frequency model of a common-source stage.



IF C_{DB} DOMINATES

$$BW = \frac{1}{2\pi R_D C_{DB}}$$

SMALL SIGNAL MODEL

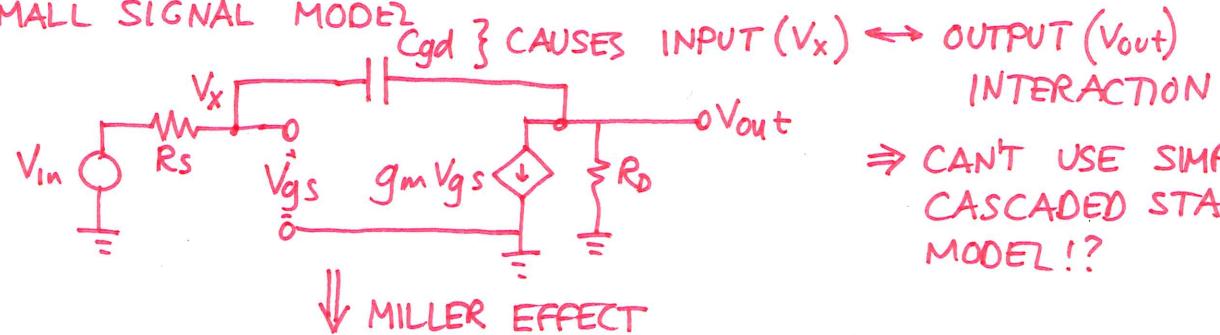


↓ MILLER EFFECT

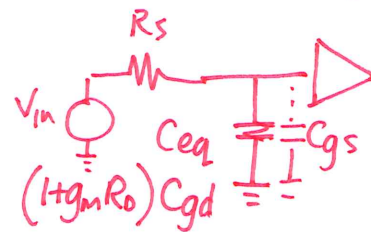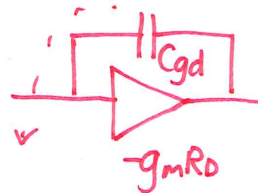



$$BW = \frac{1}{2\pi R_s [(1+g_m R_D) C_{gd} + C_{gs}]}$$

Differential pair motivation:


1) Op-amp input

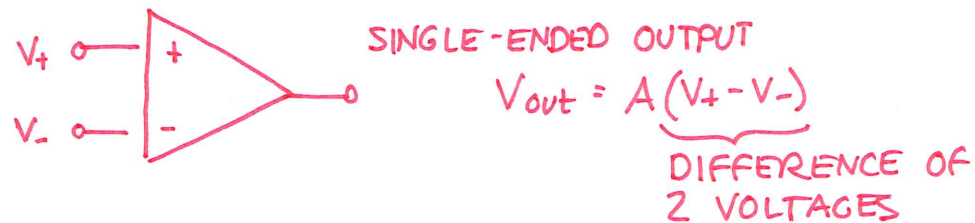

2) DC bias of common source amplifier

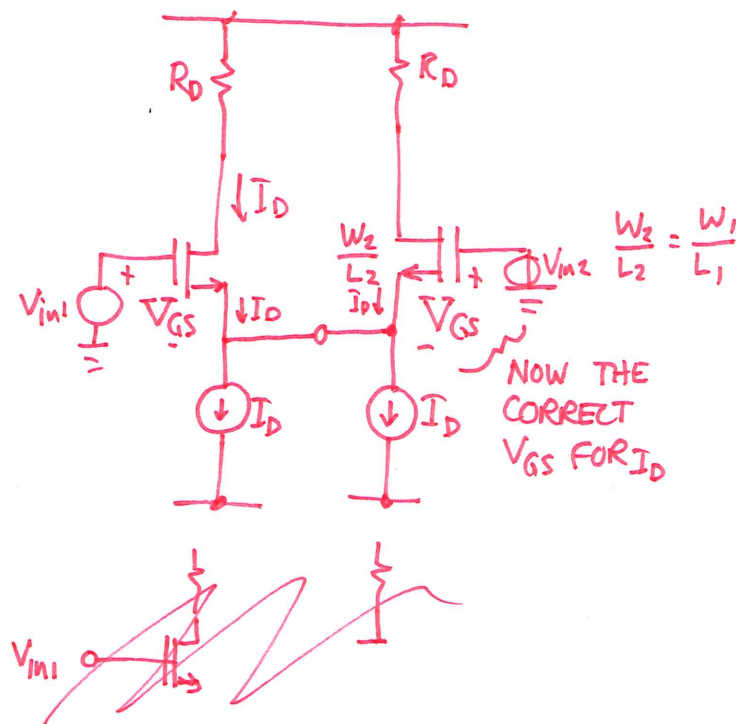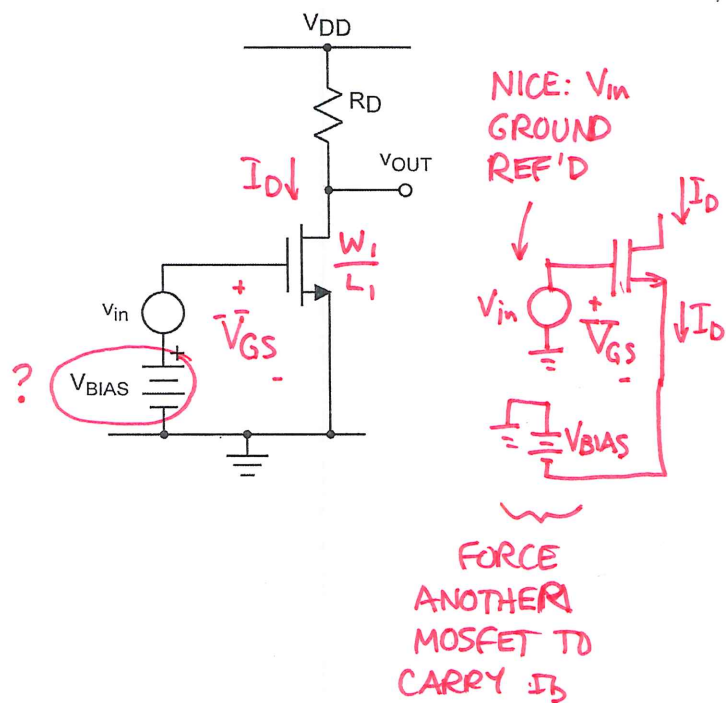

DIFFERENTIAL PAIR

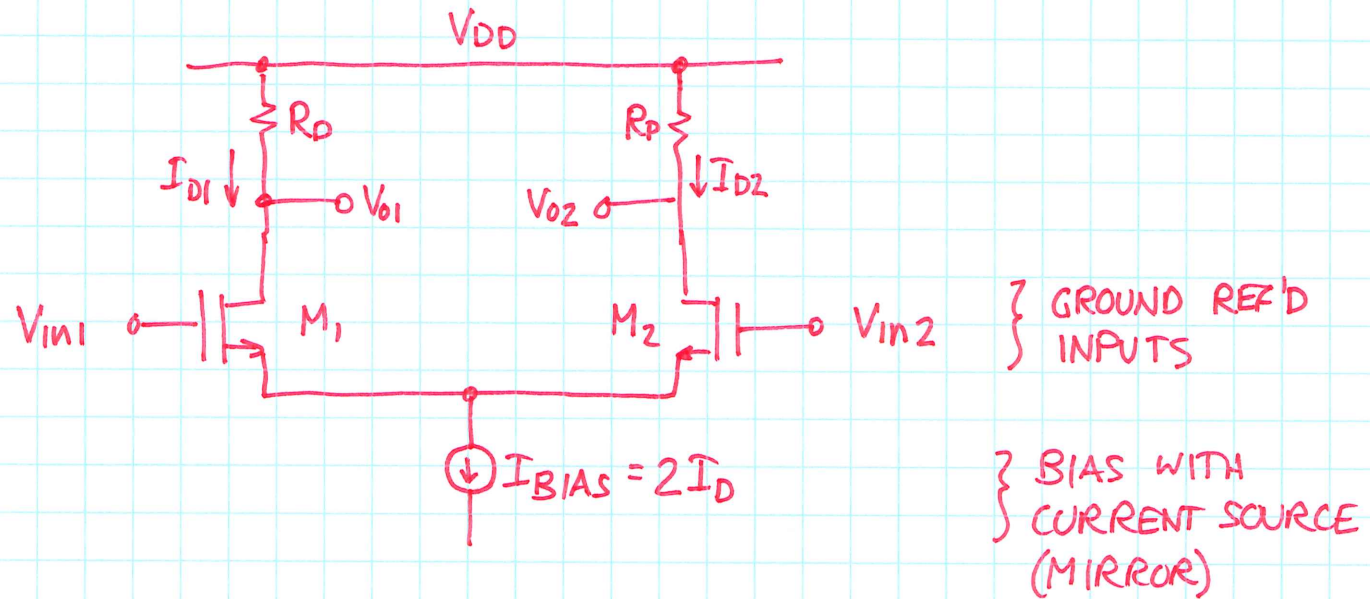

OUTPUT VOLTAGES:





$$V_{O1} = V_{DD} - I_{D1} R_D$$

$$V_{O2} = V_{DD} - I_{D2} R_D$$


Building up differential amplifier characteristic

ASSUME DRAIN VOLTAGES V_{D1}, V_{D2} OK FOR ACTIVE REGION
 $M_1 = M_2$ IDENTICAL


$V_+ \gg V_-$

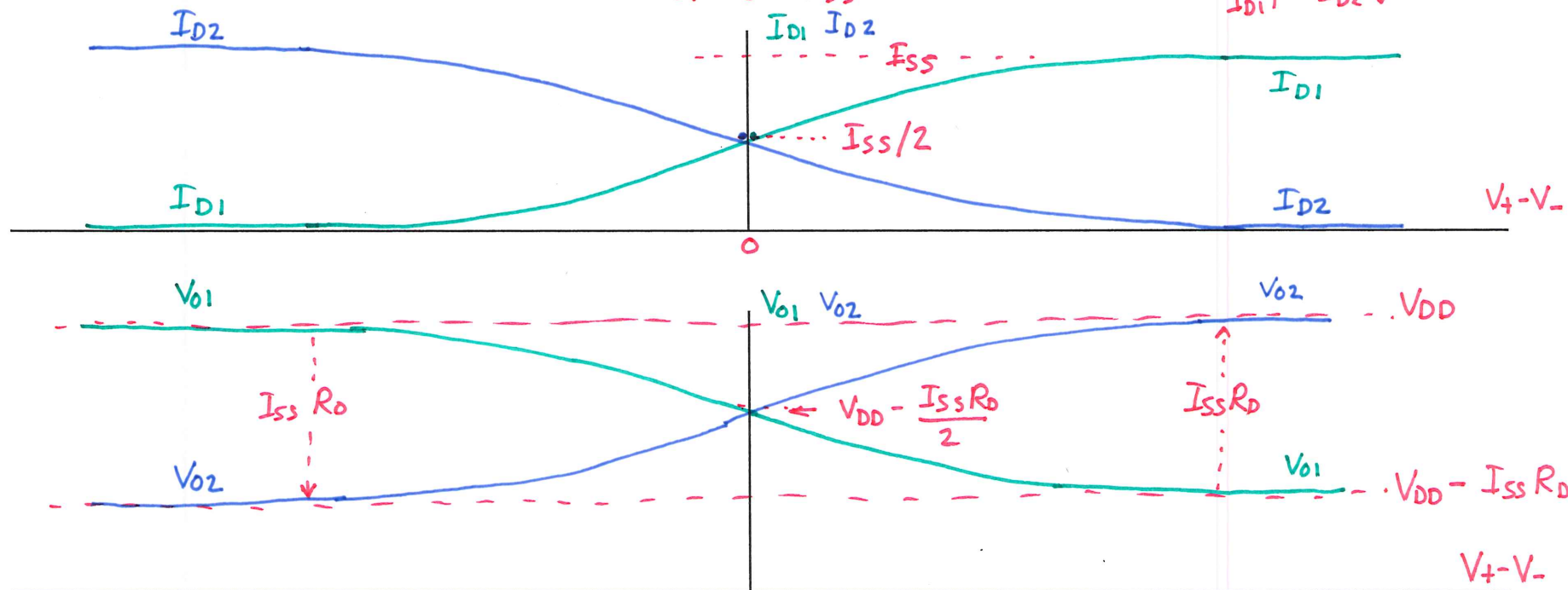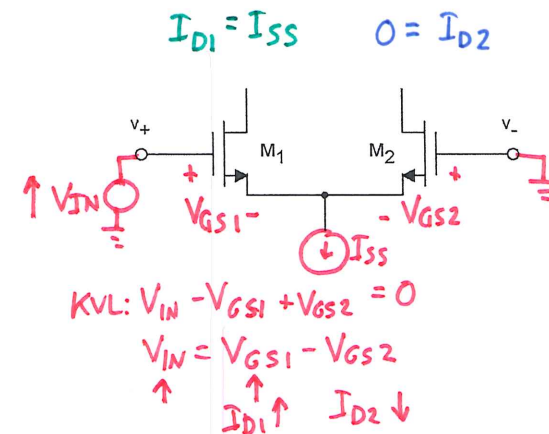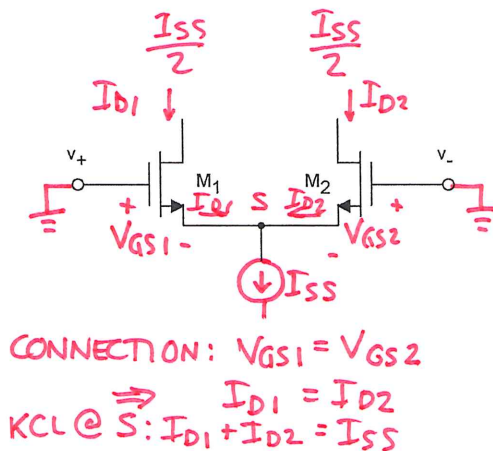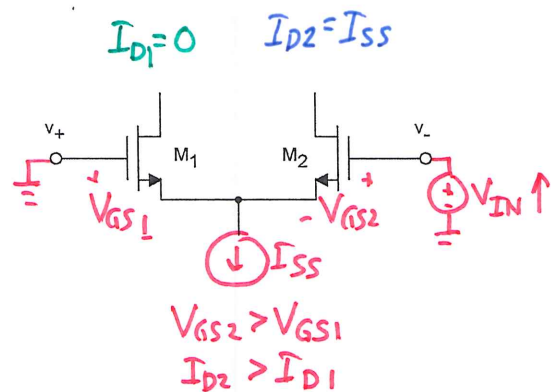

DIFFERENTIAL OUTPUT VOLTAGE

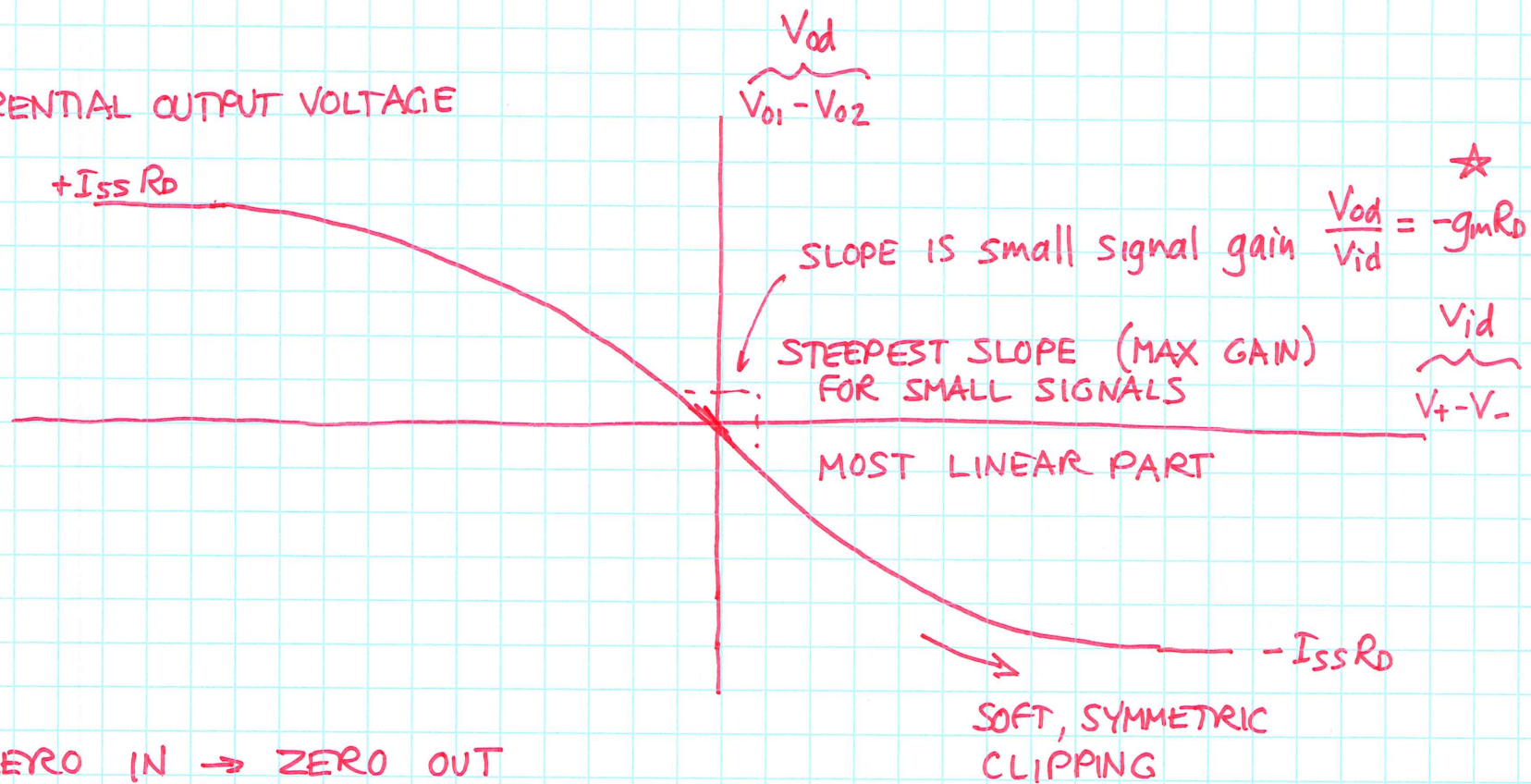

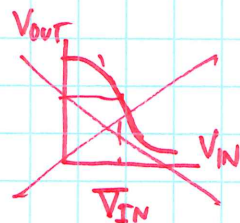
ZERO IN $\rightarrow$ ZERO OUT
 $V_{+} - V_{-}$ $V_{o1} - V_{o2}$



BARTLETT'S BISECTION THEOREM


Analysis using symmetry - "half circuit"

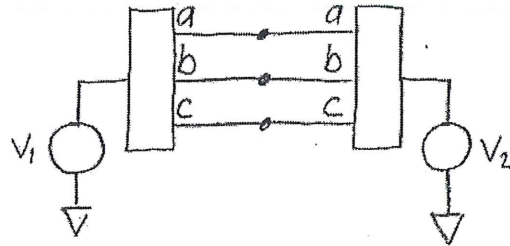Consider two completely symmetrical circuits;
a, b, c are connected points of symmetry




COMMON MODE

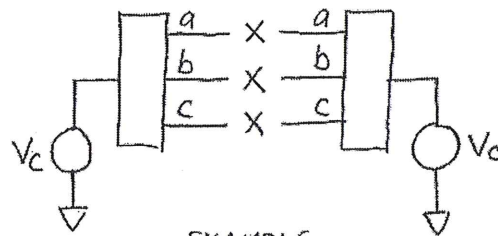If $V_1 = V_2 = V_c$ (both circuits have the same input; symmetric excitation) $\Rightarrow$ then we can open all leads between points of symmetry without affecting circuit operation; no current flows across any connection




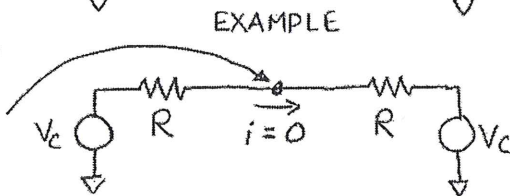EXAMPLE: $i = 0$ (no voltage drop across R_s due to symmetrical excitation. We can open this connection without affecting performance




DIFFERENTIAL MODE

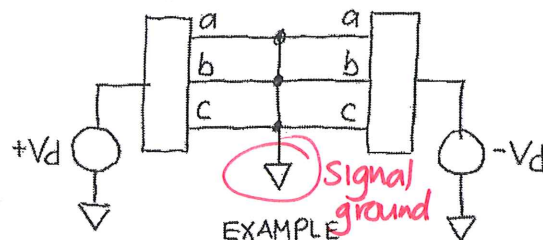If $V_1 = -V_2$ (antisymmetric excitation) $\Rightarrow$ then we can signal ground all leads between points of symmetry




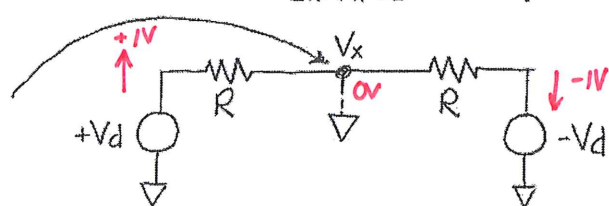EXAMPLE: by voltage divider, $V_x = 0$ regardless of V_d . Therefore we can signal ground this connection without affecting circuit performance



Any two signals can be expressed in terms of common mode, differential mode

Consider any V_1, V_2 :

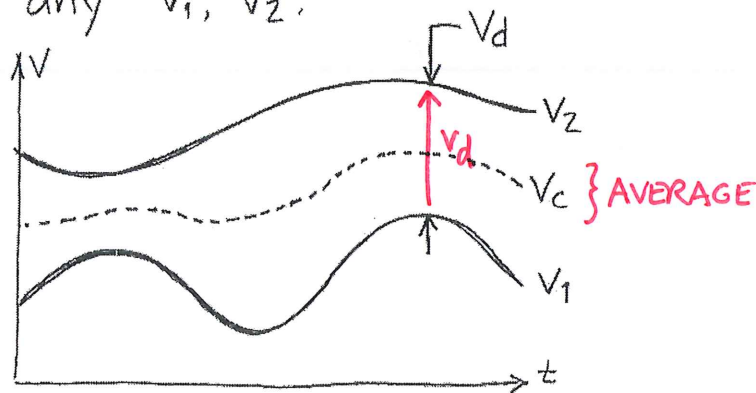

Define

$$V_c = \frac{V_1 + V_2}{2}$$


$$V_d = V_2 - V_1$$

straightforward to verify that




$$V_1 = V_c - \frac{V_d}{2}$$

$$V_2 = V_c + \frac{V_d}{2}$$

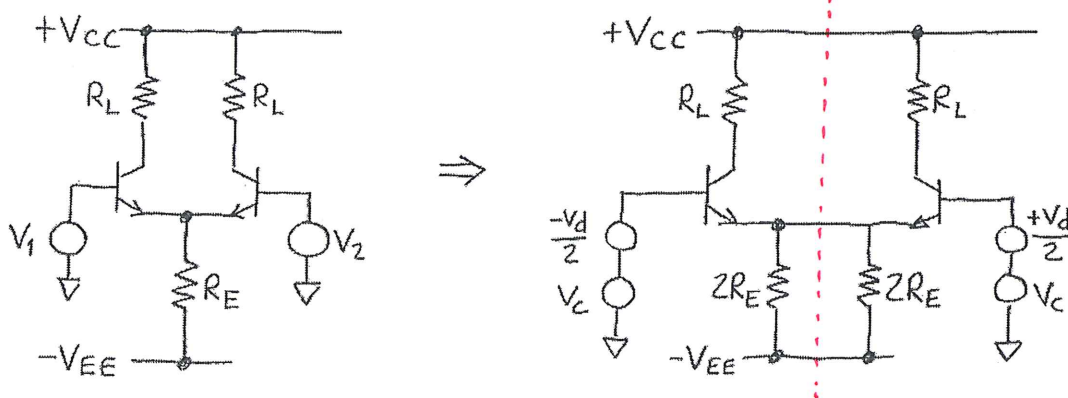
Key: analyze differential amplifier by decomposing inputs into V_c and V_d , then using symmetry (Bartlett's bisection theorem) and superposition



REDRAW FOR SPLIT

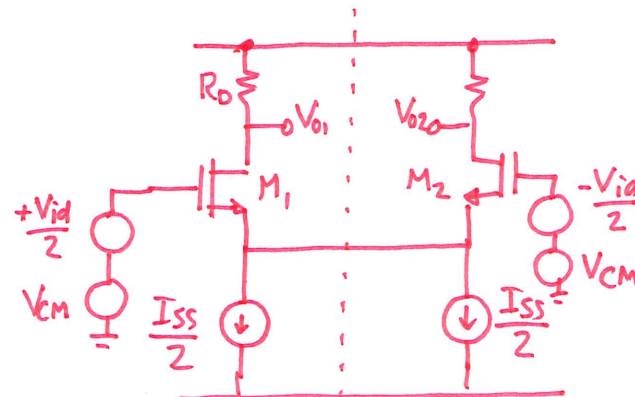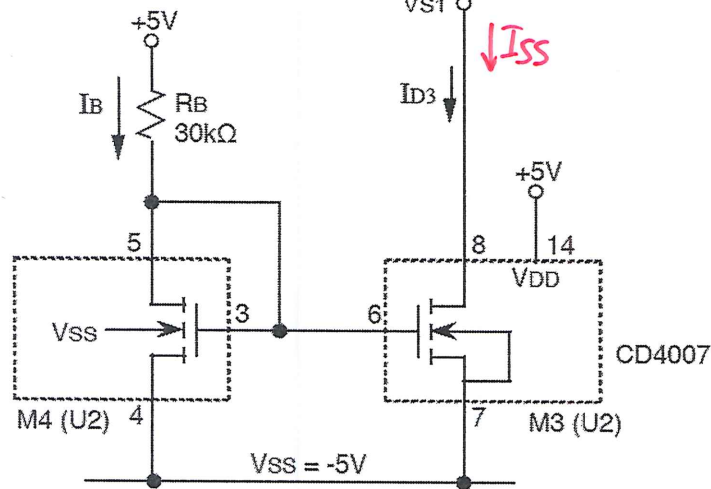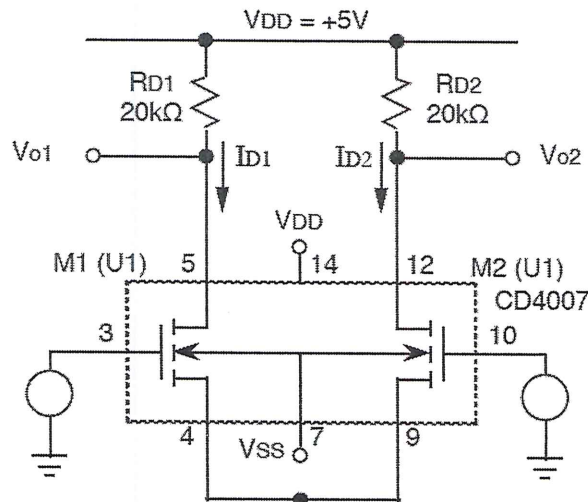

COMMON MODE

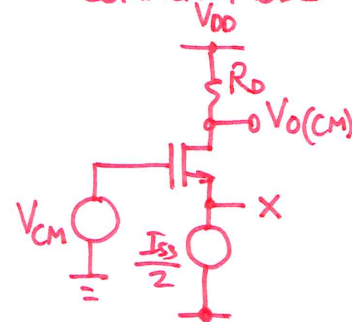


DC BIAS:

$$I_{D1} = \frac{I_{SS}}{2}$$

$$V_{O(CM)} = V_{DD} - \frac{I_{SS} R_D}{2}$$

DIFFERENTIAL MODE (small signal)

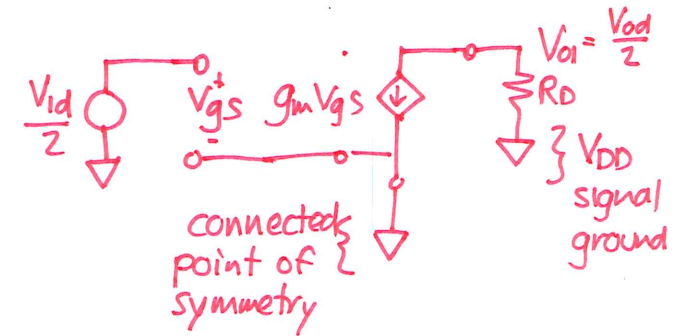

$$\frac{V_{od}/2}{V_{id}/2} = -g_m R_D \quad \left. \begin{array}{l} \text{same as} \\ \text{CS amplifier} \end{array} \right\}$$

★