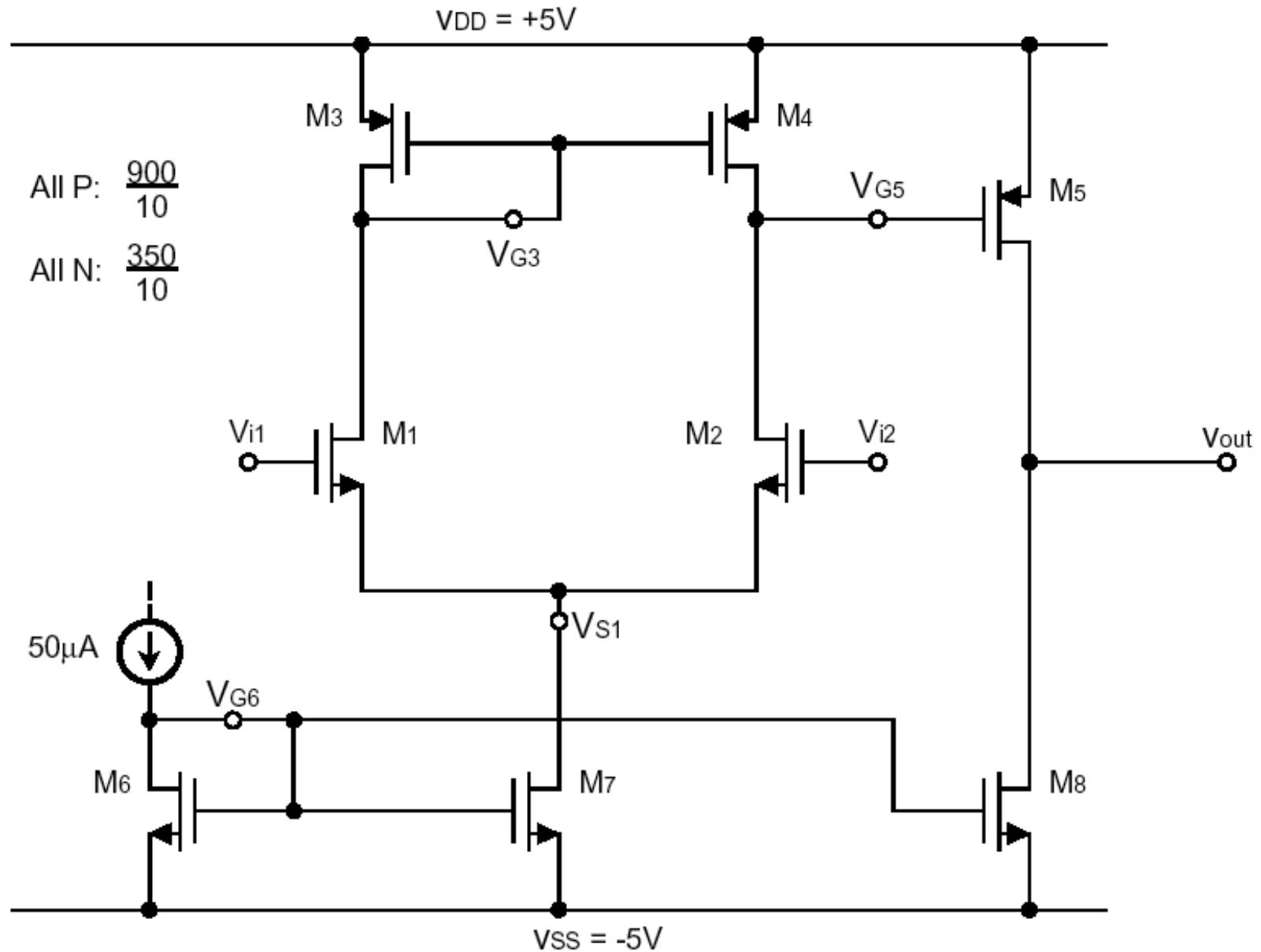


## **Labs 8 & 9 Review**


- **Operational Amplifier**
  - **Stability**
  - **Compensation**
  - **Miller Effect**
  - **Phase Margin**
  - **Unity Gain Frequency**
  - **Slew Rate Limiting**
- **Reading: Razavi ch. 9, 10**
  - **Lab 8, 9 op-amp is Fig. 10.34 in sec. 10.5.1**
  - **(see also Johns & Martin sec 5.2 pp. 232-242)**

# Two-stage op-amp



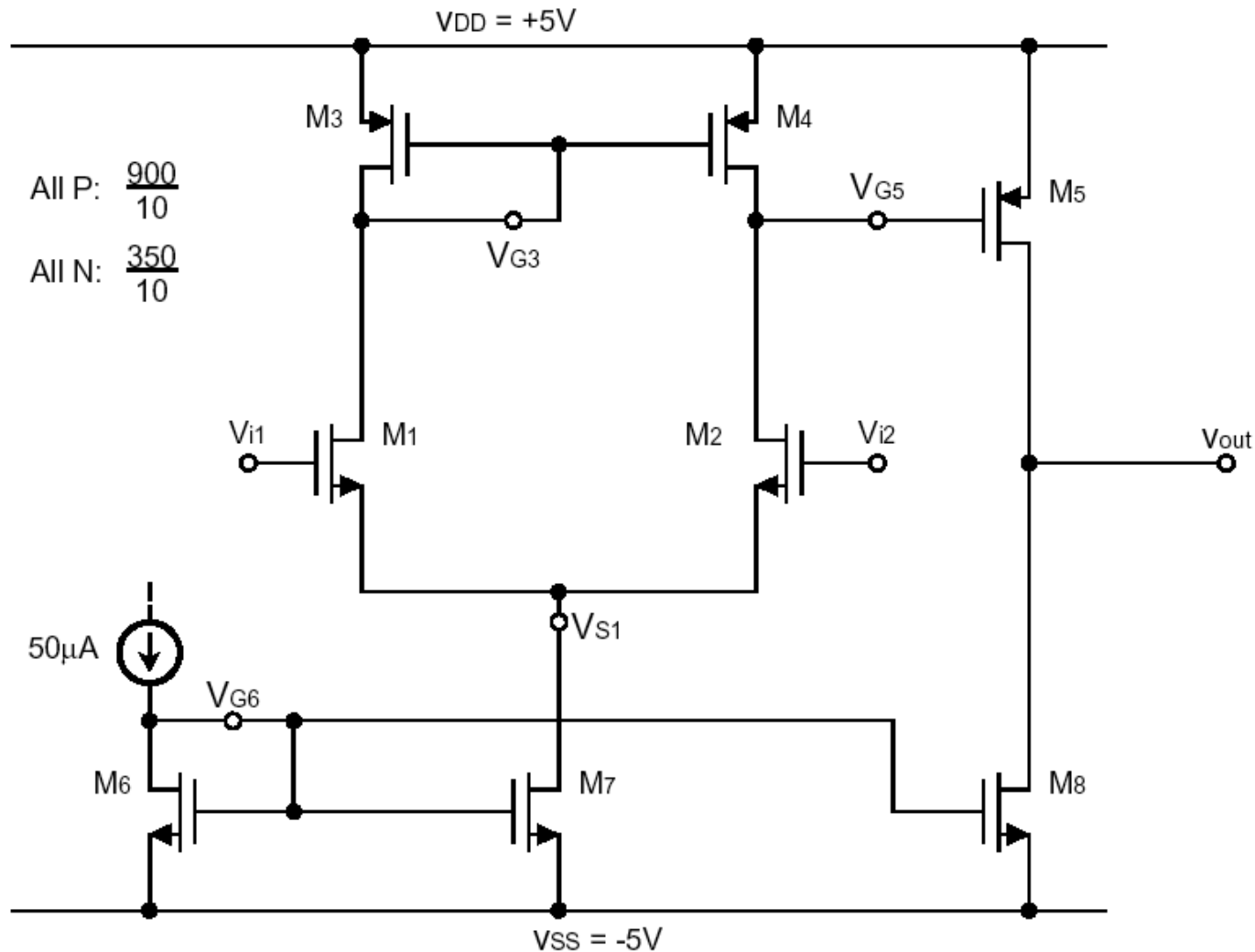
# Analysis Strategy

- Recognize sub-blocks
- Represent as cascade of simple stages



# Total op-amp model

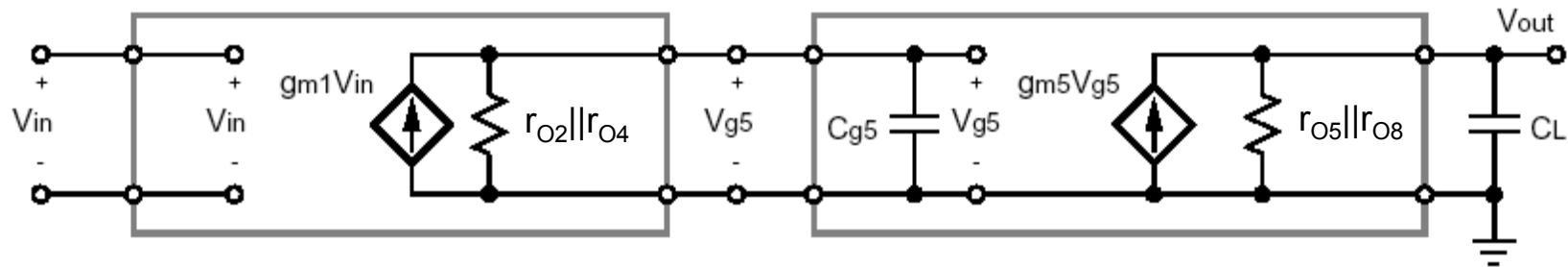

**Input differential pair      Common source stage**

## DC operating point


|           | $I_D[\mu A]$ | $V_{GS}-V_{TH}$ |
|-----------|--------------|-----------------|
| <b>M1</b> | <b>25</b>    | <b>0.235</b>    |
| <b>M2</b> | <b>25</b>    | <b>0.235</b>    |
| <b>M3</b> | <b>25</b>    | <b>0.247</b>    |
| <b>M4</b> | <b>25</b>    | <b>0.247</b>    |
| <b>M5</b> | <b>50</b>    | <b>0.350</b>    |
| <b>M6</b> | <b>50</b>    | <b>0.332</b>    |
| <b>M7</b> | <b>50</b>    | <b>0.332</b>    |
| <b>M8</b> | <b>50</b>    | <b>0.332</b>    |

## Small signal parameters

|           | $I_D[\mu A]$ | $V_{GS}-V_{TH}$ | $g_m[\mu A/V]$ | $r_o$                           |
|-----------|--------------|-----------------|----------------|---------------------------------|
| <b>M1</b> | <b>25</b>    | <b>0.235</b>    | <b>208</b>     |                                 |
| <b>M2</b> | <b>25</b>    | <b>0.235</b>    |                | <b>800k<math>\Omega</math></b>  |
| <b>M3</b> | <b>25</b>    | <b>0.247</b>    |                |                                 |
| <b>M4</b> | <b>25</b>    | <b>0.247</b>    |                | <b>1.43M<math>\Omega</math></b> |
| <b>M5</b> | <b>50</b>    | <b>0.350</b>    | <b>285</b>     | <b>715k<math>\Omega</math></b>  |
| <b>M6</b> | <b>50</b>    | <b>0.332</b>    |                |                                 |
| <b>M7</b> | <b>50</b>    | <b>0.332</b>    |                |                                 |
| <b>M8</b> | <b>50</b>    | <b>0.332</b>    |                | <b>400k<math>\Omega</math></b>  |

**Note:**  $\lambda_n = 0.050 \text{ V}^{-1}$  ;  $\lambda_p = 0.028 \text{ V}^{-1}$

# Total op-amp model: Low frequency gain

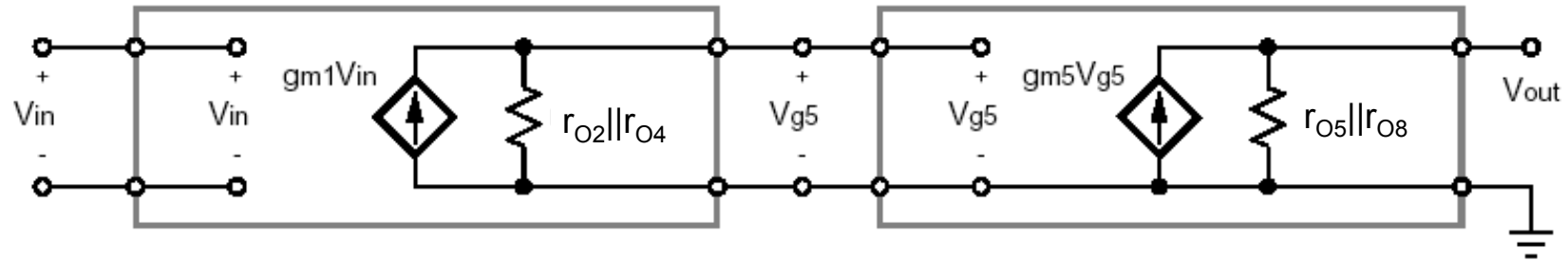

## Input differential pair

$$a_{v1} = g_{m1}(r_{O2}||r_{O4})$$

$$a_{v1} = (208\mu A/V)(800k\Omega||1.43M\Omega)$$

$$a_{v1} = 106$$


## Common source stage

$$a_{v2} = g_{m2}(r_{O5}||r_{O8})$$

$$a_{v2} = (285\mu A/V)(400k\Omega||715k\Omega)$$

$$a_{v2} = 73$$

# Total op-amp model with capacitances

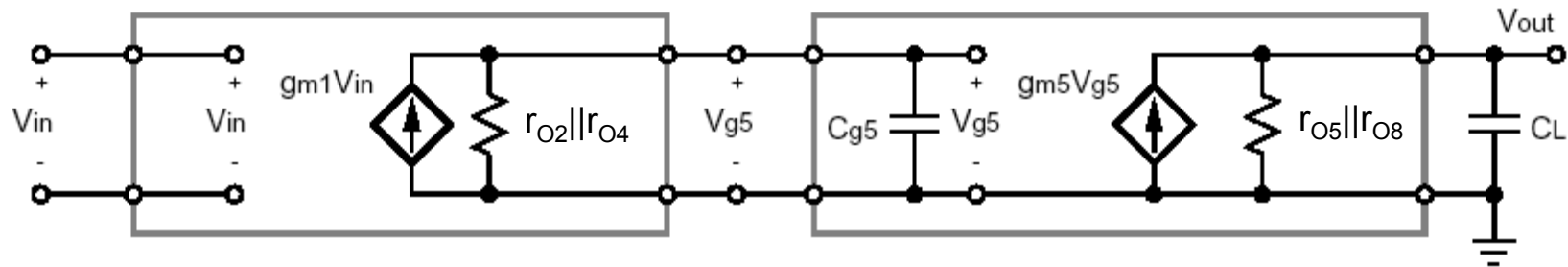


**Gate of M5**

**Load: scope probe  $\approx 10\text{pF}$**

$$C_g = (900\mu m)(10\mu m) \left( 4.17E - 4 \frac{F}{m^2} \right)$$

$$C_g = 3.74\text{pF}$$

# Total op-amp model with capacitances

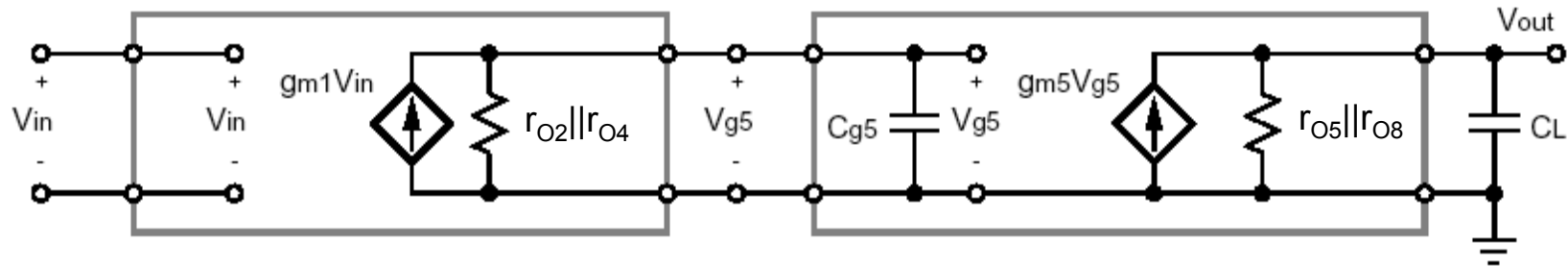

## First stage pole

$$f_{p1} = \frac{1}{2\pi(r_{O2} || r_{O4})C_{g5}}$$

$$f_{p1} = \frac{1}{2\pi(800k\Omega || 1.43M\Omega)(3.74pF)}$$

$$f_{p1} = 82kHz$$

## Second stage pole

$$f_{p1} = \frac{1}{2\pi(r_{O5} || r_{O8})C_L}$$

$$f_{p1} = \frac{1}{2\pi(400k\Omega || 715k\Omega)(10pF)}$$

$$f_{p1} = 61kHz$$

## Open loop transfer function

- **Product of individual stage transfer functions**


$$A(j\omega) = \frac{\overbrace{g_{m1}(r_{O2} \parallel r_{O4})}^{106} \overbrace{g_{m5}(r_{O5} \parallel r_{O8})}^{73}}{\left[1 + j\omega(r_{O2} \parallel r_{O4})C_{g5}\right] \left[1 + j\omega(r_{O5} \parallel r_{O8})C_L\right]}$$

- **Numerically (using  $\omega = 2\pi f$ )**

$$A(j\omega) = \frac{7738}{\left[1 + j\left(\frac{f}{82kHz}\right)\right] \left[1 + j\left(\frac{f}{61kHz}\right)\right]}$$


- **Check Bode plot simulation; predicts:**
  - DC gain =  $20\log(7738) = +78\text{dB}$
  - Unity gain frequency  $\sim 6.2\text{ MHz}$

# Two-stage op-amp: Simulation Schematic

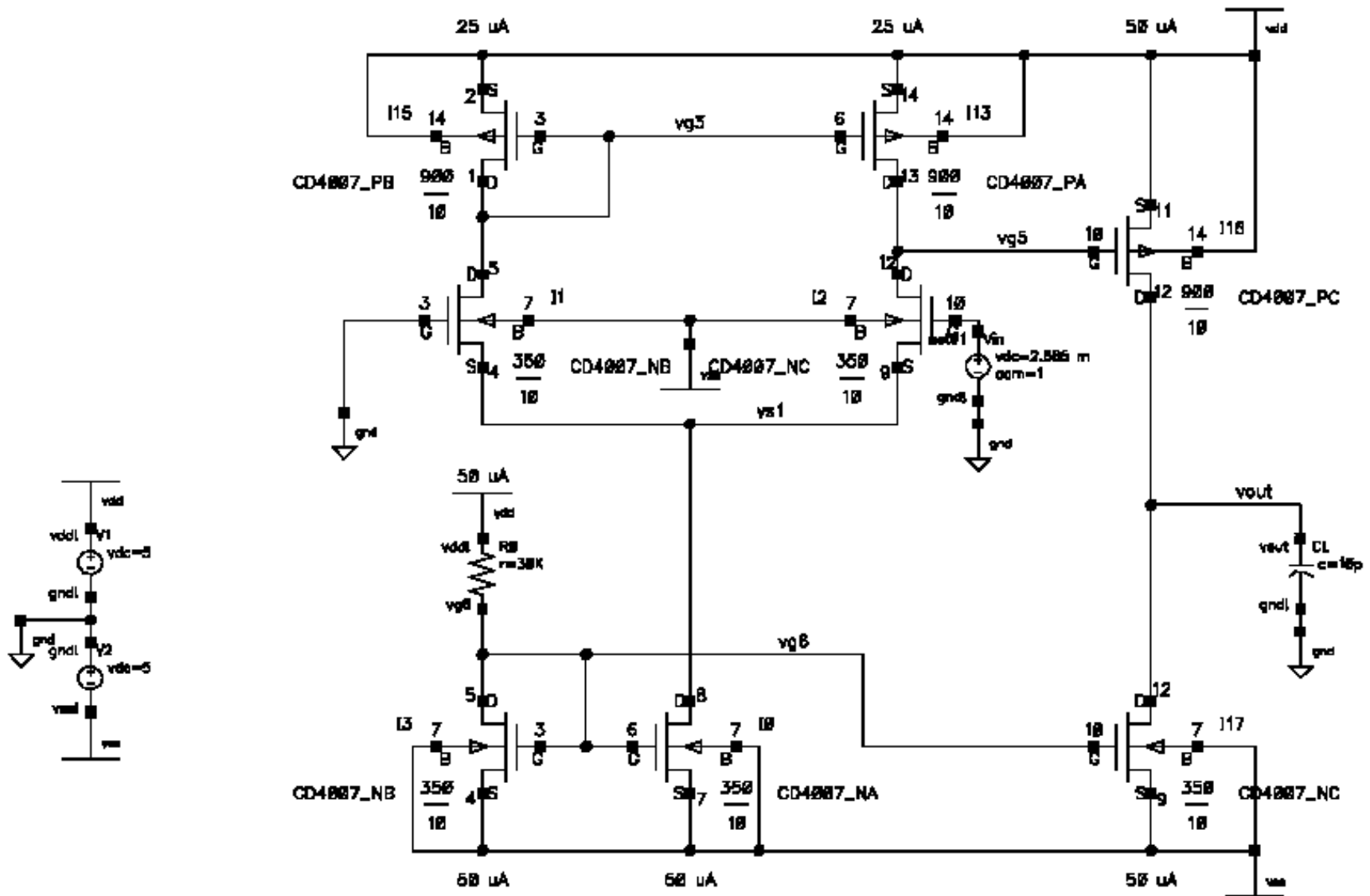


# DC Operating Point Simulation

DC Response

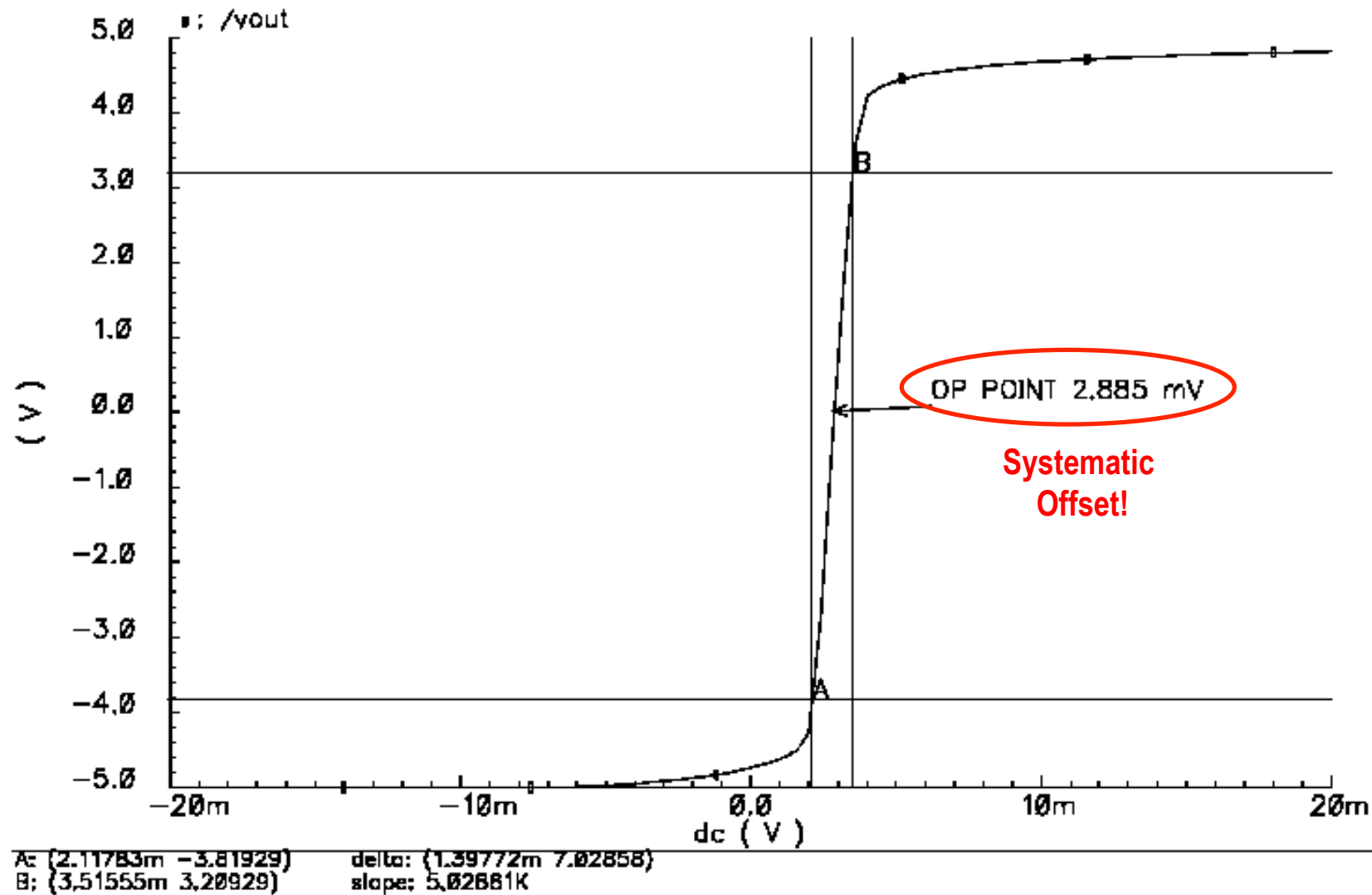


# Bode plot

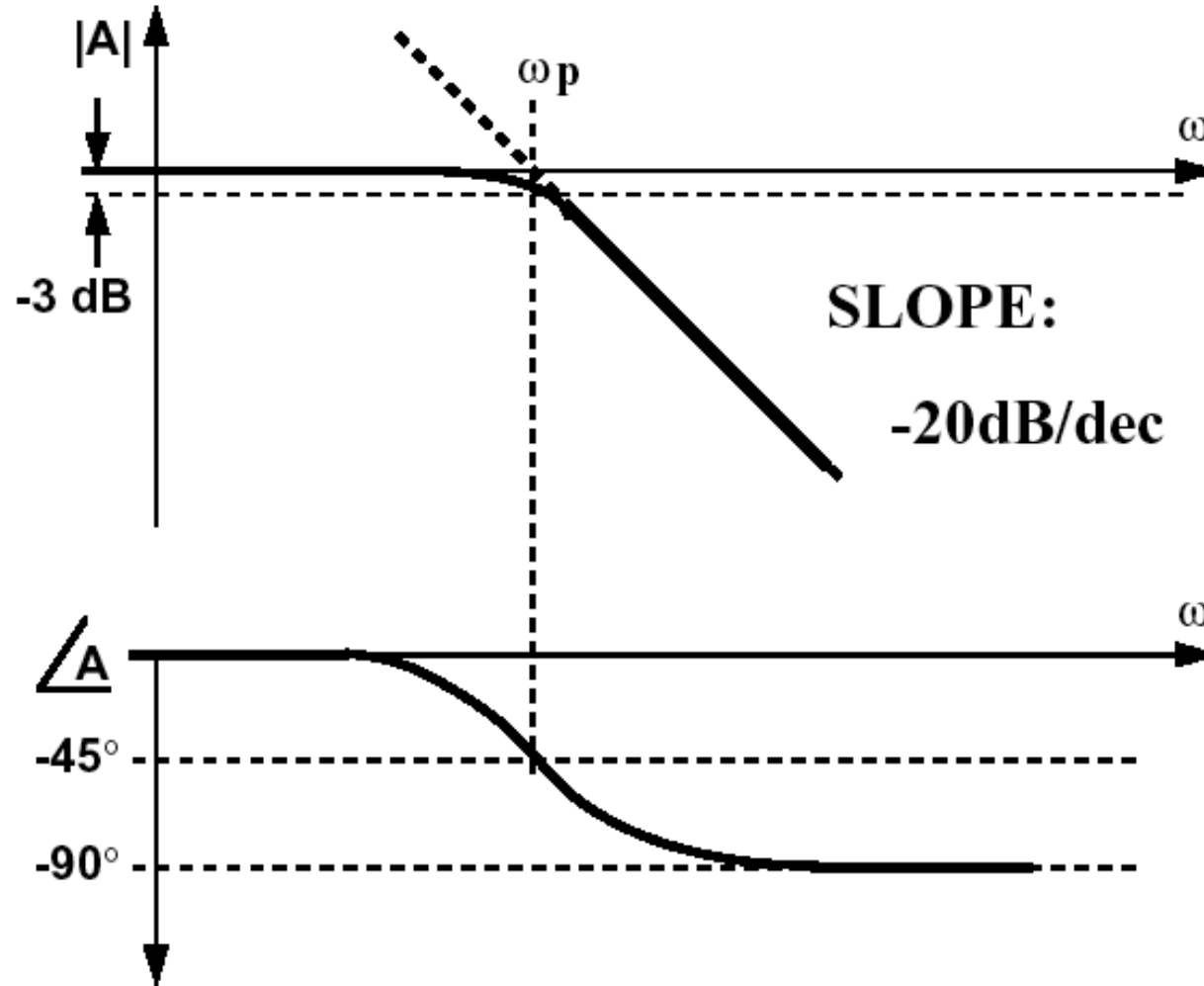


- **Magnitude, phase on log scales**
- **Pole: Root of denominator polynomial**

## Open loop Bode plot

- Product of terms : Sum on log-log plot

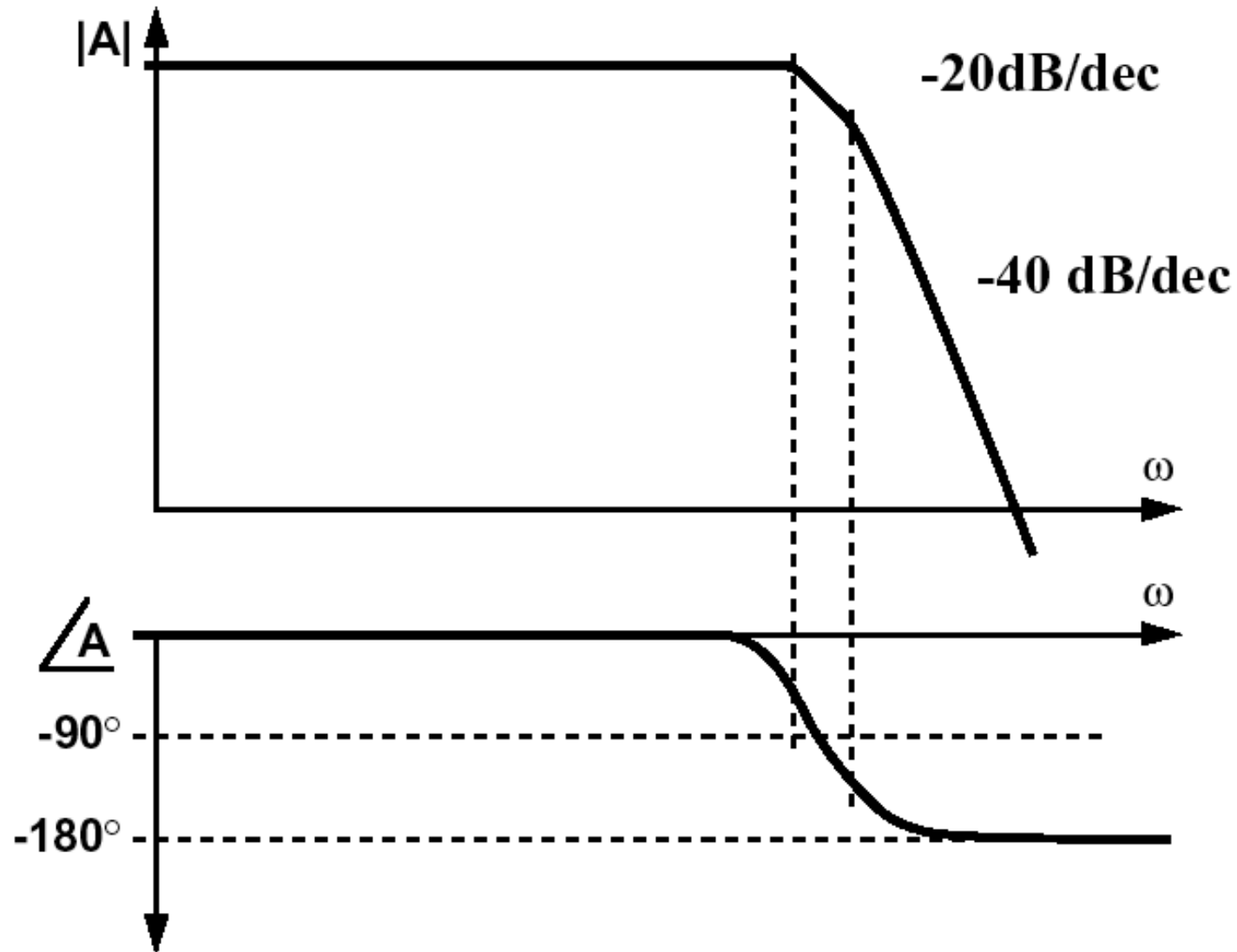


# Open Loop Bode Plot Simulation

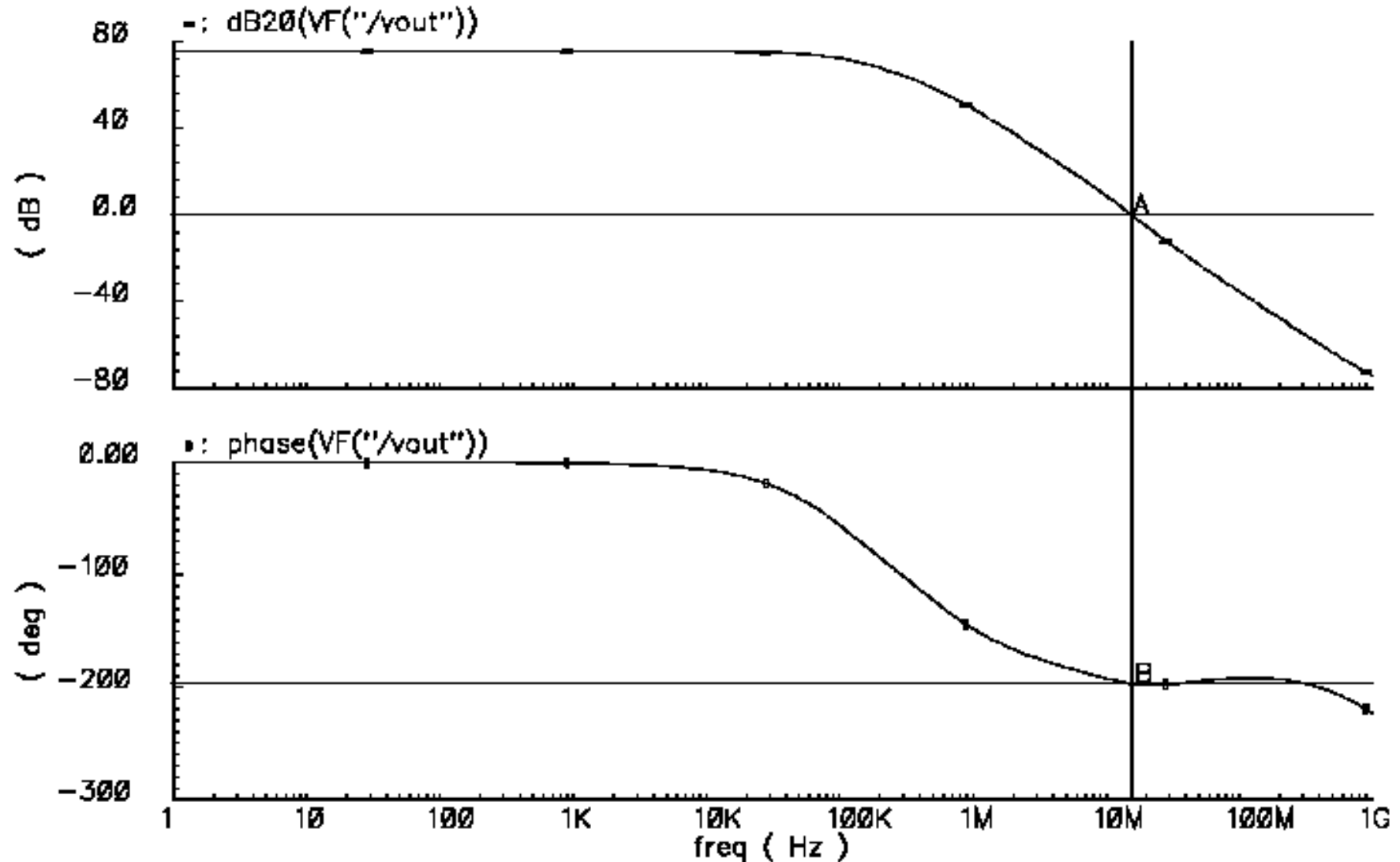


Note: AC source at input also needs DC component to account for systematic offset!

# Check Open Loop Bode Plot Simulation

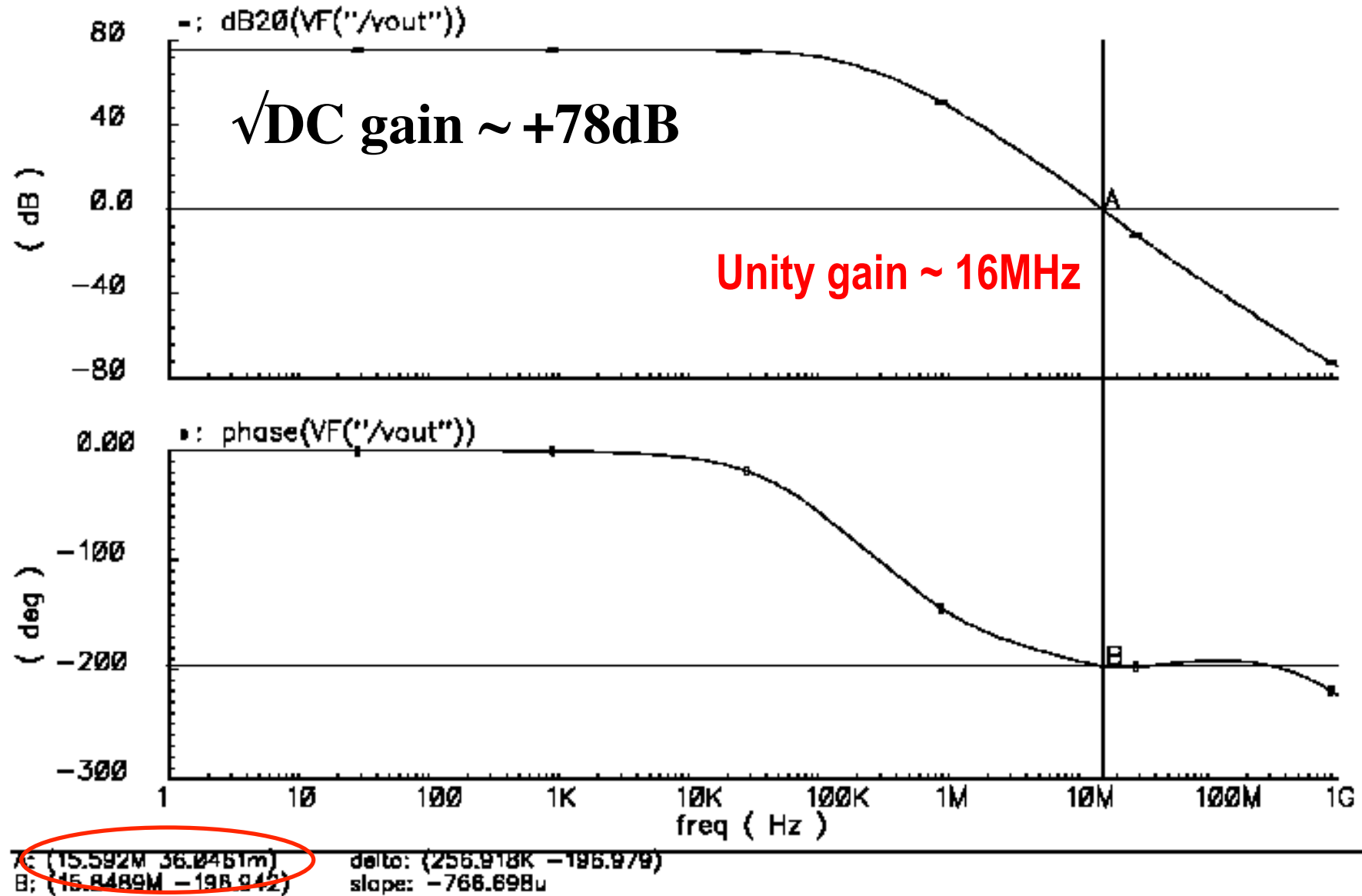
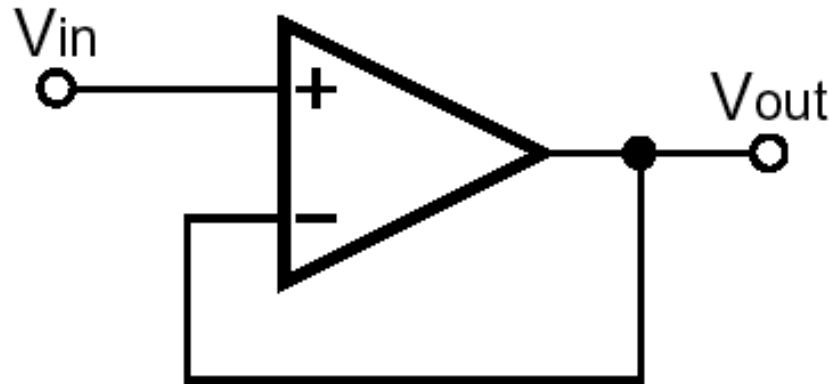
## Stability example: Closed loop follower



- **Negative feedback:**  
**Output connected to inverting input**
- **Gain should be  $\sim 1$**


$$v_{out} = A(v_{in} - v_{out})$$

$$v_{out}(A + 1) = Av_{in}$$

$$v_{out} = \underbrace{\left( \frac{A}{A + 1} \right)}_{\approx 1 \text{ as } A \gg 1} v_{in}$$

# Unity gain: Why bother?


SOURCE MODEL

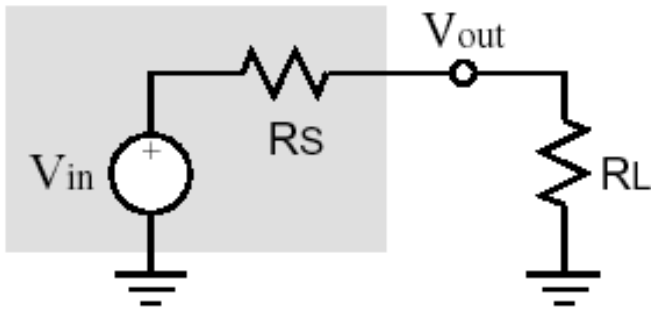

$$v_{out} = \left( \frac{R_L}{R_L + R_S} \right) v_{in}$$

- **No buffer:**  
Voltage divider
- **Signal reduced due to voltage drop across  $R_S$**

SOURCE MODEL


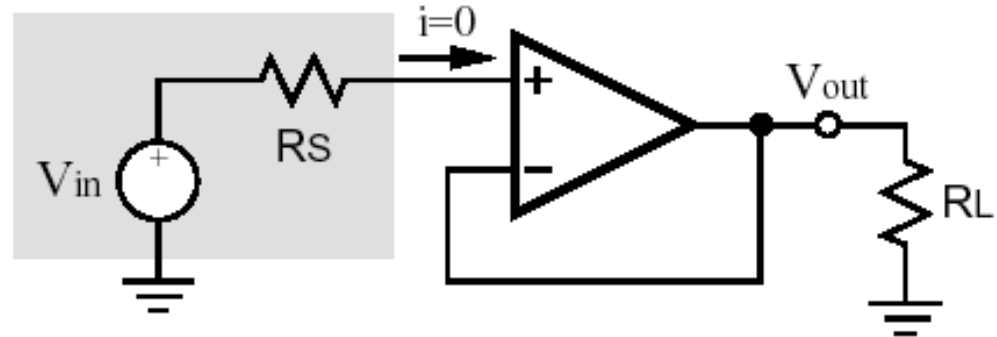


$$v_{out} = v_{in}$$

- **With buffer:**  
No current required from source
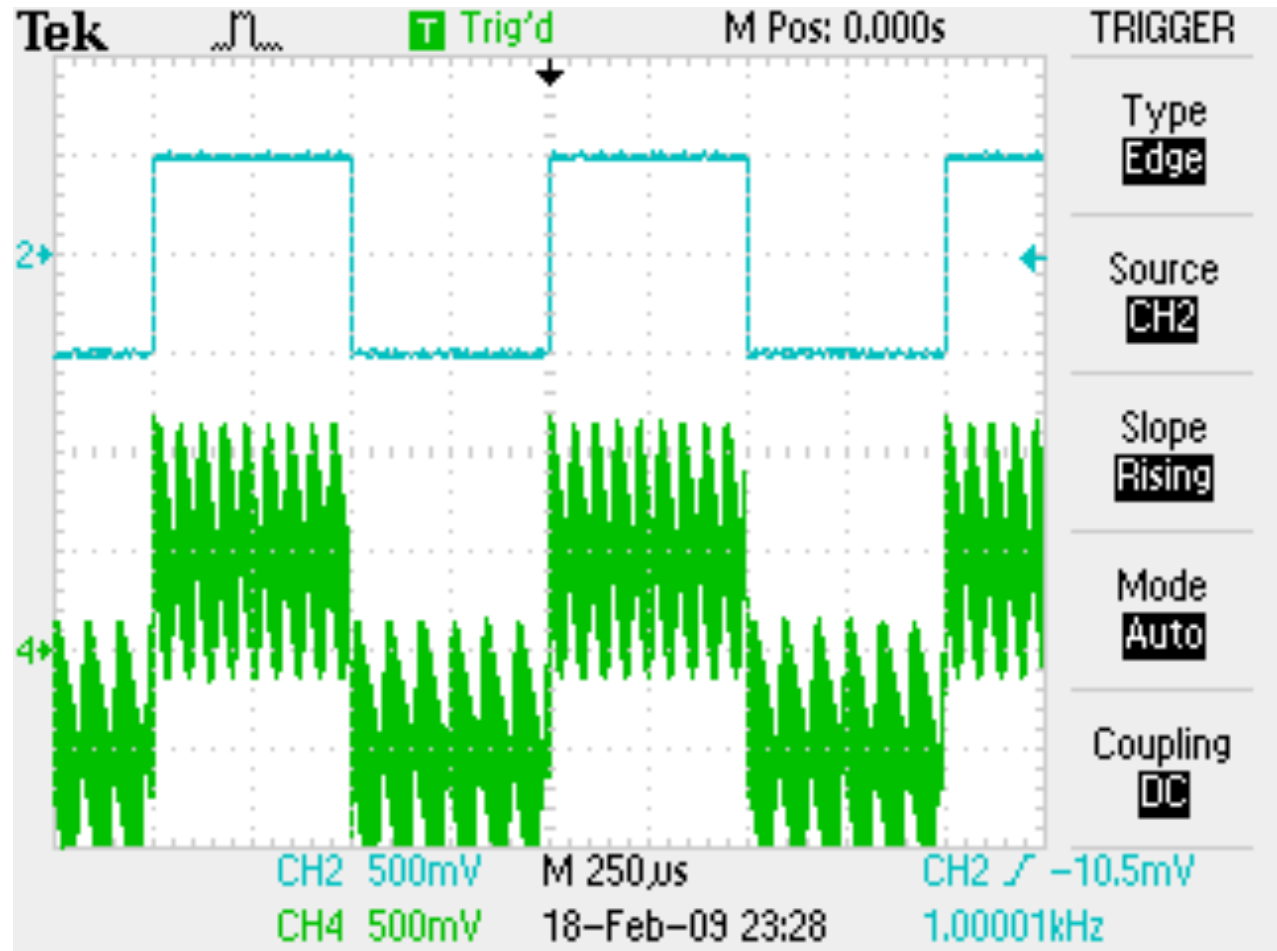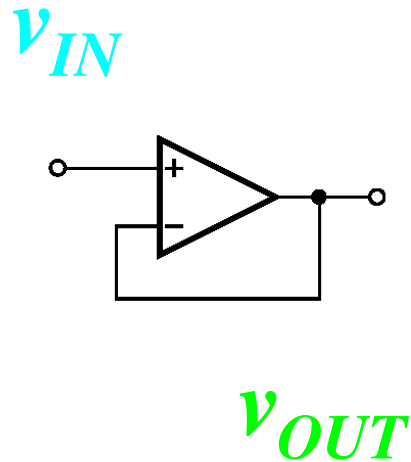
## Lab 9 Problem: Instability


- Oscillation superimposed on desired output!?!




## Lab 9 Problem: Instability

- Ground  $v_{in}$ : Output for zero input?!?
- Why? Need...

$v_{IN}$

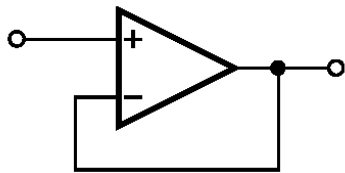


$v_{OUT}$

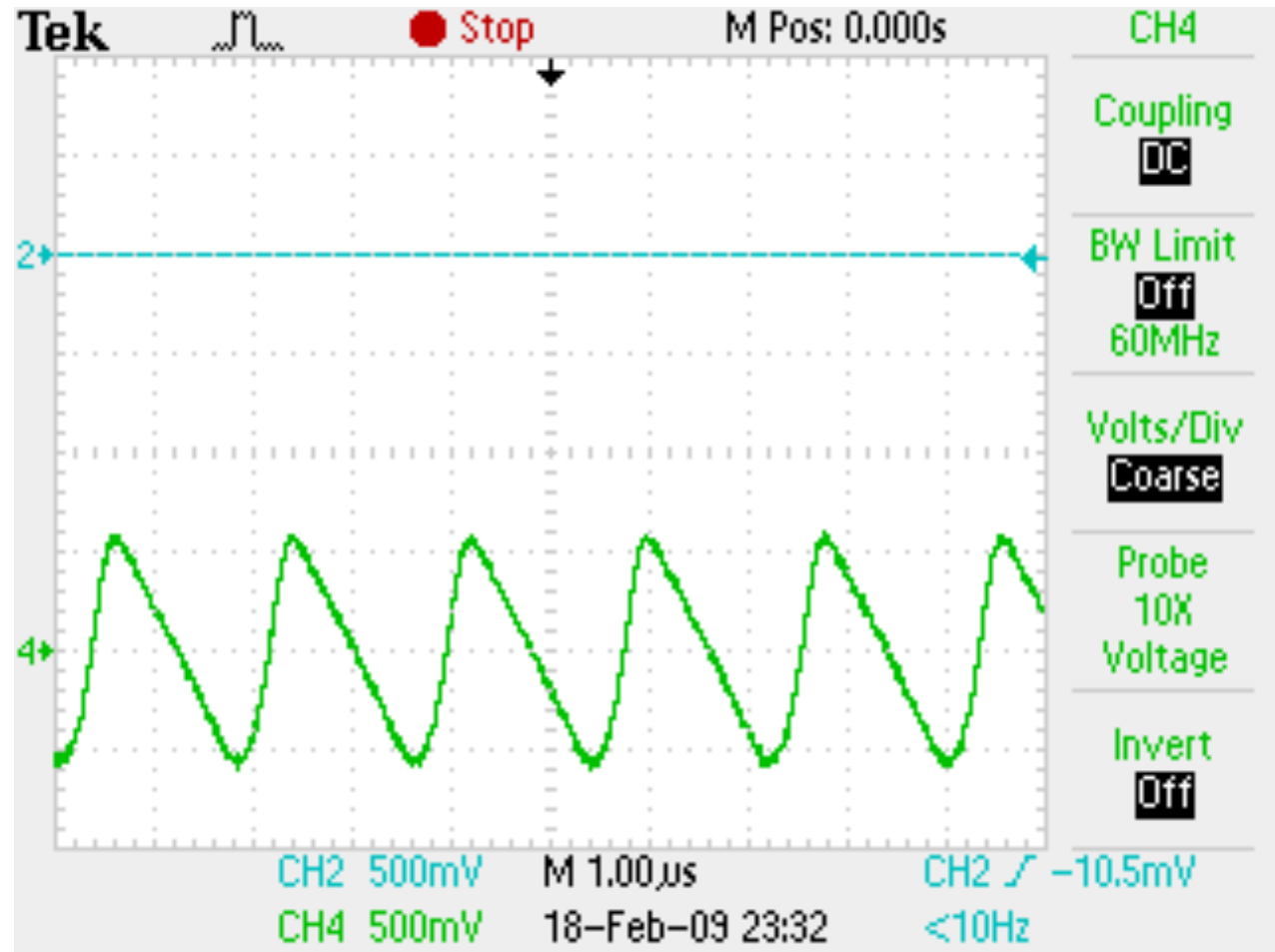
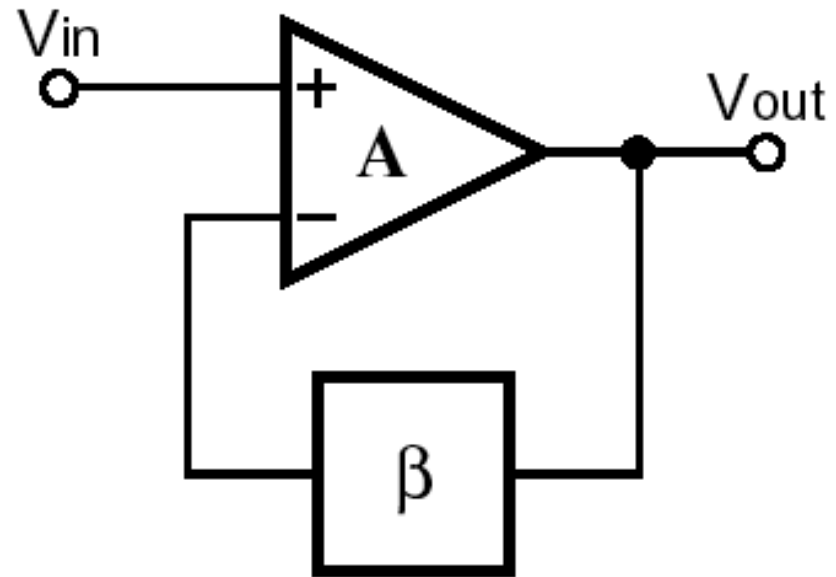
## Controls: ECE3012 in 20 minutes

- **General framework**  
**A: Forward Gain**  
 **$\beta$ : Feedback Factor**  
fraction of output  
fed back to input



## Example: Op-amp, Noninverting Gain

**A: Forward Gain**


**Op-amp open loop gain**

$$V_{\text{out}} = A(V_{+} - V_{-})$$

**Transfer function  $A(j\omega)$**

**$\beta$ : Feedback Factor**

$$\beta = \frac{R_1}{R_1 + R_2}$$

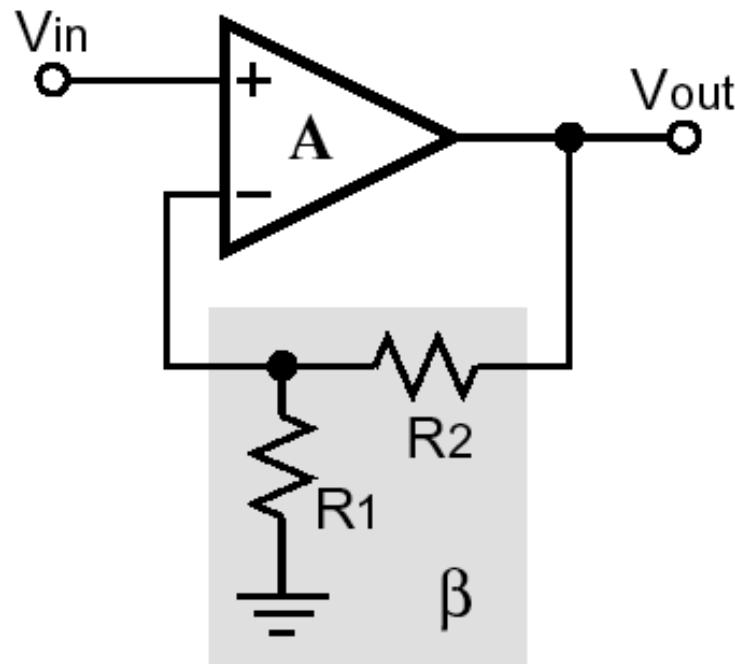

# Closed Loop Gain

- **Output**


$$v_{out} = A \underbrace{(v_{in} - \beta v_{out})}_{v_+ - v_-}$$

- **Solve for  $v_{out}/v_{in}$**

$$v_{out} = Av_{in} - A\beta v_{out}$$

$$(1 + A\beta)v_{out} = Av_{in}$$
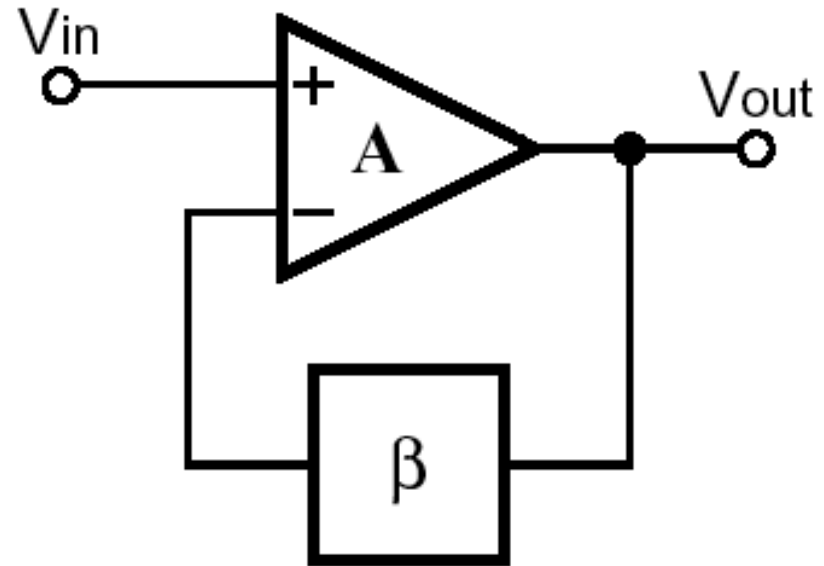
$$\boxed{\frac{v_{out}}{v_{in}} = \frac{A}{1 + A\beta}}$$



## Op-amp with negative feedback

- If  $A\beta \gg 1$

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + A\beta} \approx \frac{A}{A\beta} \rightarrow \frac{v_{out}}{v_{in}} \approx \frac{1}{\beta}$$

- Closed loop gain determined only by  $\beta$
- Advantage of negative feedback:  
Open loop gain  $A$  can be ugly (nonlinear, poorly controlled) as long as it's large!


## Example: Op-amp, Noninverting Gain

**$\beta$ : Feedback Factor**

$$\beta = \frac{R_1}{R_1 + R_2}$$

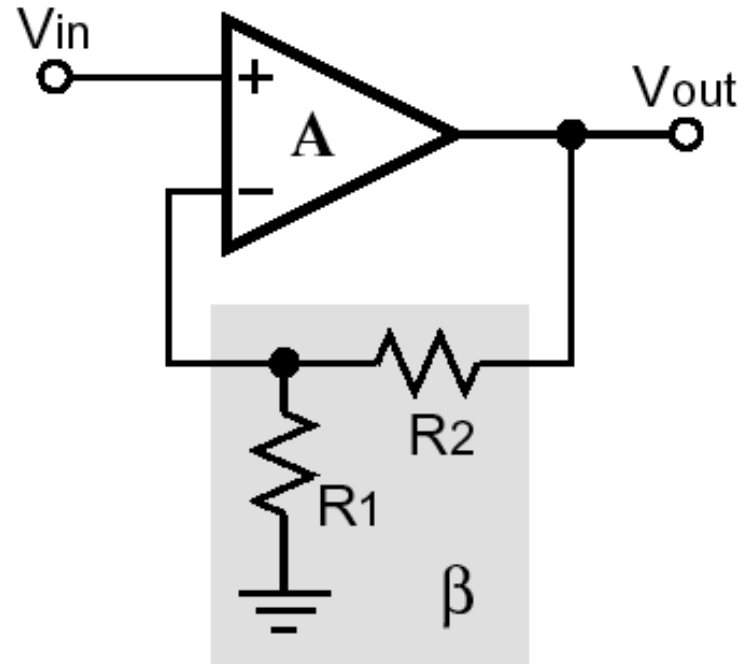**Closed loop gain**

$$\frac{v_{out}}{v_{in}} = \frac{R_1 + R_2}{R_1} = \frac{1}{\beta}$$




## Reexamine closed loop transfer function

- **Output with no input:  
infinite gain**
- **Infinite when  $1+A\beta = 0$**
- **Condition for oscillation:**  
$$1+A\beta = 0$$
- **In general  $A, \beta$  functions of  $\omega$**
- **If there's a frequency  $\omega$  at which  $1+A\beta = 0$ :  
Oscillation at that frequency!**

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + A\beta}$$
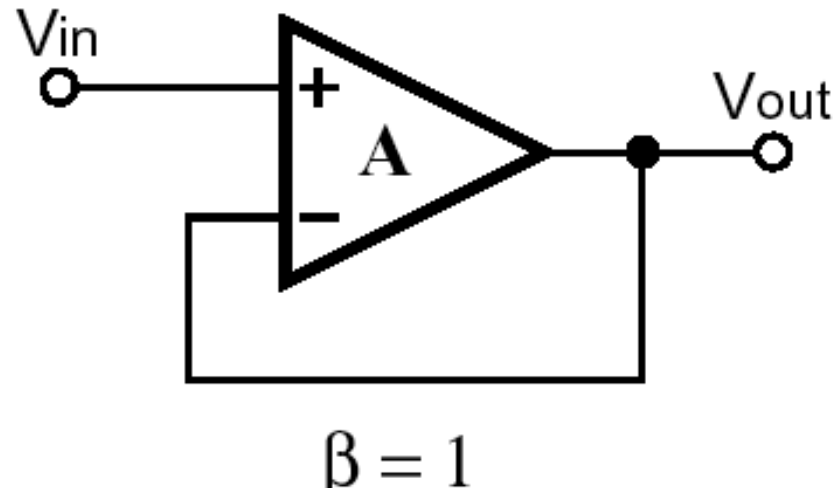
## Example: follower

$$\beta = 1 \rightarrow \frac{v_{out}}{v_{in}} = \frac{A}{1 + A}$$



- Use  $A(j\omega)$ ,  
solve for  $1+A = 0$
- No thanks!

$$A(j\omega) = \frac{g_{m1}(r_{O2} \parallel r_{O4})g_{m5}(r_{O5} \parallel r_{O8})}{\left[1 + j\omega(r_{O2} \parallel r_{O4})C_{g5}\right]\left[1 + j\omega(r_{O5} \parallel r_{O8})C_L\right]}$$

## Reexamine condition for oscillation

$$1 + A\beta = 0 \rightarrow A\beta = -1$$


**Magnitude and phase condition:**

$$|A\beta| = 1 \quad \text{AND} \quad \angle A\beta = -180^\circ$$

- **Easier to get from Bode plot**


## Look at original $A\beta$ for 2 stage op-amp

- Find  $\omega$  at which  $|A\beta| = 1$ ; Check  $\angle A\beta - 180^\circ$  ?

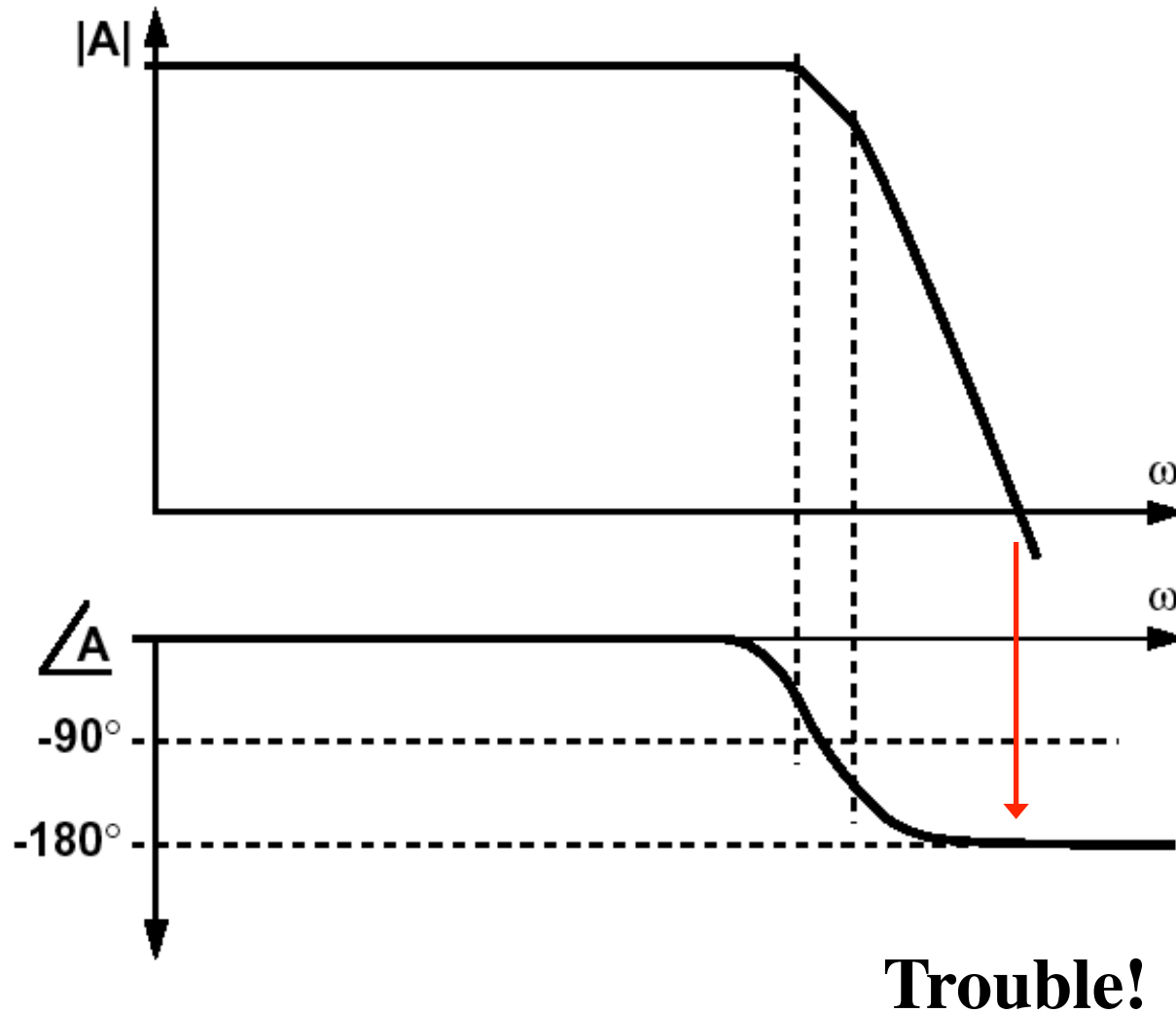

# Simulation $A\beta$ for 2 stage op-amp


AC Response

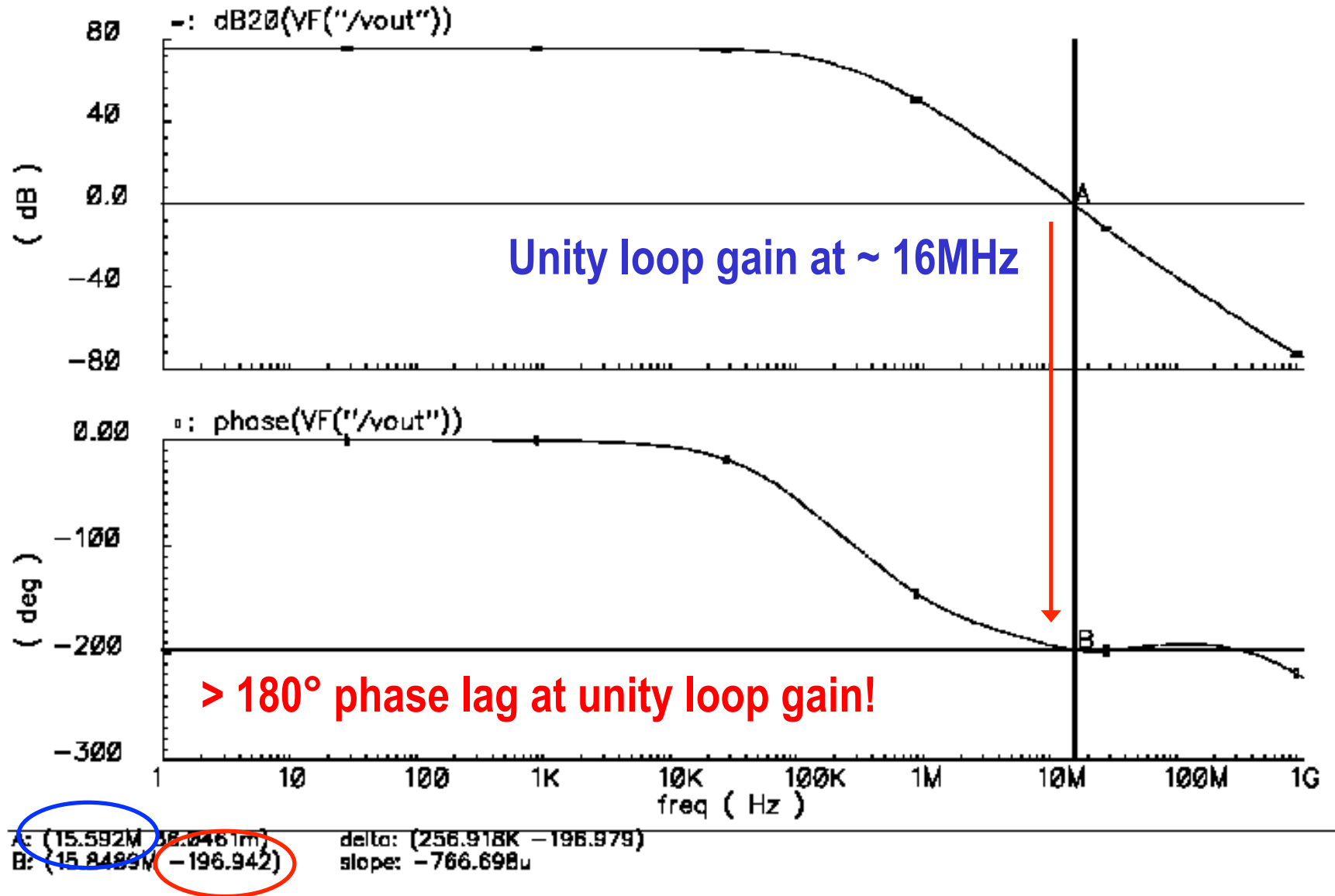

- Causes closed-loop instability
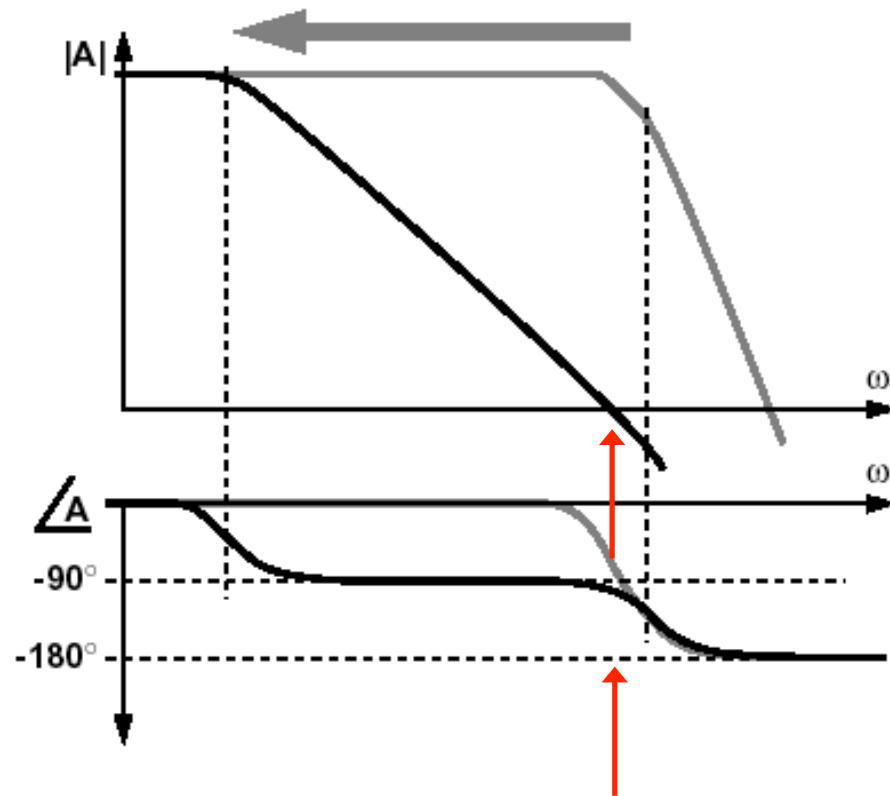
# Compensation: “Dominant Pole”

- Move one pole to lower frequency
- How?





Move unity loop gain frequency  $f_T$  to lower value

So accumulated phase lag at  $f_T$  hasn't reached  $-180^\circ$

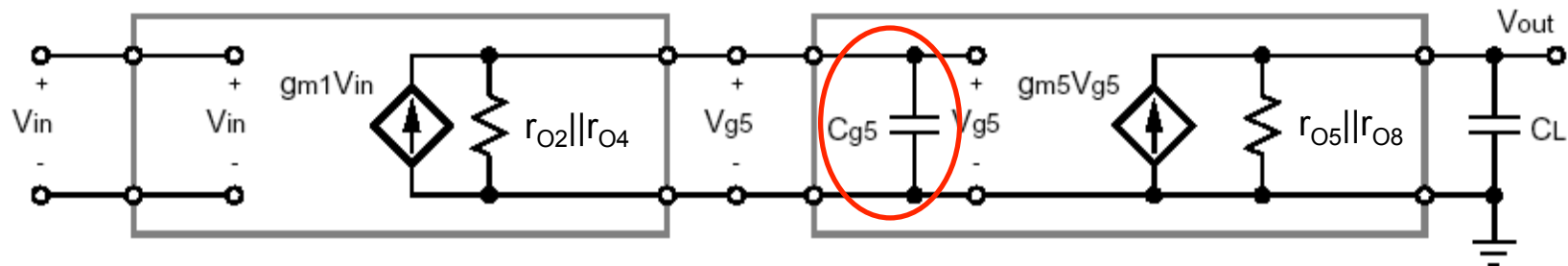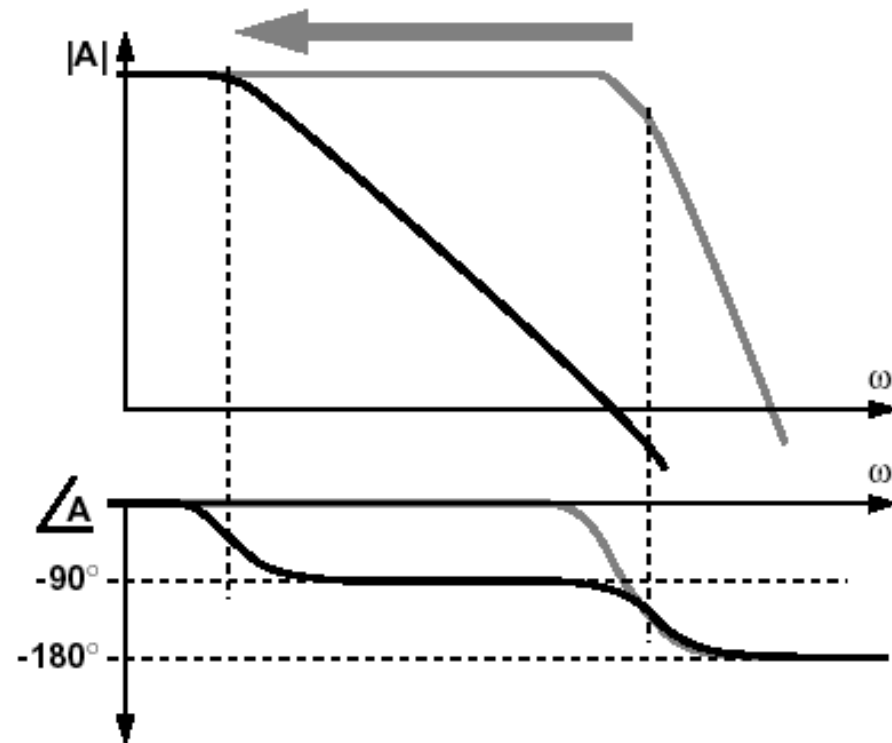
# Compensation: “Dominant Pole”

- Need to increase capacitance by  $\approx 1000\times$ :  
**BAD! Die area cost**


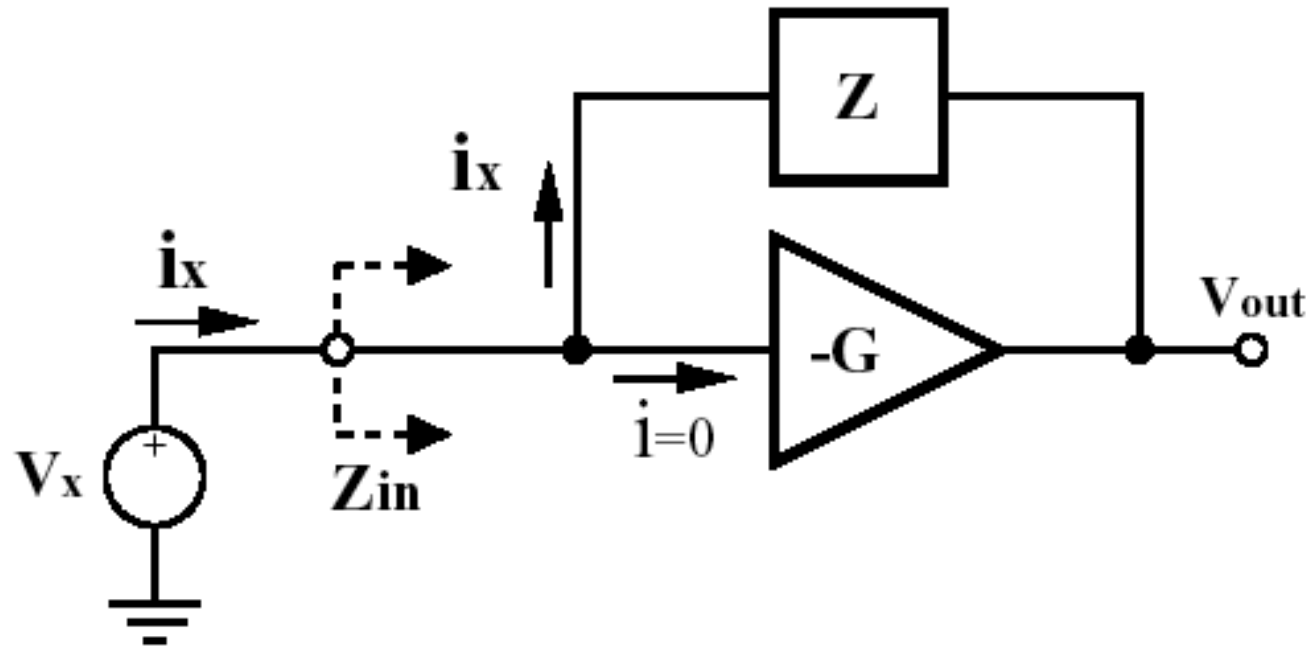
# Miller Effect

- Impedance across inverting gain stage  $G$
- Reduced by factor equal to  $(1+G)$




## Math for Miller effect

$$i_x = \frac{v_x - (-Gv_x)}{Z}$$

$$i_x = \frac{v_x(1+G)}{Z}$$
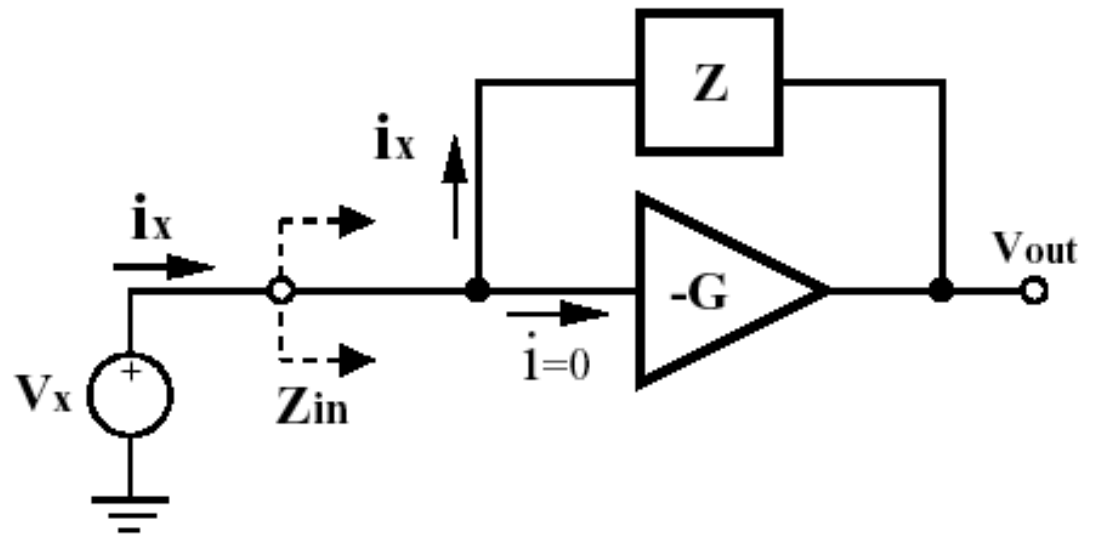
$$\frac{v_x}{i_x} = Z_{in} = \frac{Z}{(1+G)}$$



- Impedance across inverting gain stage  $G$
- Reduced by factor equal to  $(1+G)$

## **Example: Impedance is capacitive**

- **Capacitance multiplied by (1+G)**

$$Z_{in} = \frac{Z}{(1 + G)}$$

$$Z = \frac{1}{sC} \quad \rightarrow \quad Z_{in} = \frac{1}{s \underbrace{(1 + G)C}_{C_{eq}}}$$


- **Equivalent capacitance higher by factor 1+G**
- **Problem for high bandwidth amplifiers**
- **Opportunity for compensation ...**

# Miller Compensation

- **Need effect of large capacitance**
- **Use Miller effect to multiply small on-chip capacitance to higher effective value**
- **Effect of large capacitance without die area cost of large capacitance**


# New schematic

- Add  $C_C$  across 2nd stage

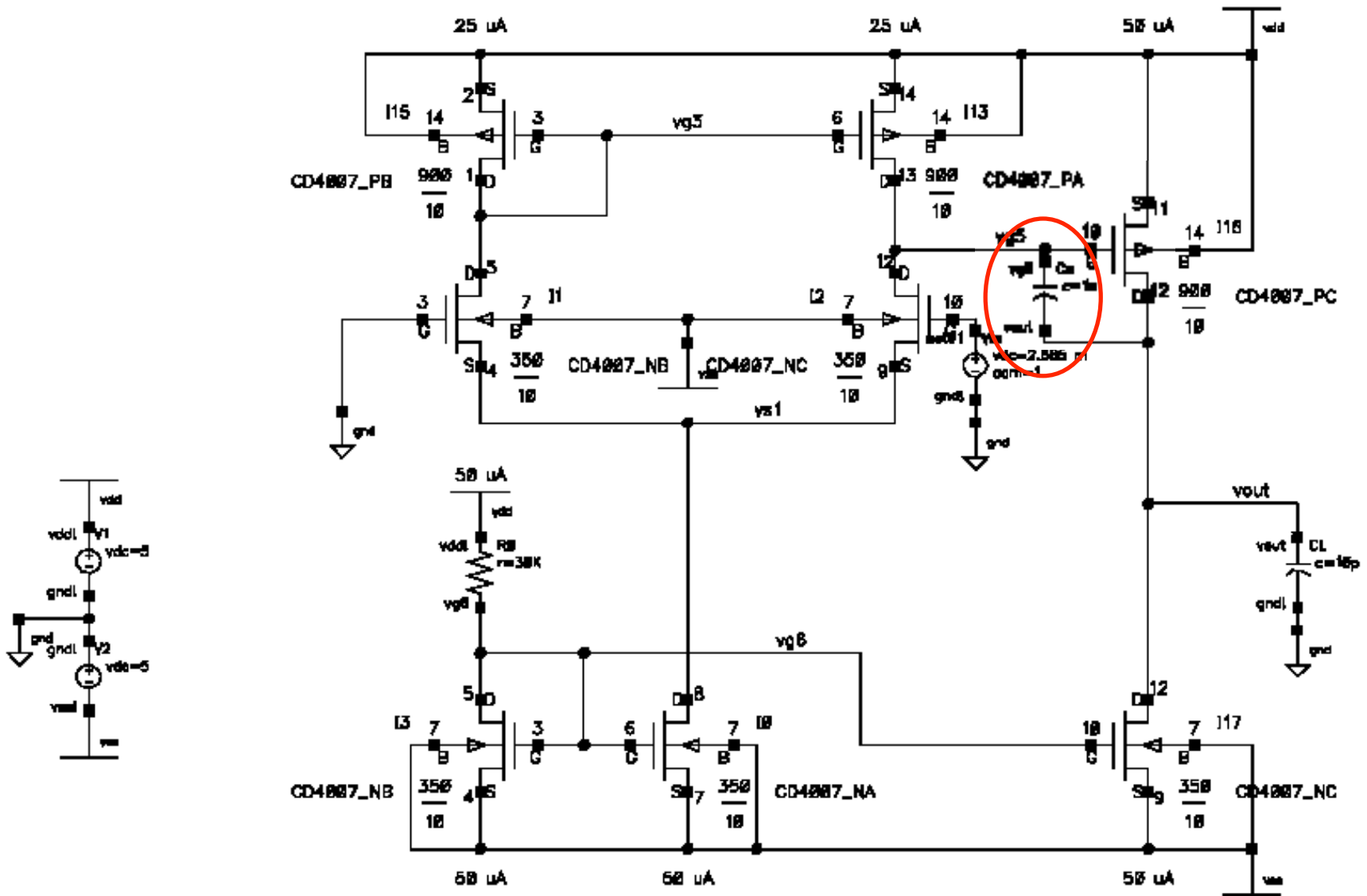



# New loop gain transfer function

AC Response

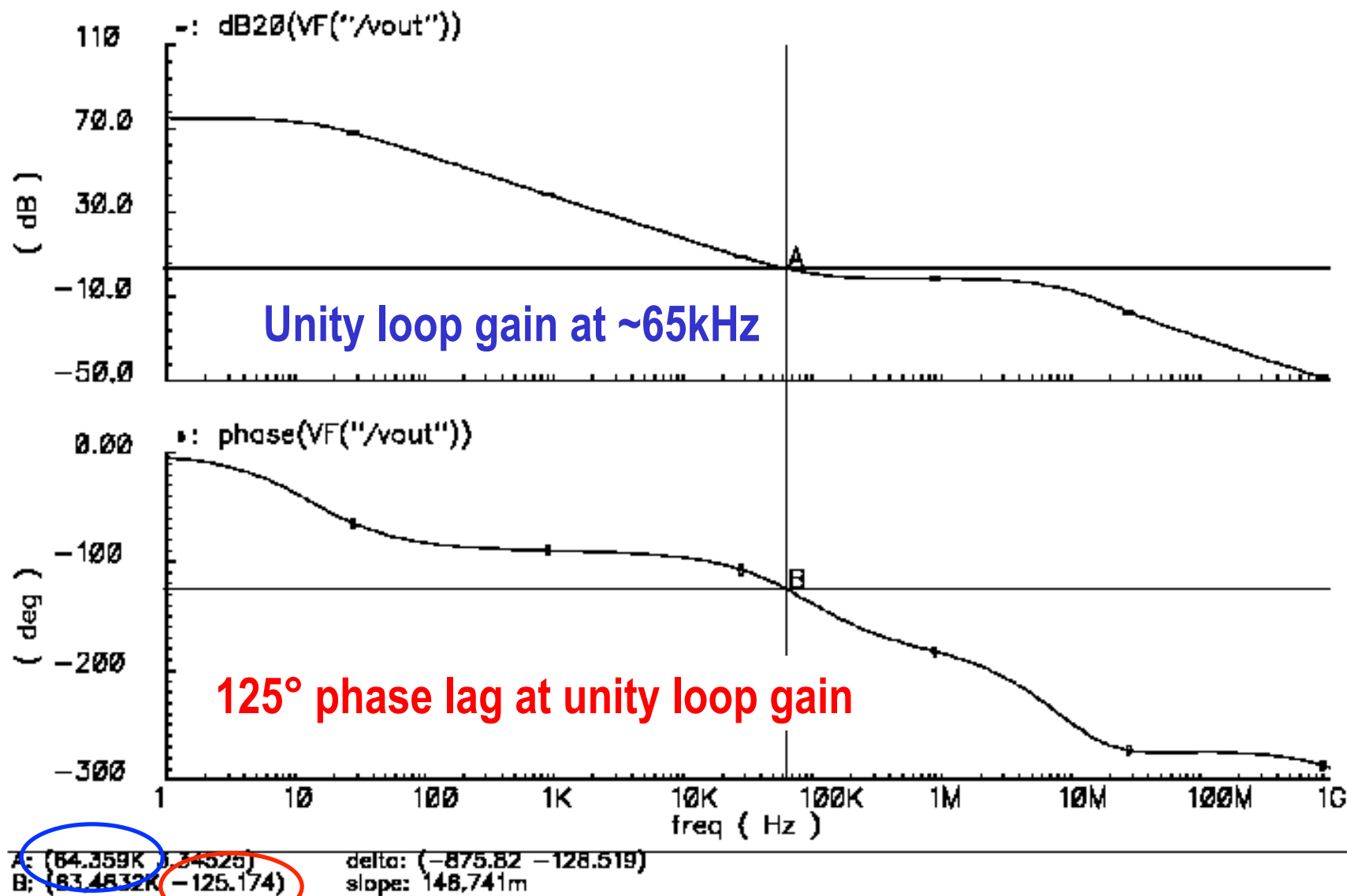



# New step response

- No oscillation!

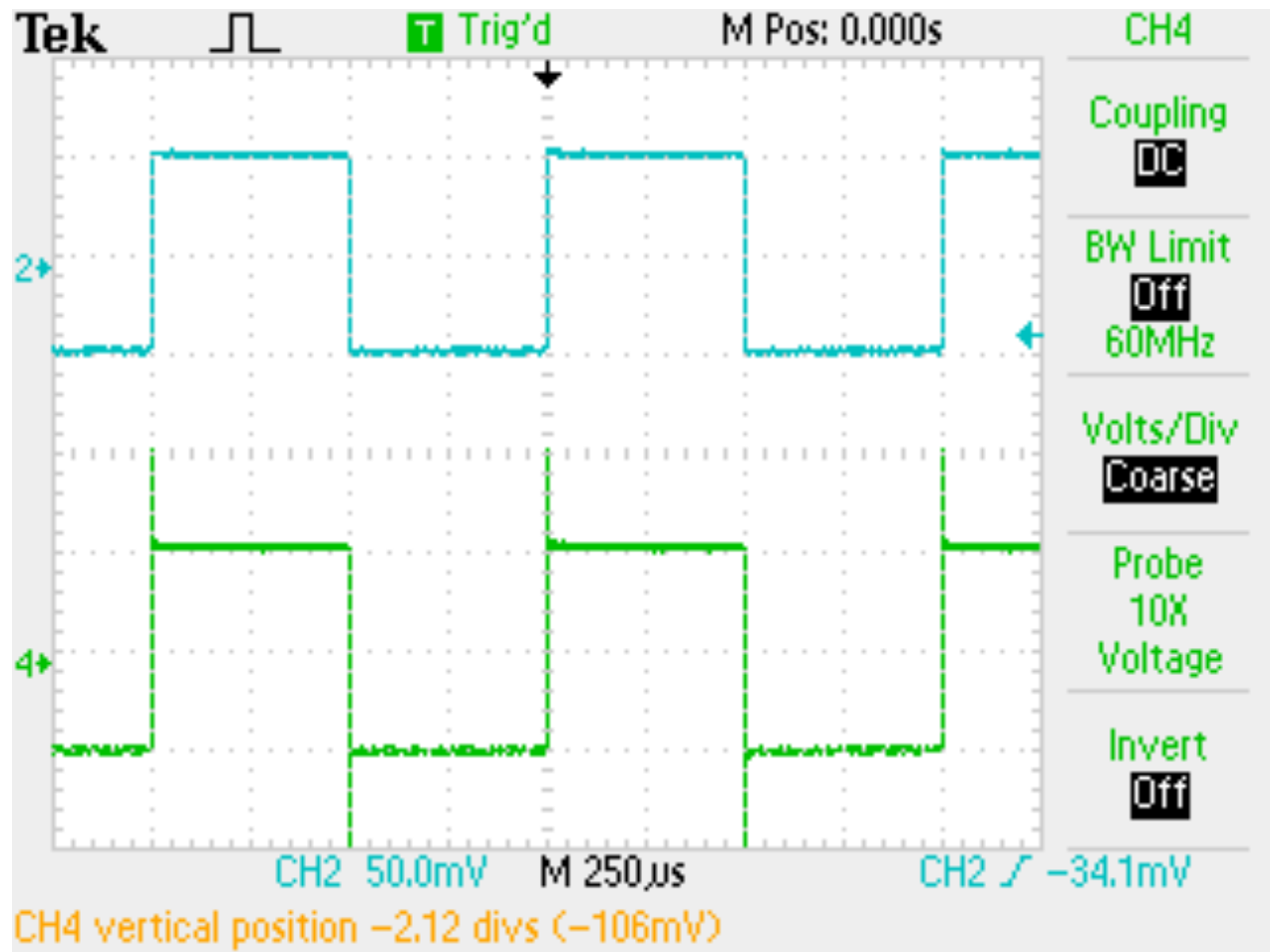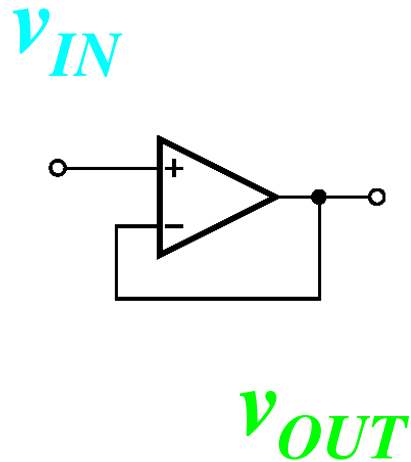

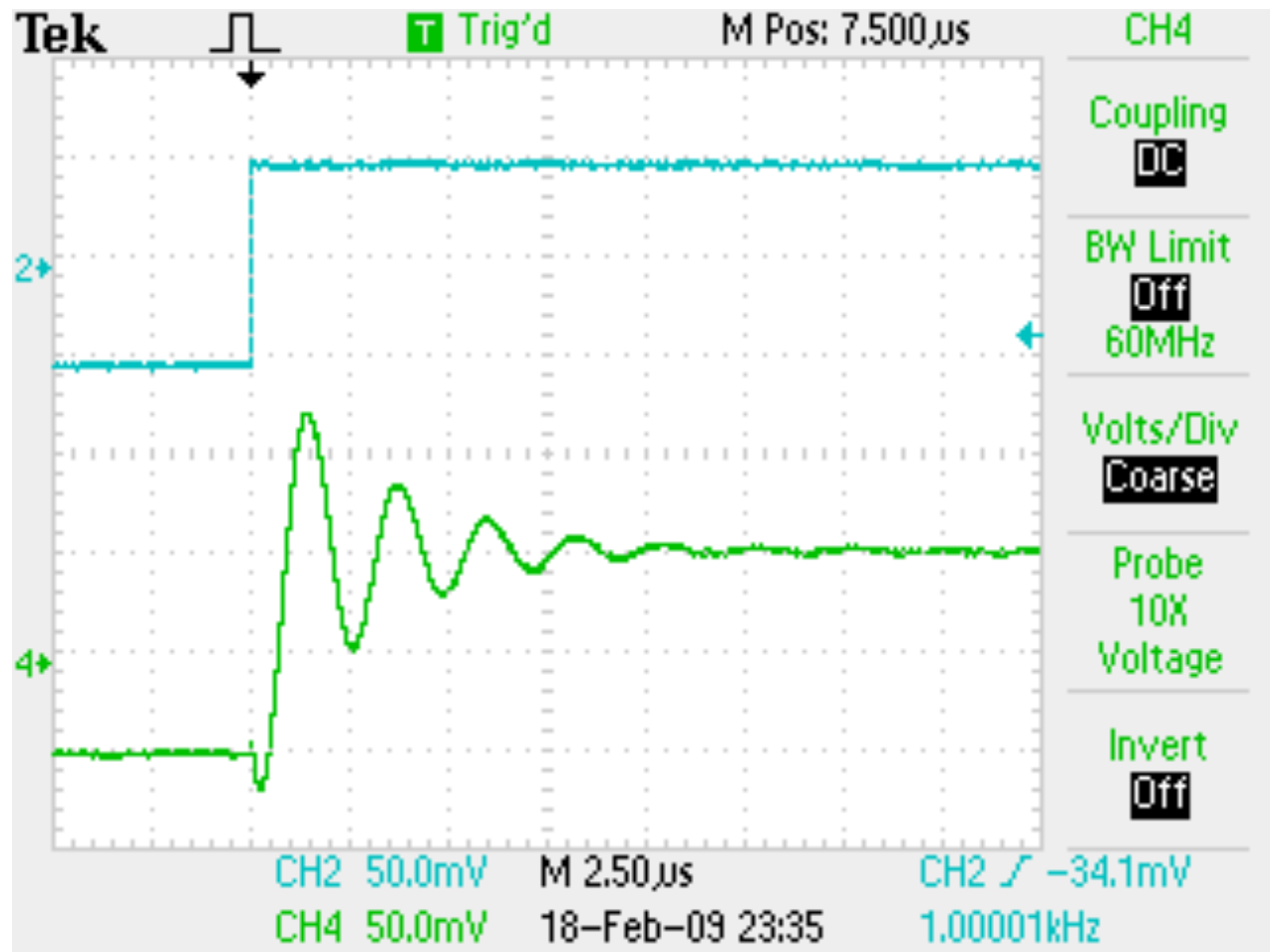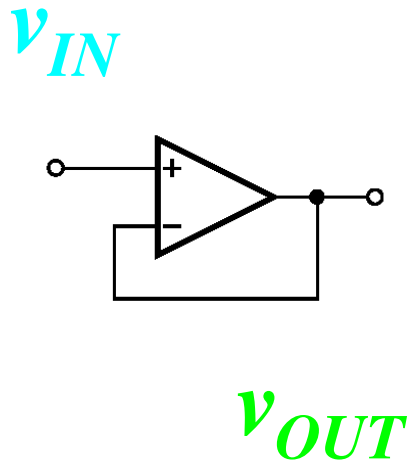
## New step response with $C_C$

- Zoom in on small-signal step response:  
Some overshoot and ringing



# Reason: RHP zero in complete transfer function

AC Response

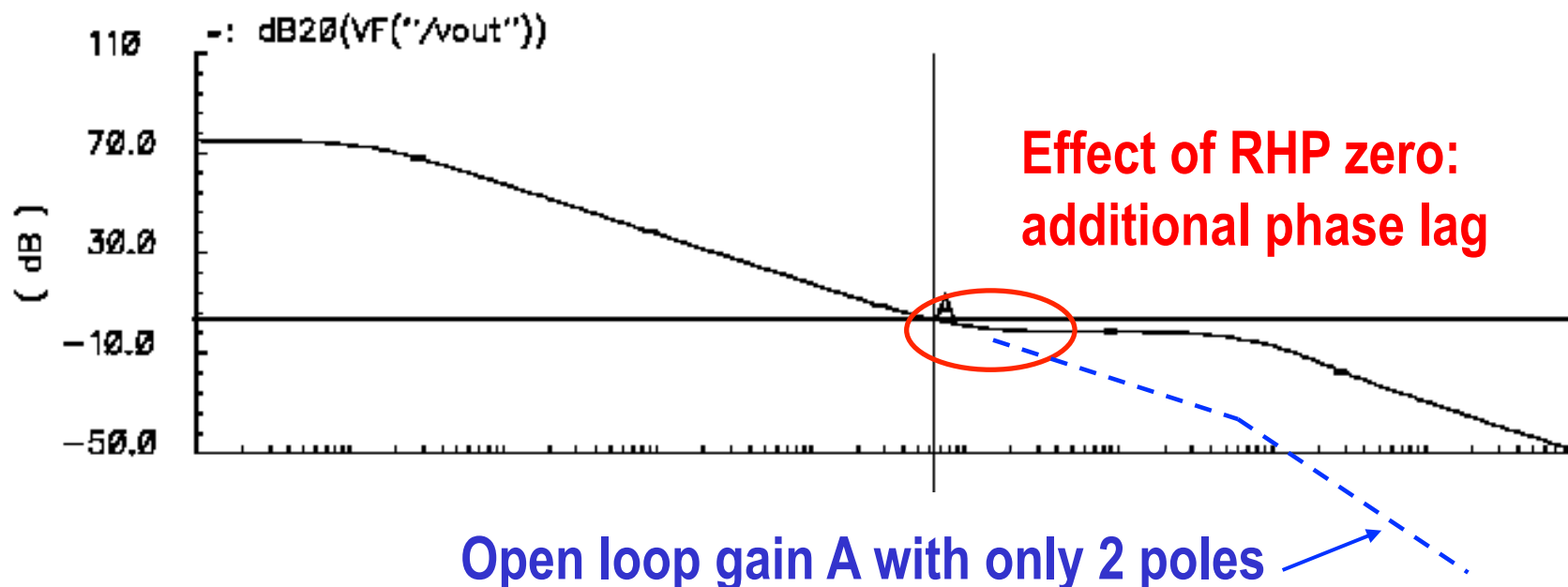


- Complete transfer function looks like:

$$A(j\omega) = \frac{A_0 [1 - j(\omega/\omega_Z)]}{[1 + j(\omega/\omega_{p1})][1 + j(\omega/\omega_{p2})]}$$

- See Razavi 10.5, Johns & Martin 5.2


## "Phase margin"

- How stable is new transfer function?
- Phase margin =  
Phase lag at  $|A\beta| = 1$   
minus  $(-180^\circ)$
- Usually want at least  $60^\circ$  for stable step response

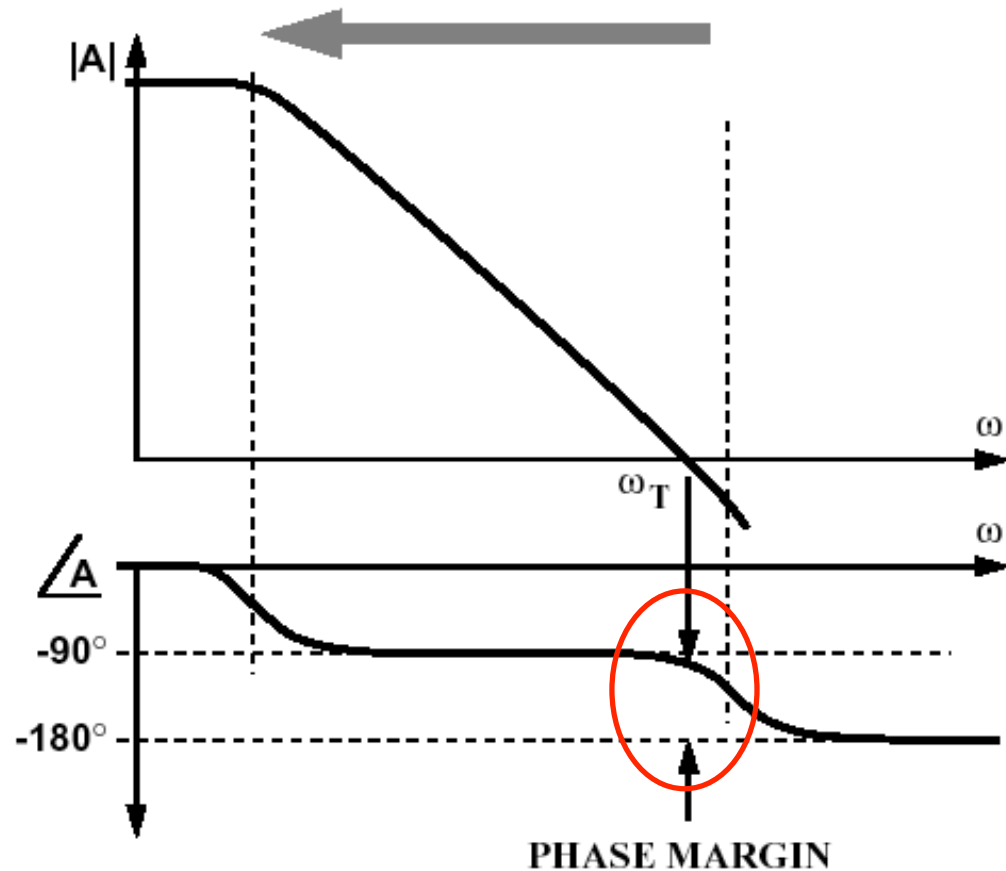


# Phase margin of op-amp with $C_r$

AC Response

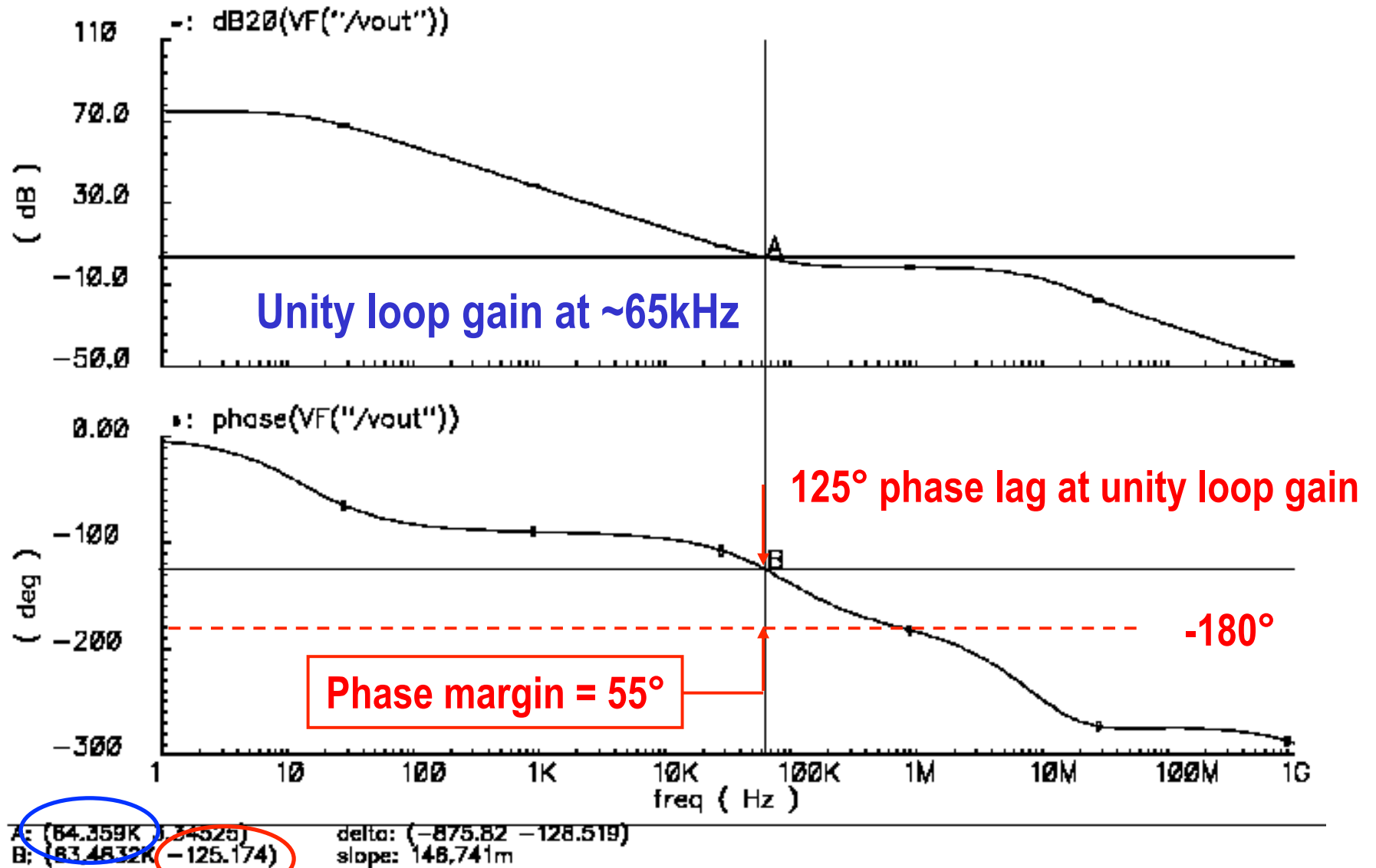


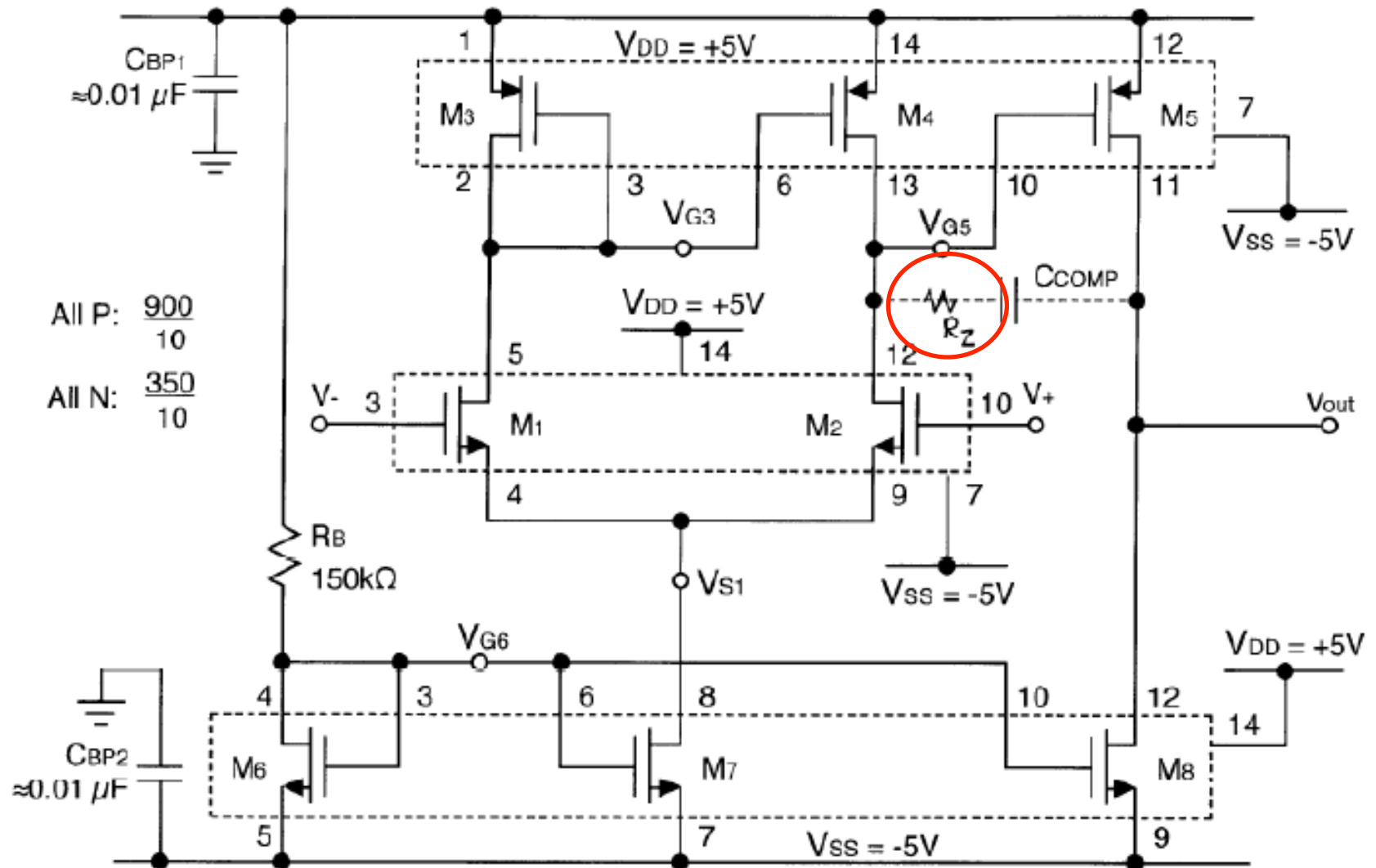
# Solution to RHP zero problem

- Add  $R_Z$  in series with  $C_C$   
Moves RHP zero to much higher frequency



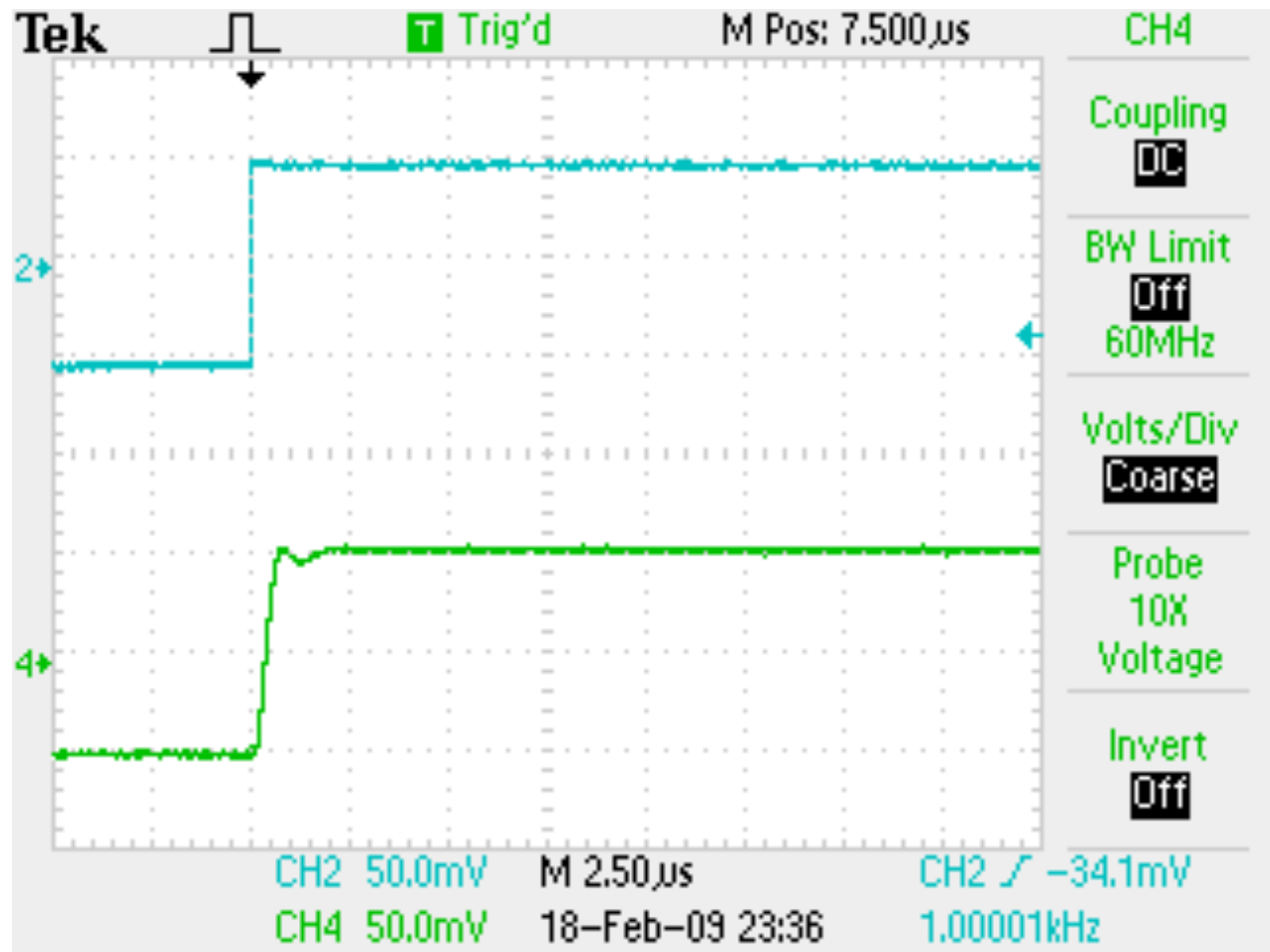
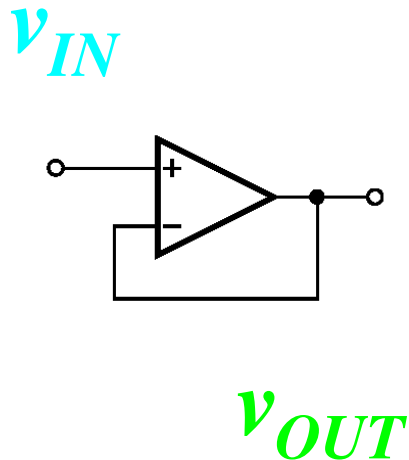
## New step response with $R_Z$ , $C_C$

- Zoom in on small-signal step response:  
No overshoot, ringing: phase margin improved




# Large signal step response

- Slew Rate Limiting!?!

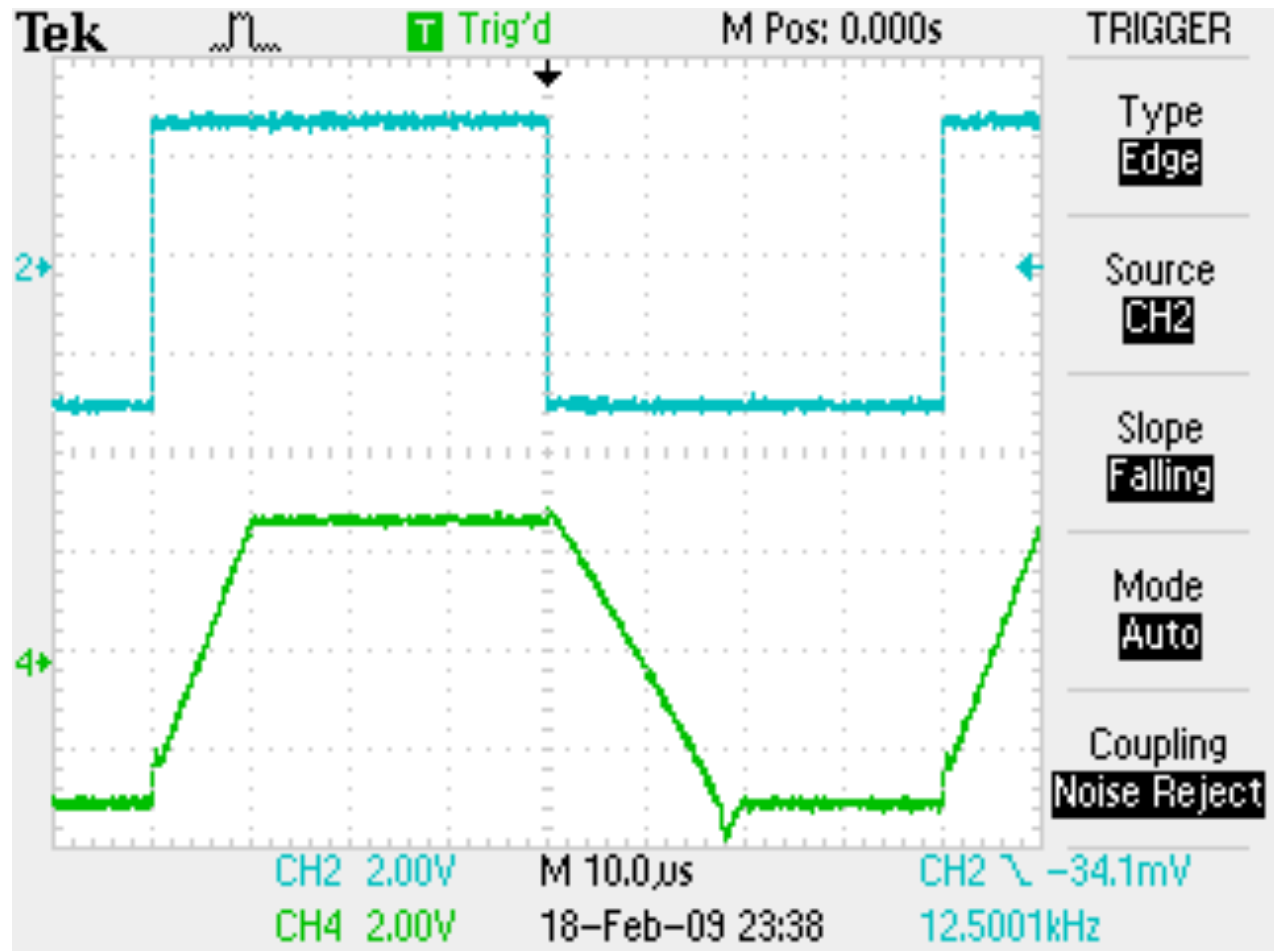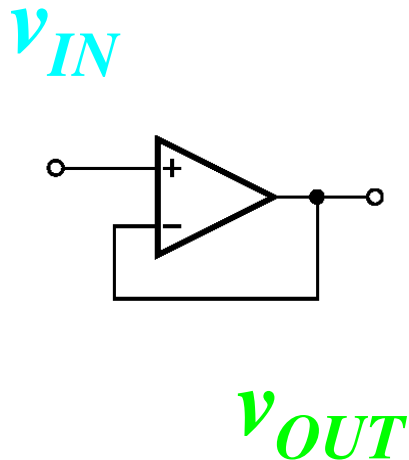


See Solomon op-amp paper for model; rising/falling asymmetry

# Dominant pole op-amp model

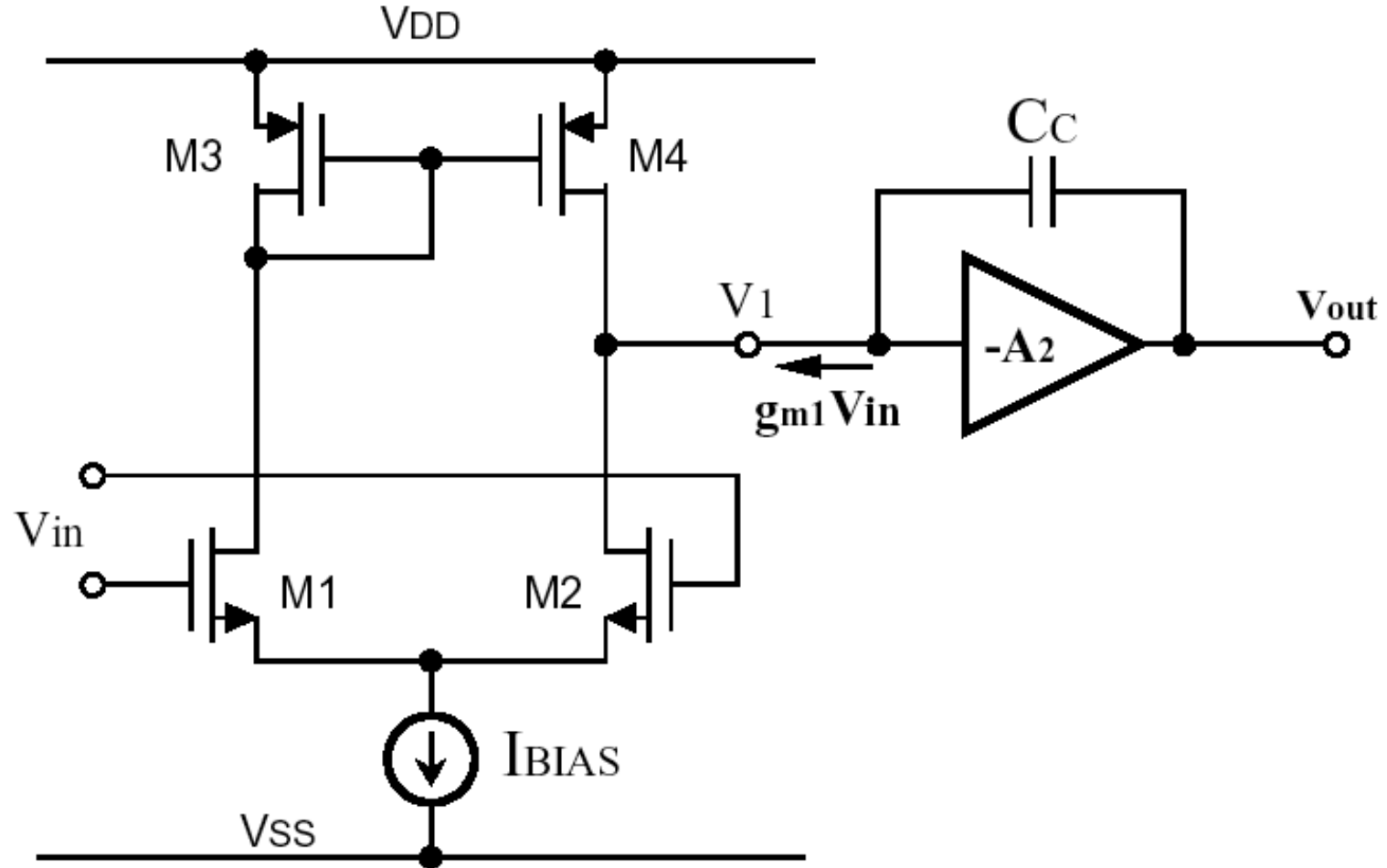

- **Simpler model with dominant pole from  $C_C$**
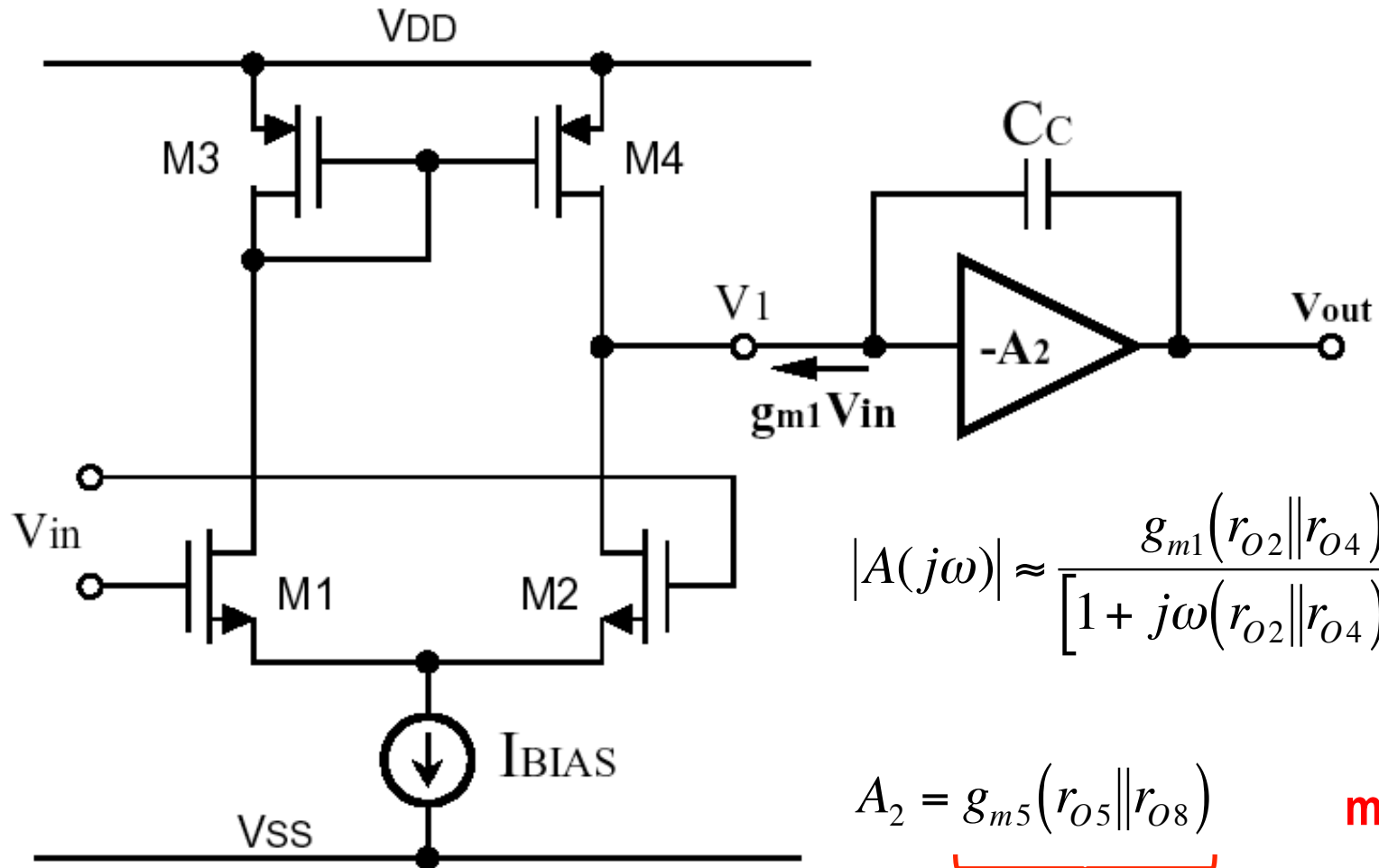
# Approximate dominant pole transfer function



$$|A(j\omega)| \approx \frac{g_{m1}(r_{O2} \parallel r_{O4})A_2}{\left[1 + j\omega(r_{O2} \parallel r_{O4})A_2C_c\right]}$$

$$A_2 = g_{m5}(r_{O5} \parallel r_{O8})$$

2<sup>nd</sup> stage gain

Miller  
multiplied  
 $C_c$


# Unity gain frequency

- Depends only on
  - Input stage transconductance  $g_{m1}$
  - Compensation capacitor  $C_C$

$$|A(j\omega)| \approx \frac{g_{m1}(r_{O2} \parallel r_{O4})A_2}{\omega(r_{O2} \parallel r_{O4})A_2C_C}$$



$$|A(j\omega)| = 1 \quad \text{at} \quad \omega_T$$

$$\omega_T \approx \frac{g_{m1}}{C_C}$$

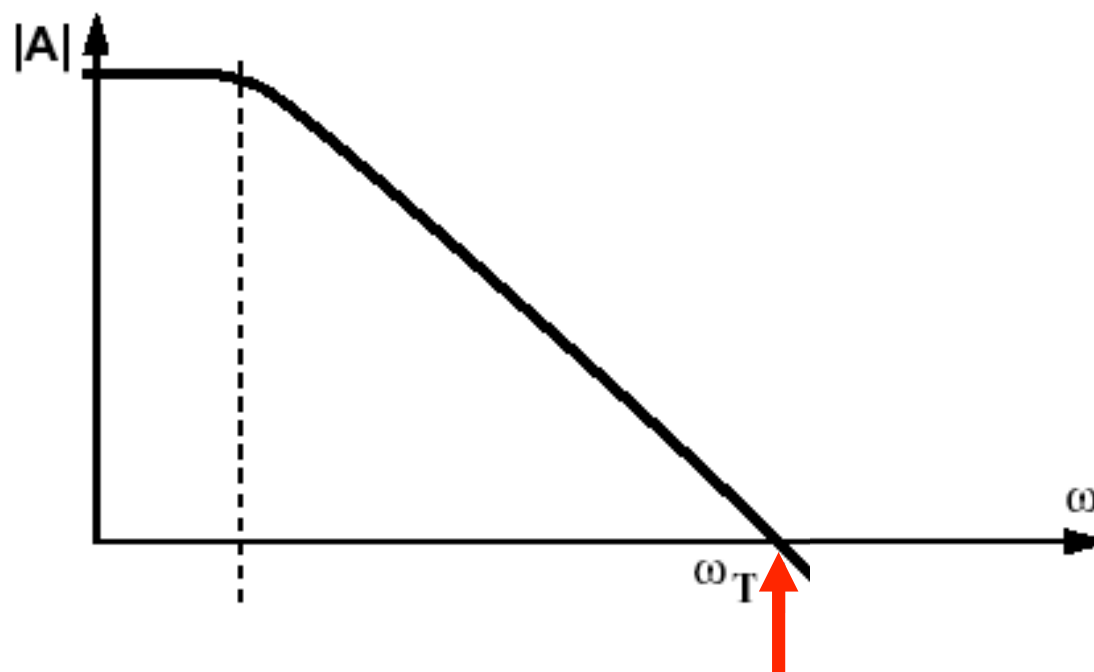

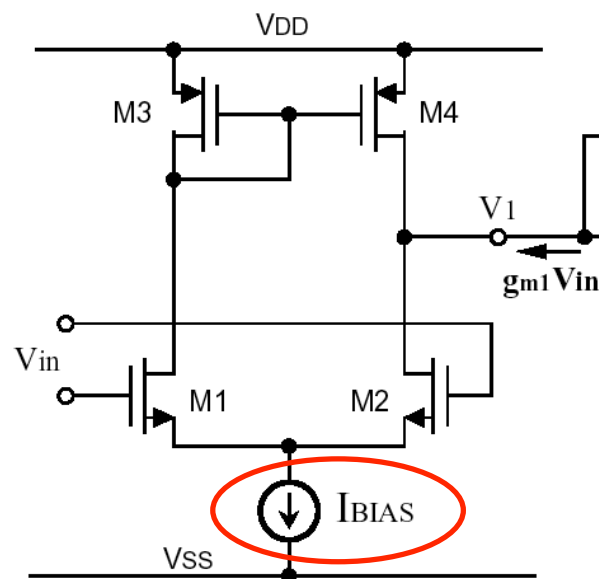
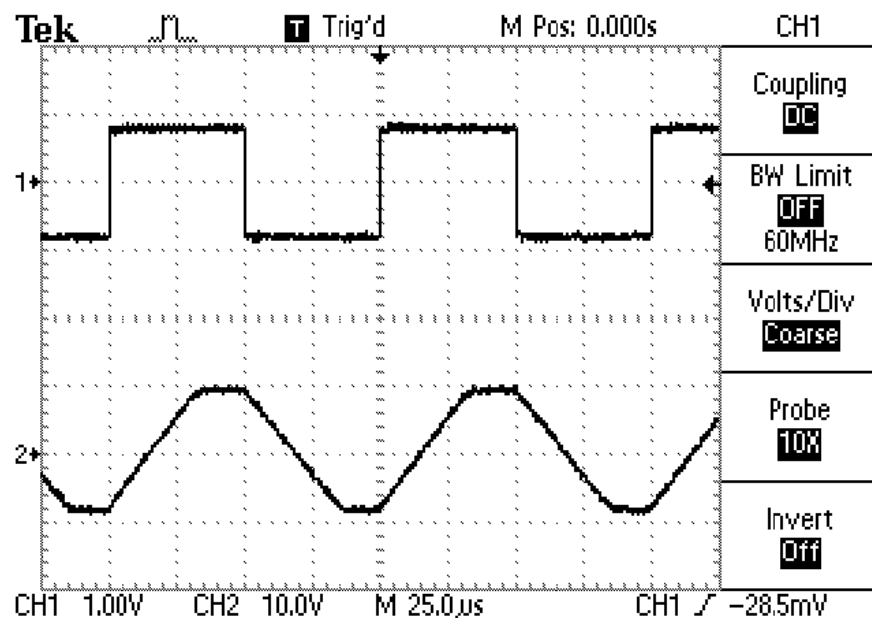
# Slew rate

- $I = C \, dV/dt$
- Only limited current  $I_{BIAS}$  available to charge, discharge  $C_C$


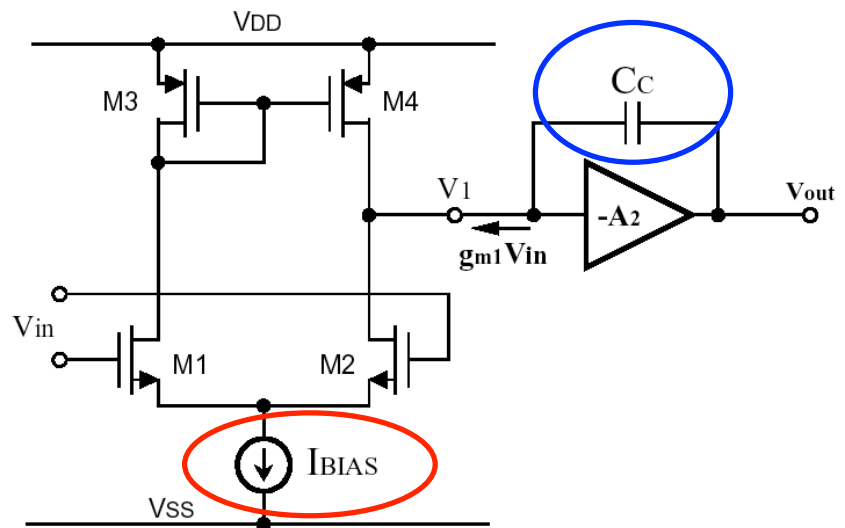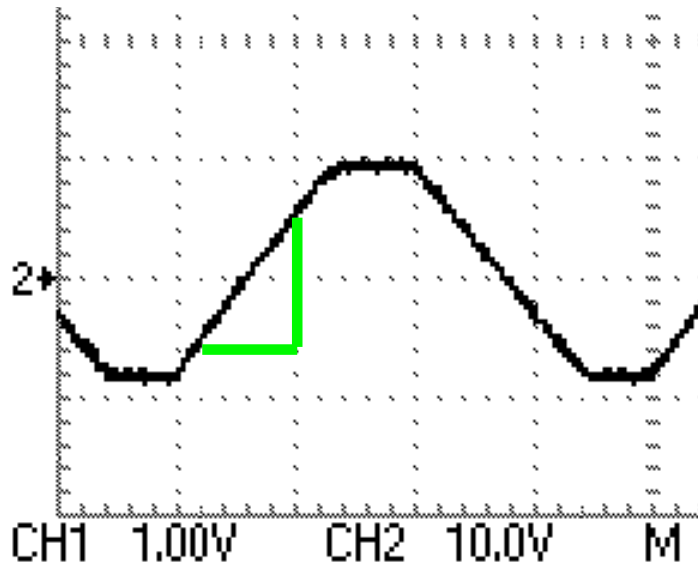
# Slew rate

- $$I = C \frac{dV}{dt} \Rightarrow \frac{dV}{dt} = \frac{I_{BIAS}}{C_C}$$



## **Summary Op-amp:**

- **Stability**
- **Compensation**
- **Miller effect**
- **Phase Margin**
- **Unity gain frequency**
- **Slew Rate Limiting**