


## **Studio 4 Review**

- **Common Source Amplifier, Resistive Load**
- **Small Signal Modeling**

# Review operating regions: N-channel MOSFET


| GATE              | DRAIN                      | REGION     | FIRST ORDER BEHAVIOR                                                                                                                                              | NOT EXACTLY:                                                                                                                                           |
|-------------------|----------------------------|------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------|
| $V_{GS} > V_{TH}$ | $V_{DS} > V_{GS} - V_{TH}$ | SATURATION | DRAIN "LOOKS LIKE" CURRENT SOURCE;<br>$I_D$ DEPENDS ONLY ON $V_{GS} - V_{TH}$<br>$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$                   | CHANNEL LENGTH MODULATION<br>$I_D$ DEPENDS SOMEWHAT ON $V_{DS}$<br>$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 [1 + \lambda V_{DS}]$ |
|                   | $V_{DS} < V_{GS} - V_{TH}$ | TRIODE     | D-S CHANNEL "LOOKS" RESISTIVE<br>$I_D = V_{DS} / R_{on}$ $R_{on}$ DEPENDS ON $V_{GS} - V_{TH}$<br>$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$ | NONLINEAR AS $V_{DS}$ INCREASES<br>$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]$                       |
| $V_{GS} < V_{TH}$ | $ V_{DS}  < V_{bkd}$       | CUTOFF     | SWITCH "OFF" $I_D = 0$                                                                                                                                            | $I_D \approx$ pA to nA SUBTHRESHOLD CURRENT<br>BREAKDOWN IF $ V_{DS} $ EXCEEDS $V_{bkd}$                                                               |
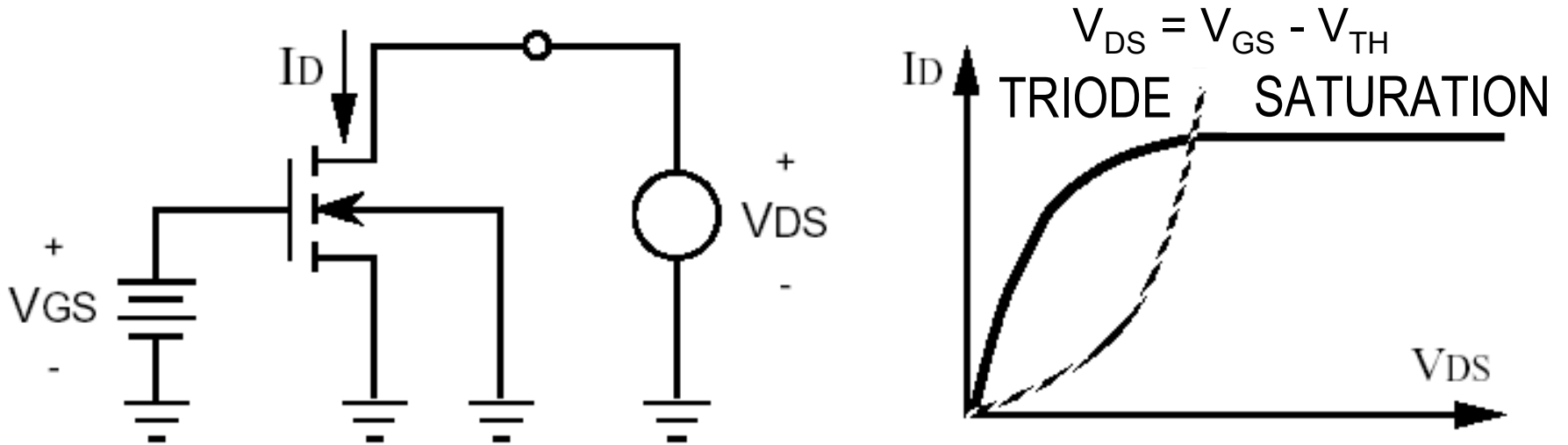
## Review MOSFET: Vary $V_{DS}$ ( $V_{GS}$ fixed)



- Need  $V_{GS} > V_{TH}$  (avoid cutoff region)

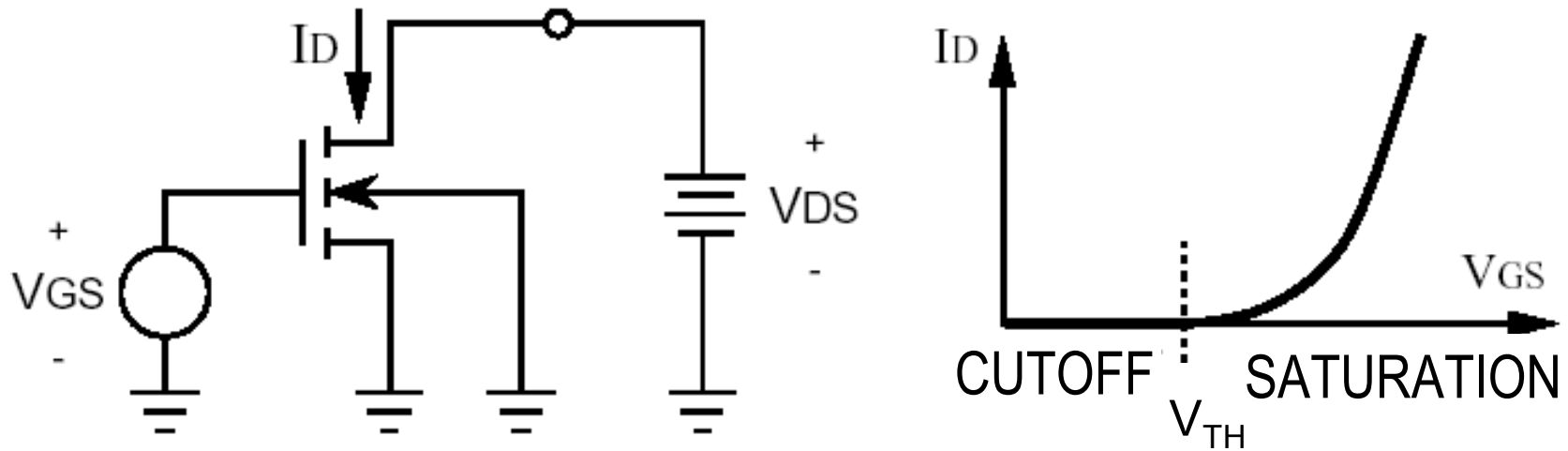
## Review MOSFET: Vary $V_{GS}$ ( $V_{DS}$ fixed)



- Need  $V_{DS} > V_{GS} - V_{TH}$  (avoid triode region)
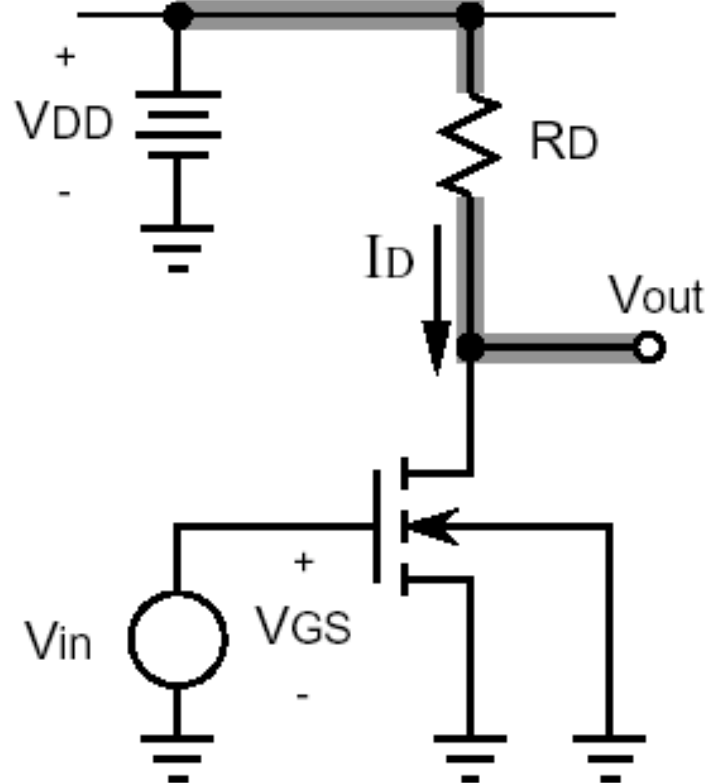
# Common Source Amplifier

- $V_{IN}$  goes up  $\Rightarrow$   
Increase  $V_{GS}$   $\Rightarrow$   
Increase  $I_D$
- KVL path for  $V_{out}$   
 $V_{out} = V_{DD} - I_D R_D$
- MOSFET in saturation:
- $I_D$  increases  $\Rightarrow$   
 $I_D R_D$  drop increases  $\Rightarrow$   
 $V_{OUT}$  goes down




$V_{IN}$  goes up  $\Rightarrow V_{OUT}$  goes down

# Common Source Amplifier

- **INVERTING GAIN**


**GATE  $\Rightarrow$  DRAIN**

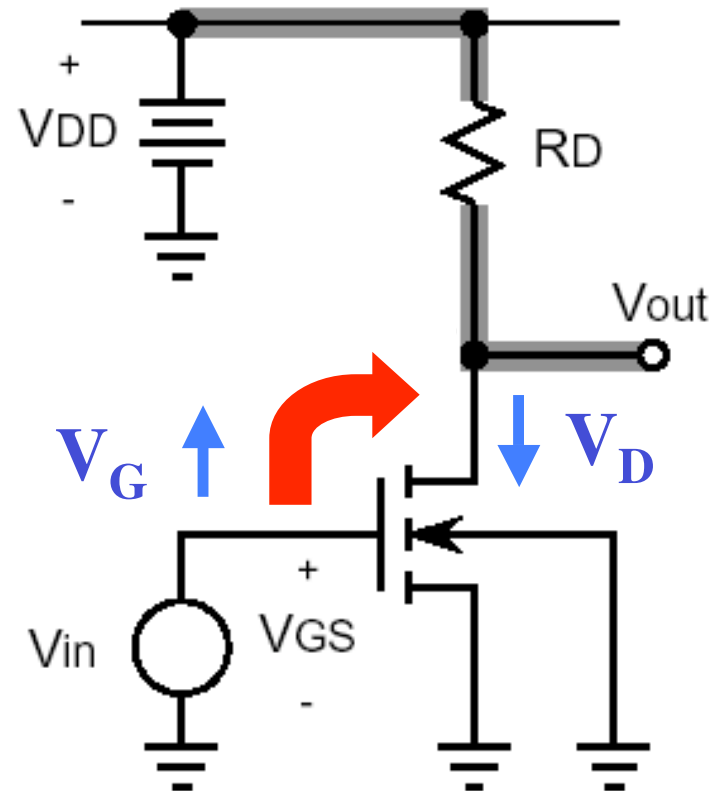

**$V_{IN}$  goes up  $\Rightarrow V_{OUT}$  goes down**

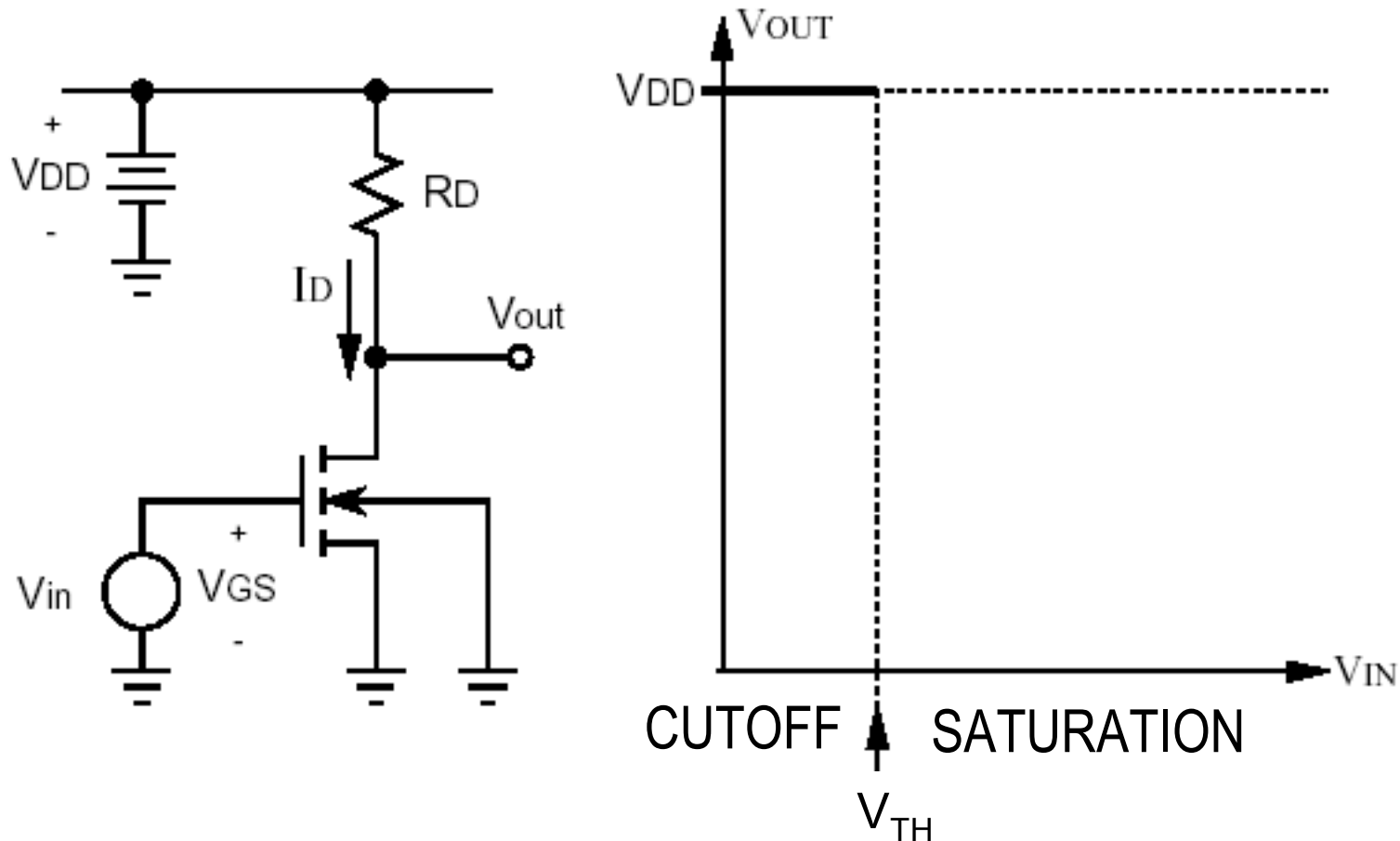
## Build up input-output characteristic

- $V_{IN} < V_{TH} \Rightarrow V_{GS} < V_{TH} \Rightarrow$   
**Cutoff:**  $I_D = 0$   $V_{OUT} = V_{DD}$



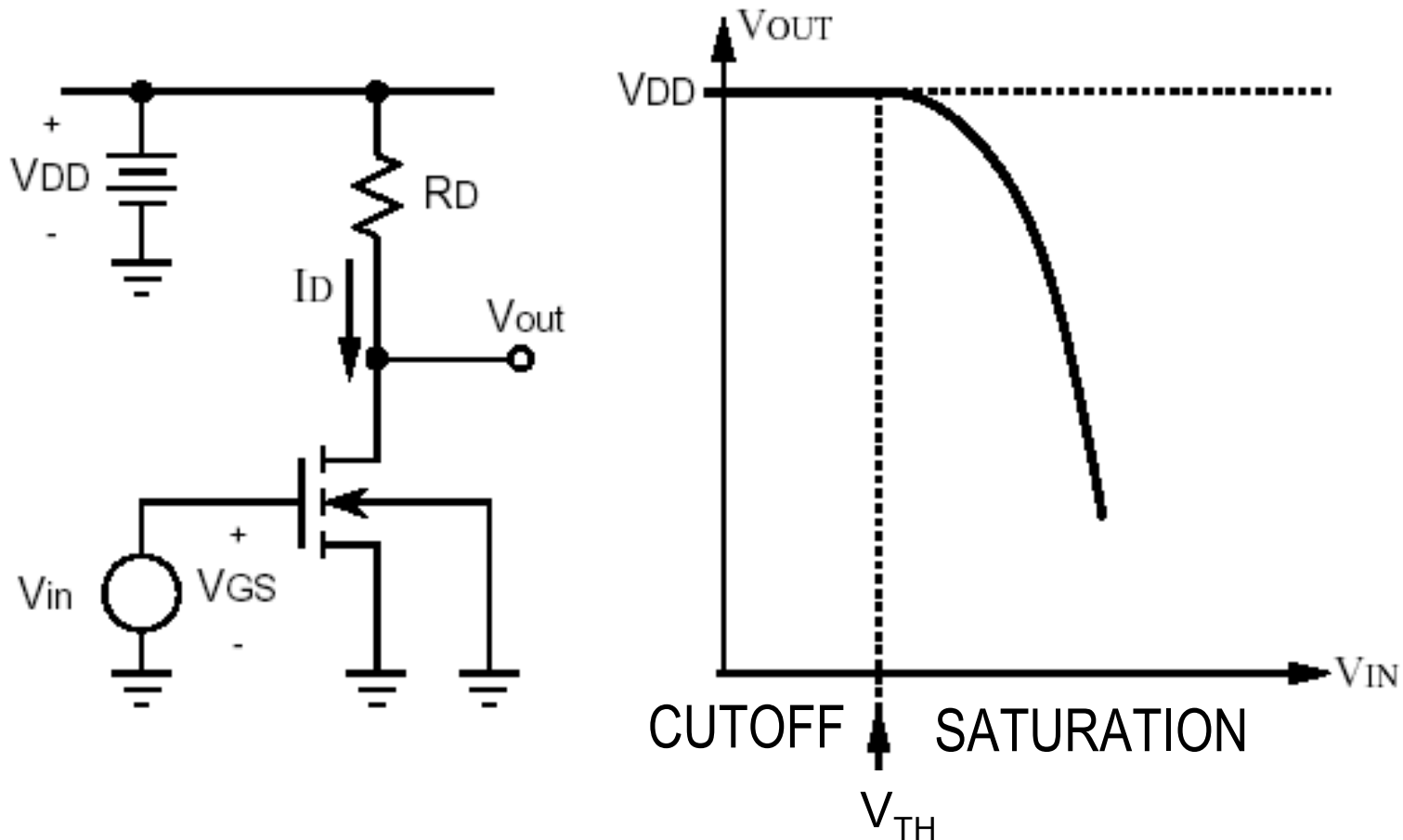
## Build up input-output characteristic

- $V_{IN} > V_{TH}$   $V_{GS} > V_{TH}$   $V_{OUT} = V_{DD} - \underbrace{\frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2}_{I_D} R_D$
- **Saturation:**  $I_D$  from square law


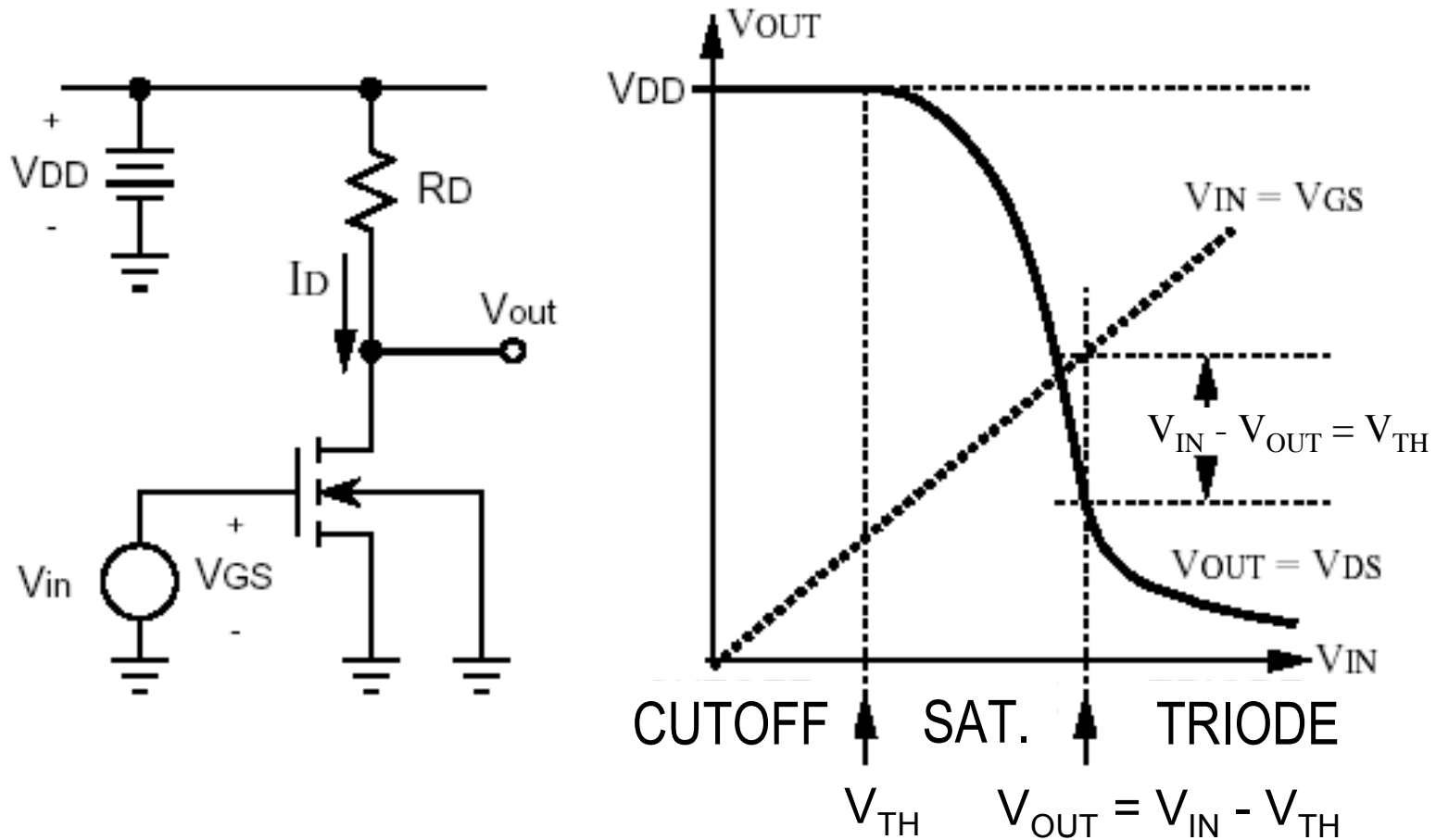
# Condition for saturation-triode boundary

- $V_{DS} = V_{GS} - V_{TH} \Rightarrow$
- On boundary, both triode, saturation equations apply



## Condition for saturation-triode boundary


- **Expression for  $V_{out}$  on boundary (use square law)**

$$\underbrace{V_{DD} - \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2 R_D}_{V_{OUT}} = V_{in} - V_{TH}$$


- **Ugly quadratic: solve numerically or let SPICE do it**

# Triode

- Ugly math: let SPICE do the work

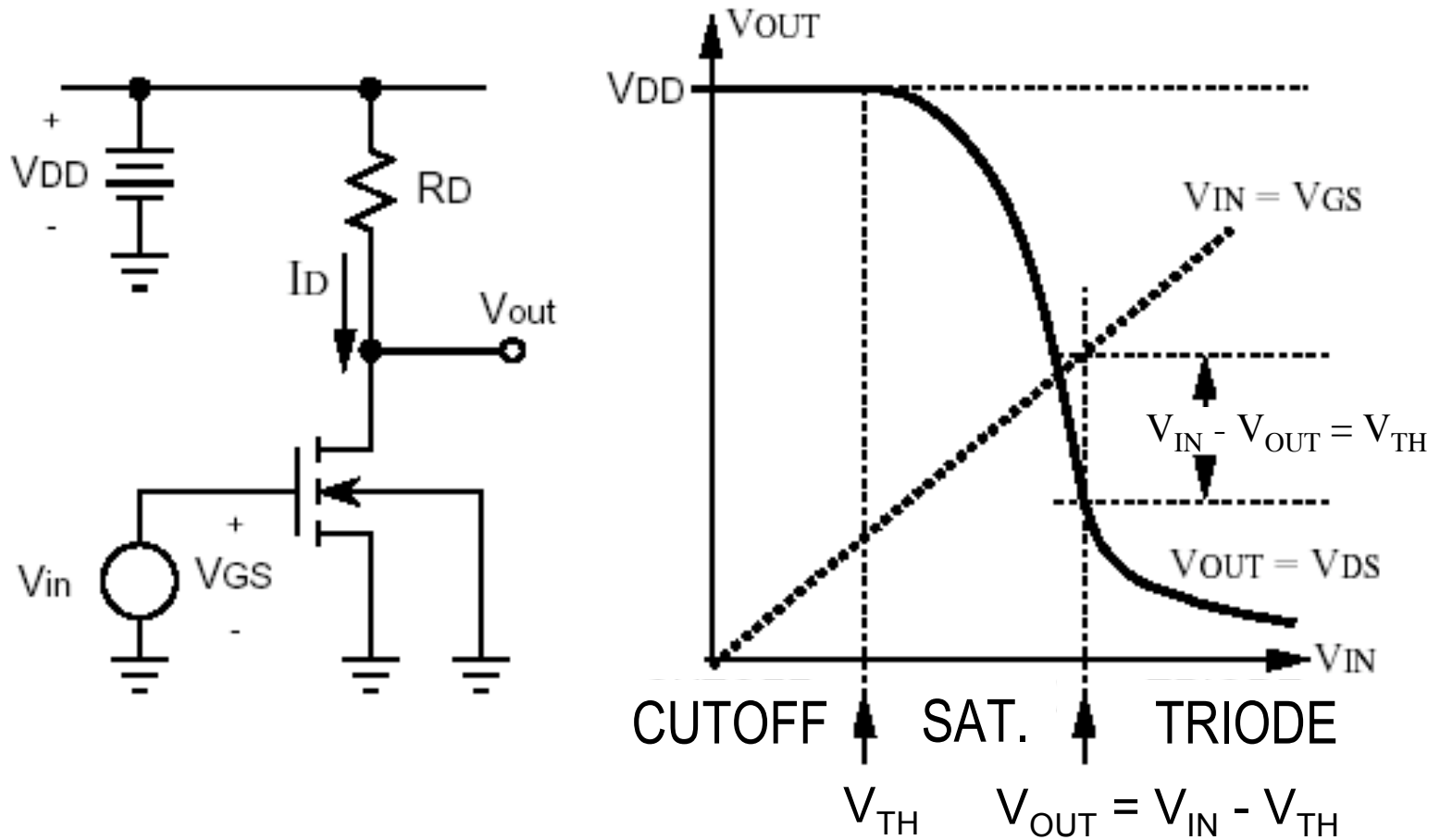


# Input-output characteristic

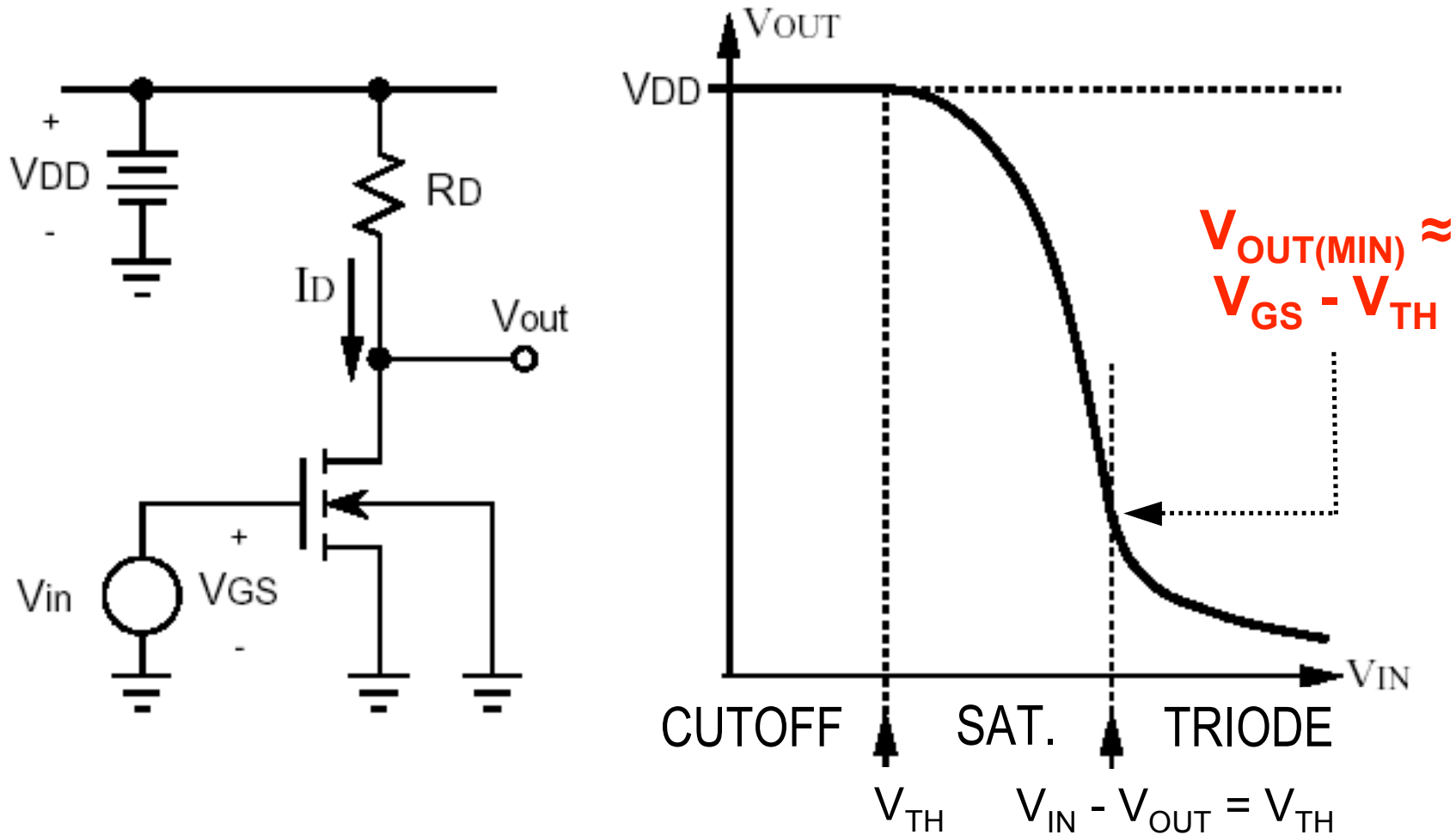

- Minimum output  $\approx V_{GS} - V_{TH}$  (gate overdrive!)
- Maximize output swing  $\Leftrightarrow$  minimize overdrive



# Input-output characteristic

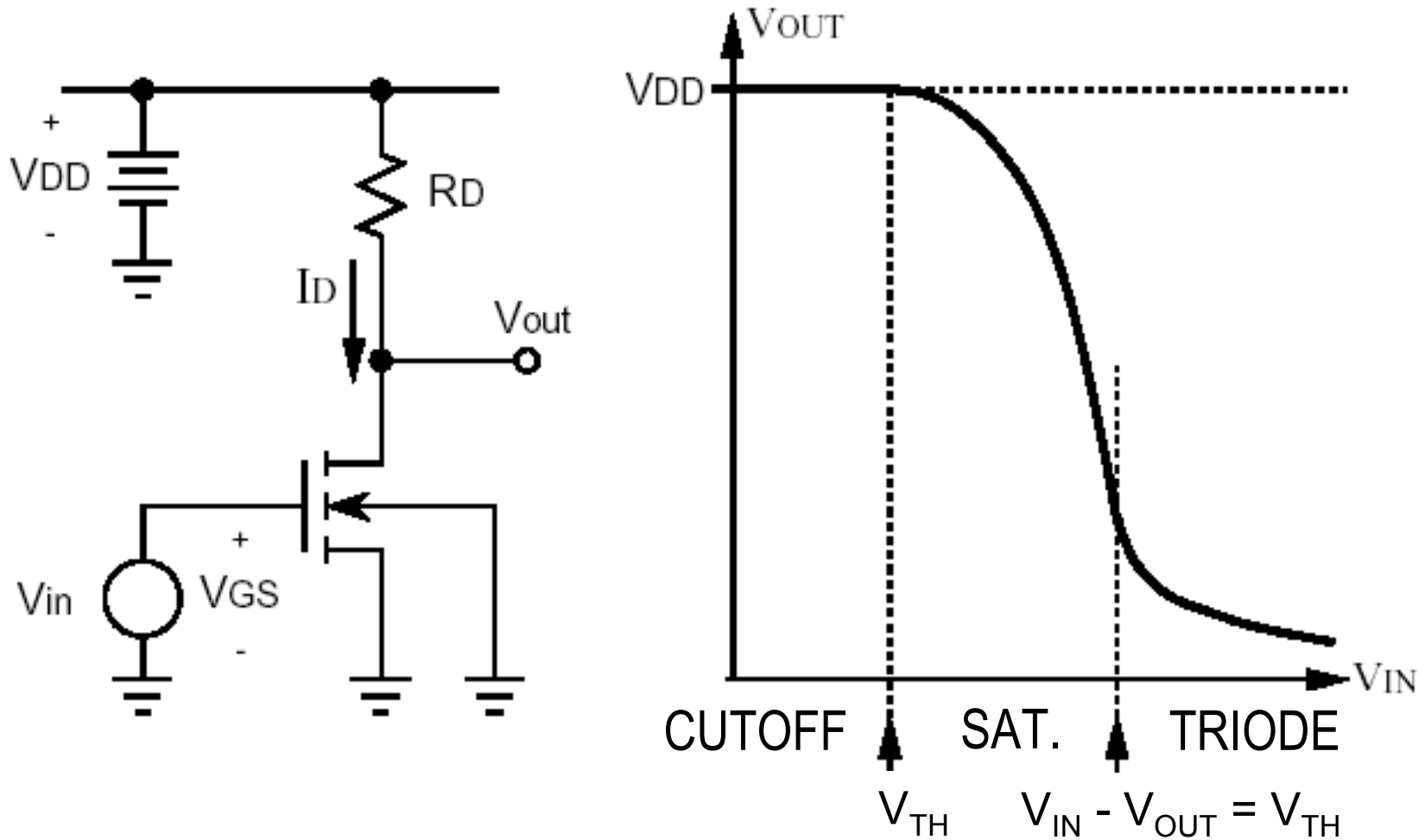


- Compare to desired amplifier characteristic ...
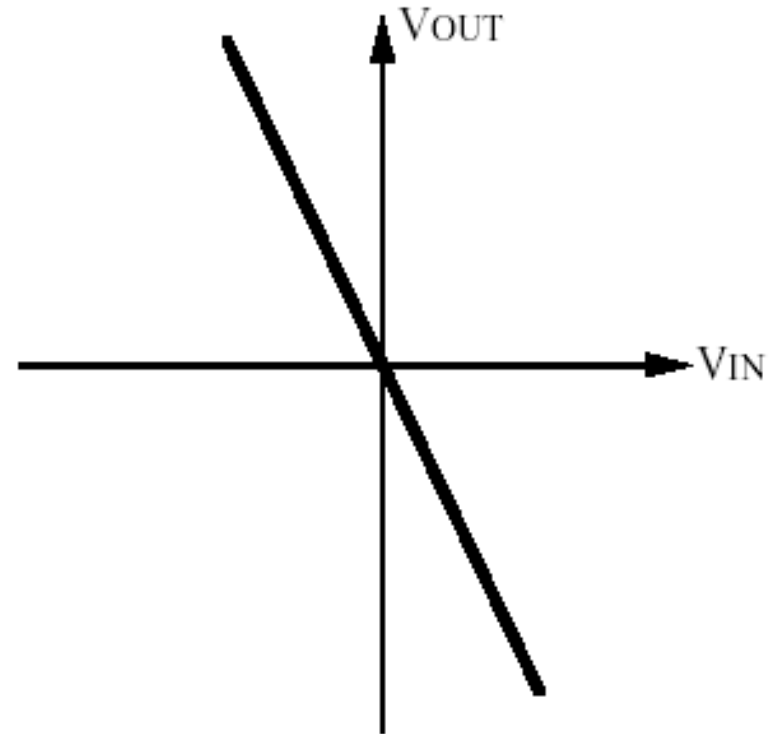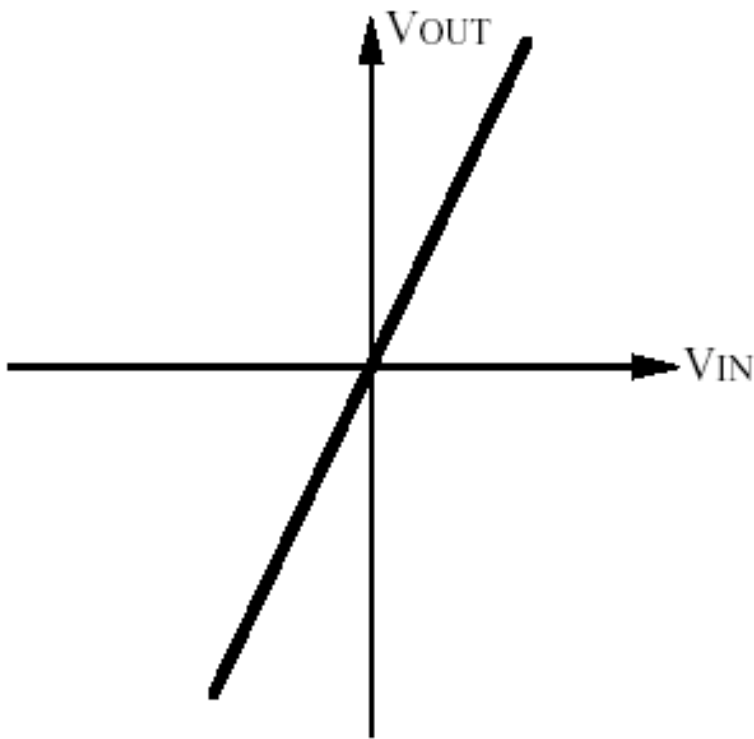
## Desired linear amplifier characteristic

$$V_{\text{out}} = a_v V_{\text{in}} \quad (\text{negative slope OK - but should be linear!})$$


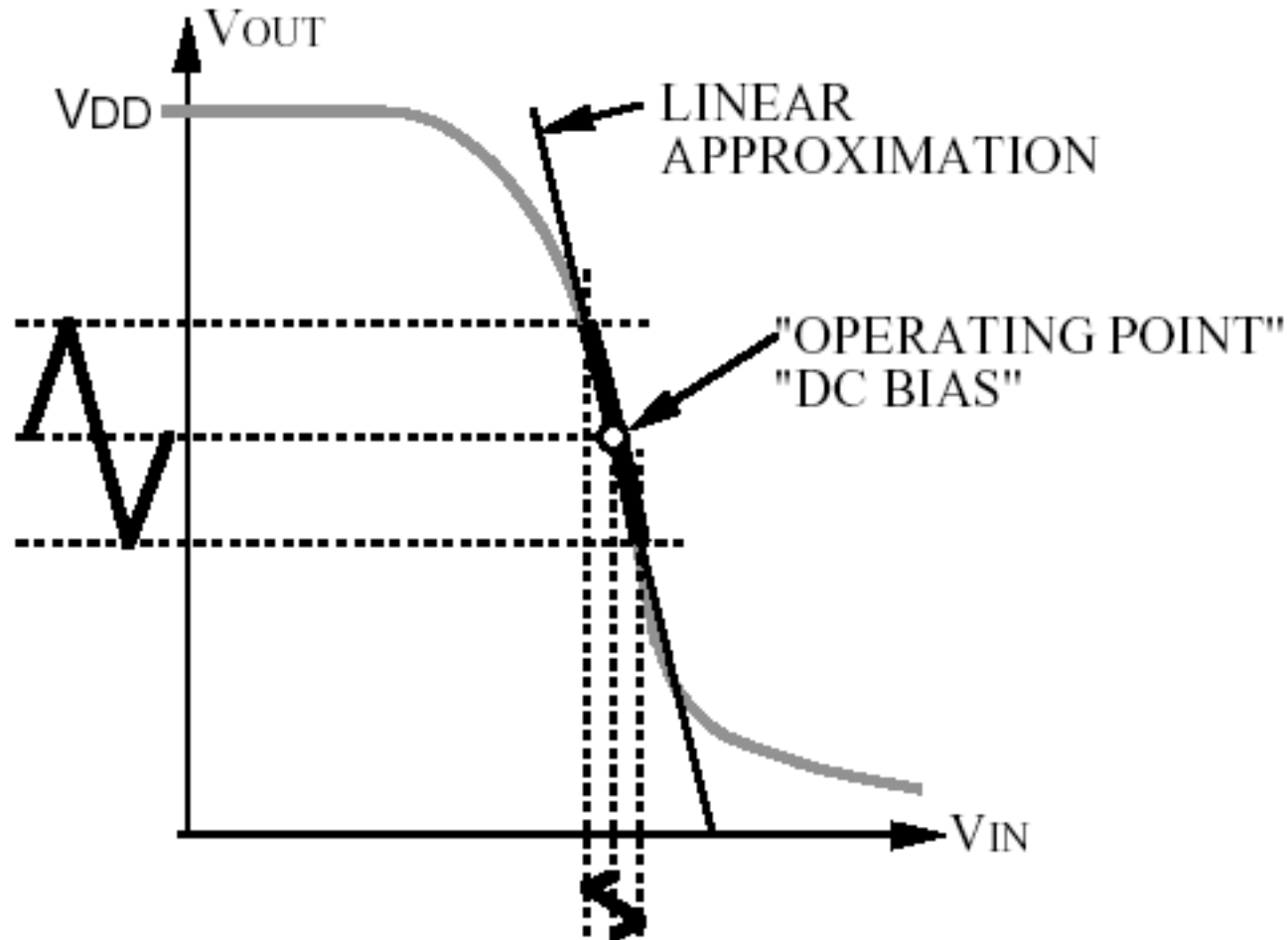
# Linear (sort of) part of input-output characteristic



- **Key: Small signal  $\Rightarrow$  Slope = Derivative**

## Slope: derivative

- **Find slope (small signal gain)**

$$\frac{dV_{OUT}}{dV_{in}} = \frac{d}{dV_{in}} \left[ V_{DD} - \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{in} - V_{TH})^2 R_D \right]$$

$$\frac{dV_{OUT}}{dV_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) R_D$$

- **Constant terms (such as supply  $V_{DD}$ ) drop out**
- **Why carry constant terms through equations if they're just going to drop out when we take derivative? ...**

# Small Signal Analysis

- **What it is**
  - **A method of analysis that allows us to get approximate analytic expressions (equations) for nonlinear circuits which can't be solved easily.**
  - **"Take derivative first"**

## **Small Signal Analysis: Why you do it**

- **Linear signal analysis : powerful tool**
- **Use it to analyze systems that aren't linear.**
- **Anything (even a nonlinear circuit element) looks linear if you look at small enough changes from an operating point.**

## **Small Signal Analysis: Procedure:**

- 1. First, find the DC (large signal) operating point for each element in the nonlinear circuit.**
- 2. Redraw the circuit: replace each circuit element with its small-signal model**
- 3. Solve the small-signal circuit model using all the linear analysis tools you know and love**
- 4. Total behavior is sum of  
DC (large signal) operating point  
+ small signal component "riding on" DC bias  
from large signal operating point solution**

## **Small Signal Analysis: Procedure:**

**1. First, find the DC (large signal) operating point for each element in the nonlinear circuit.**

**– Possible methods:**

- Solve nonlinear equations (e.g. quadratic for saturation region MOSFET square-law model)**
- Iteratively solve nonlinear equations (e.g. SPICE)**
- Approximate analysis (e.g. for diode, assume  $V_D = 0.7V$  when forward biased)**
- Graphical technique**

**– Small signal solution will "ride on" bias levels provided by large signal operating point solution**

## **Small Signal Analysis: Procedure:**

### **2. Redraw the circuit: replace each circuit element with its small-signal model**

- Linear elements (e.g. pure R, L, C) stay the same**
- Constant V/I Sources: Gone!**  
**("take derivative first"):**
  - DC voltage sources: replace with short circuit**
  - DC current sources: replace with open circuit**

## **Small Signal Analysis: Procedure:**

- **Nonlinear element: Replace with small-signal model**
  - **For each type of device, small-signal model is obtained from derivative of appropriate terminal characteristic to find linear approximation for behavior around operating point.**
  - **Usually just do this once for each type of device; small signal model parameters are a function of large signal operating point (e.g. small signal MOSFET model derived once; then for each application of model use operating point information to calculate small signal parameters).**

## **Small Signal Analysis: Procedure:**

- 3. Solve the small-signal circuit model using all the linear analysis tools you know and love:**
  - Good Old Ohm's Law**
  - Can use Thevenin's theorem to simplify large circuits**
  - Can use superposition to calculate response to different inputs**
  - Can use transfer functions to express frequency-dependent behavior**
  - Can always use KVL, KCL, nodal analysis (these don't require linearity)**

## **Small Signal Analysis: Procedure:**

- 4. Total behavior is sum of DC (large signal) operating point + small signal component "riding on" DC bias from large signal operating point solution**

## **Small Signal Analysis: Limitations**




- **If actual signal isn't "small", then "solution" won't be valid!**
- **How small is "small"? Depends on accuracy required. Need to look at derivation of model for individual devices used.**
- **ALWAYS check output waveform max/min to be sure assumptions for linear model are valid (for example, output not clipped at supply rails)**

# Simplest MOSFET Small Signal Model

- **Saturation Region: Transconductance  $g_m$**

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$
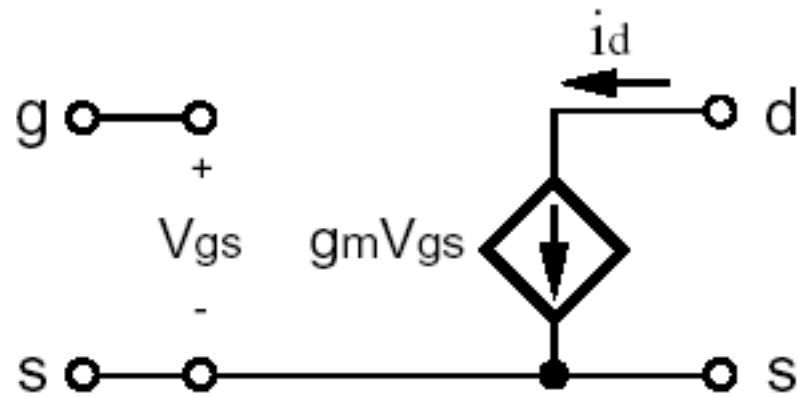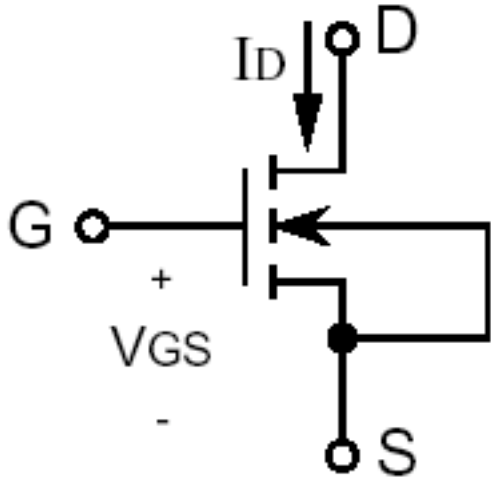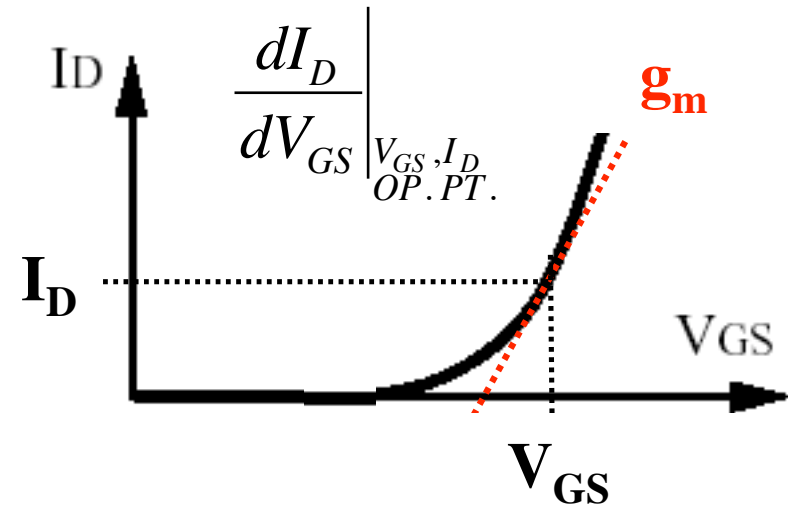
$$\frac{dI_D}{dV_{GS}} = g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$



# Summary

- **MOSFET operating regions**
- **Common source amplifier**
- **Large signal input-output characteristic**
- **Small-signal concept**

## **Lab exercise**

- **Plot Large Signal input-output characteristic**
- **Measure small-signal gain**