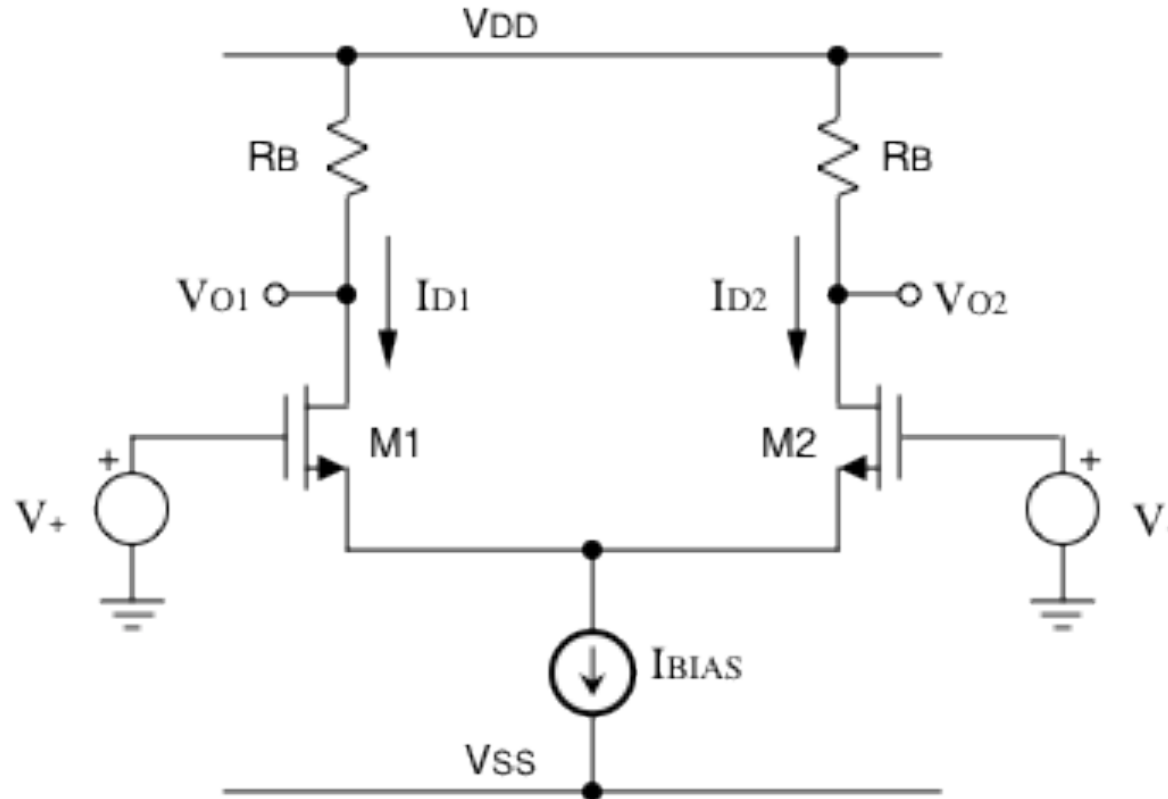


Studio 7 Overview


- **Differential Amplifier, Current Mirror Load**
 - **Textbook Razavi 4.1-4.3, 5.3**

Circuit: Differential Amplifier (Resistive Load)





Differential input voltage controls “split” of I_{BIAS} to I_{D1} , I_{D2}

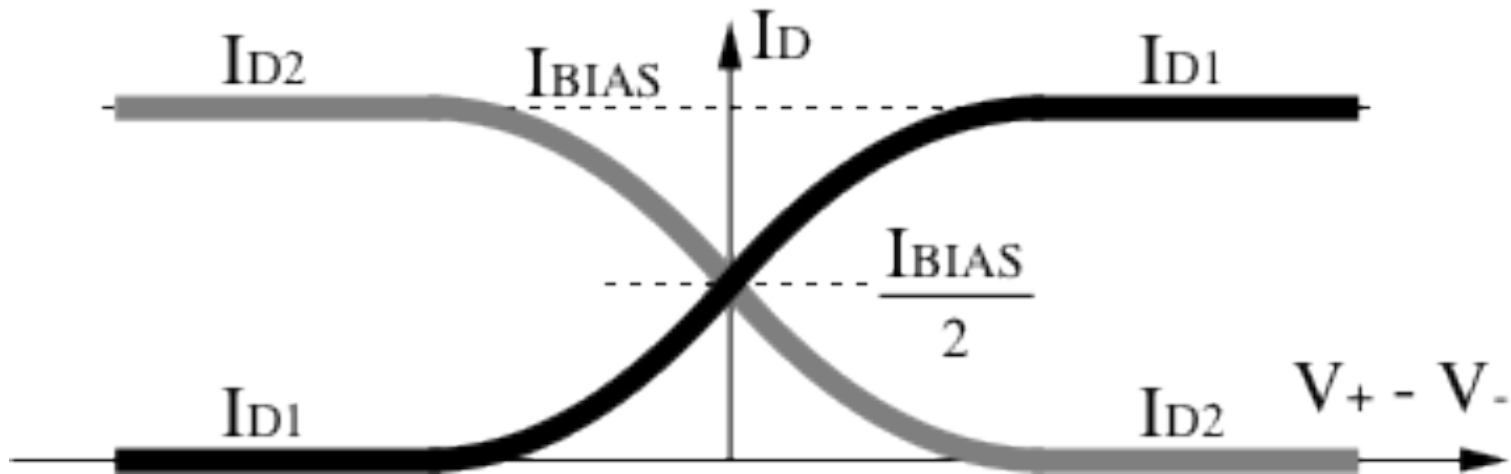Qualitative V-I Characteristic: "Connect the dots"



- General shape for any differential pair: MOSFET, BJT, JFET, ...
- Specifics depend on bias, technology, etc.



Voltage Output

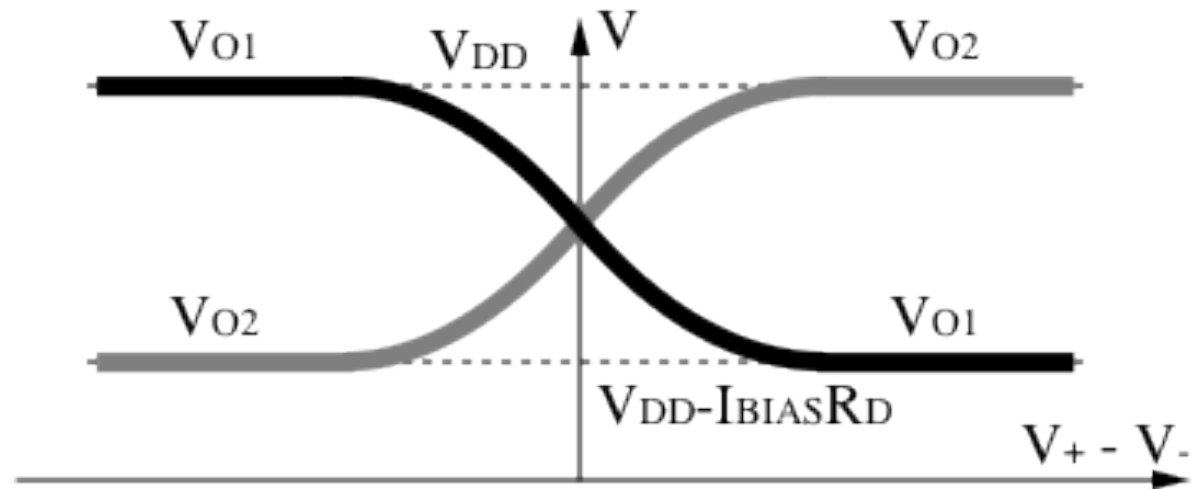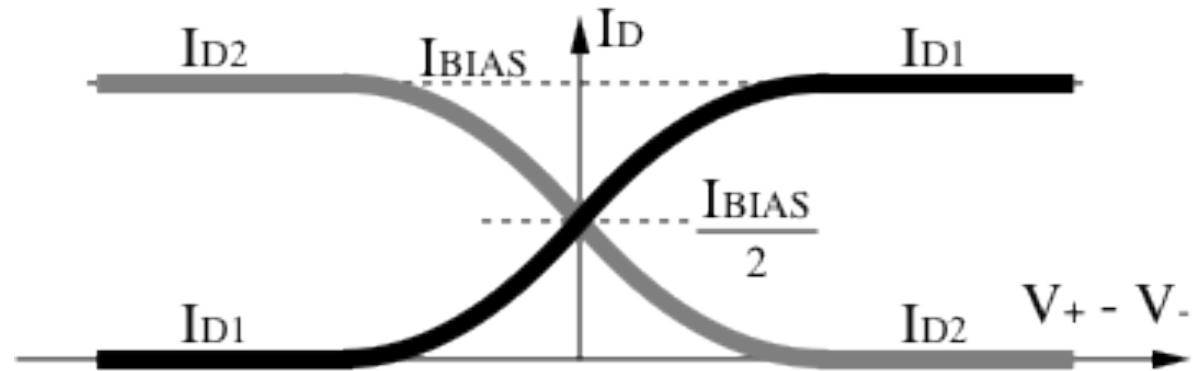


$$V_{O1} = V_{DD} - I_{D1}R_D$$

$$V_{O2} = V_{DD} - I_{D2}R_D$$

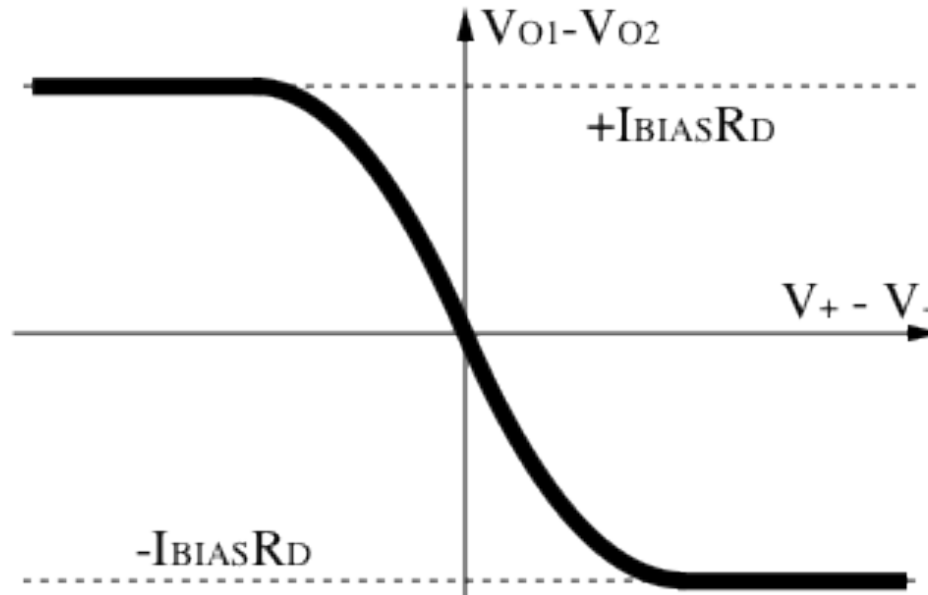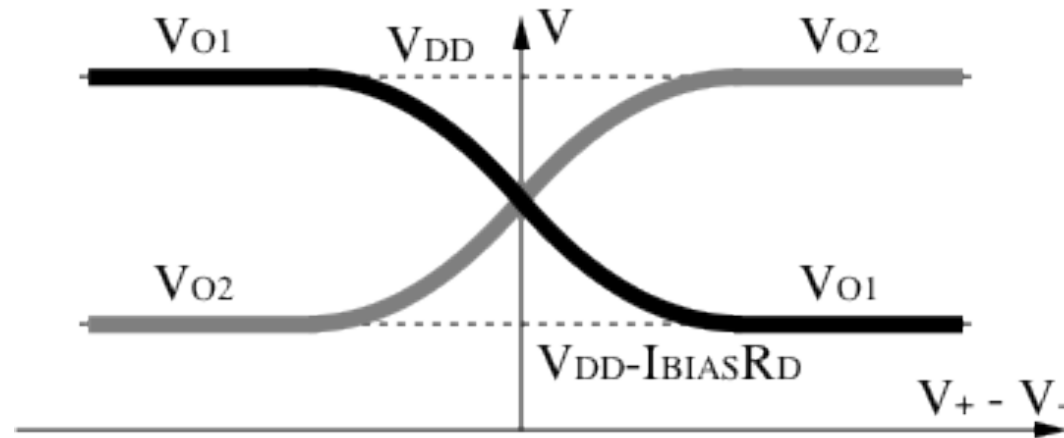Differential Voltage Output: $V_{OD} = V_{O1} - V_{O2}$



Differential Voltage Output

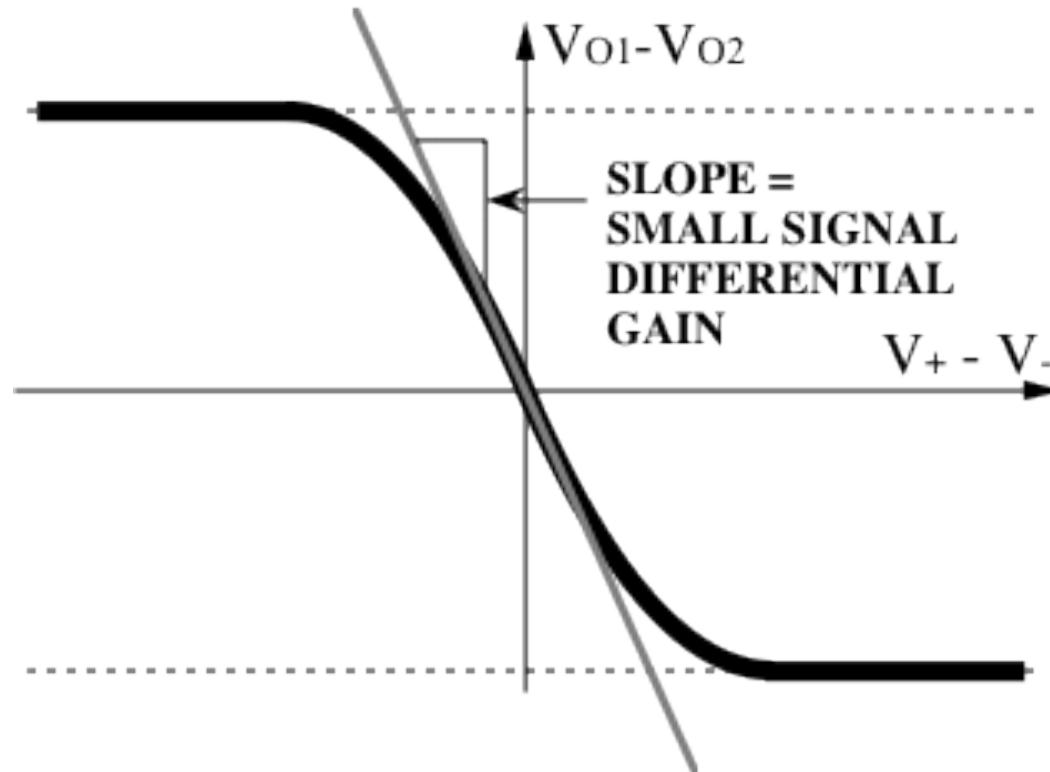


- Slope of plot at operating point (origin):
Small signal differential gain $a_{v(\text{diff})}$

Differential Gain


- **Need to improve $\Rightarrow$ need to be quantitative**
- **Analytic tool:**
Bartlett's Bisection Theorem
- **Applies for symmetrical circuits**
- **Simplifies analysis:**
Allows splitting of circuit into separate halves

Bartlett's Bisection Theorem

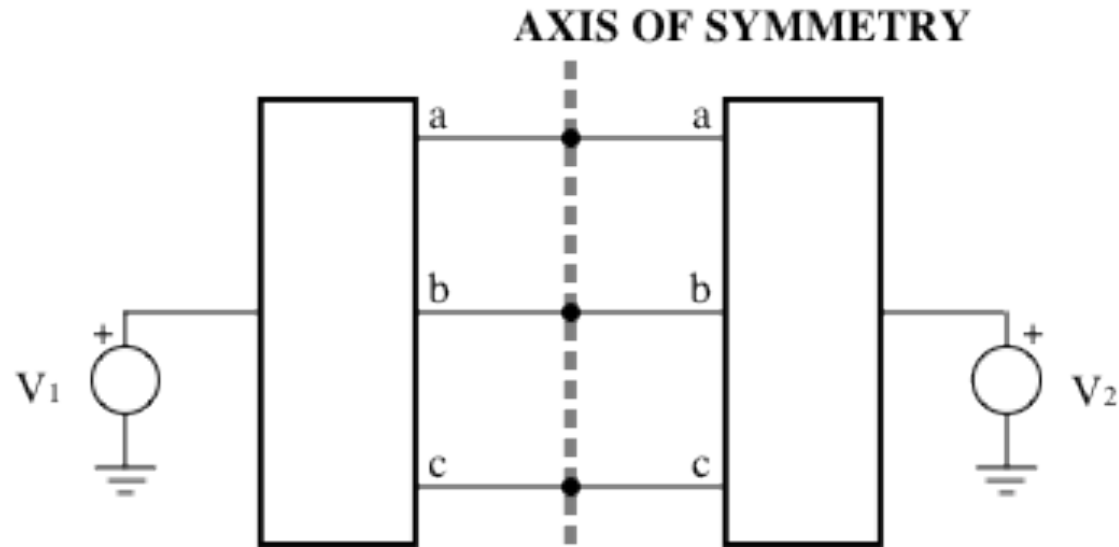- Two completely symmetrical circuits
a, b, c are connected points of symmetry




Common mode: Symmetric excitation

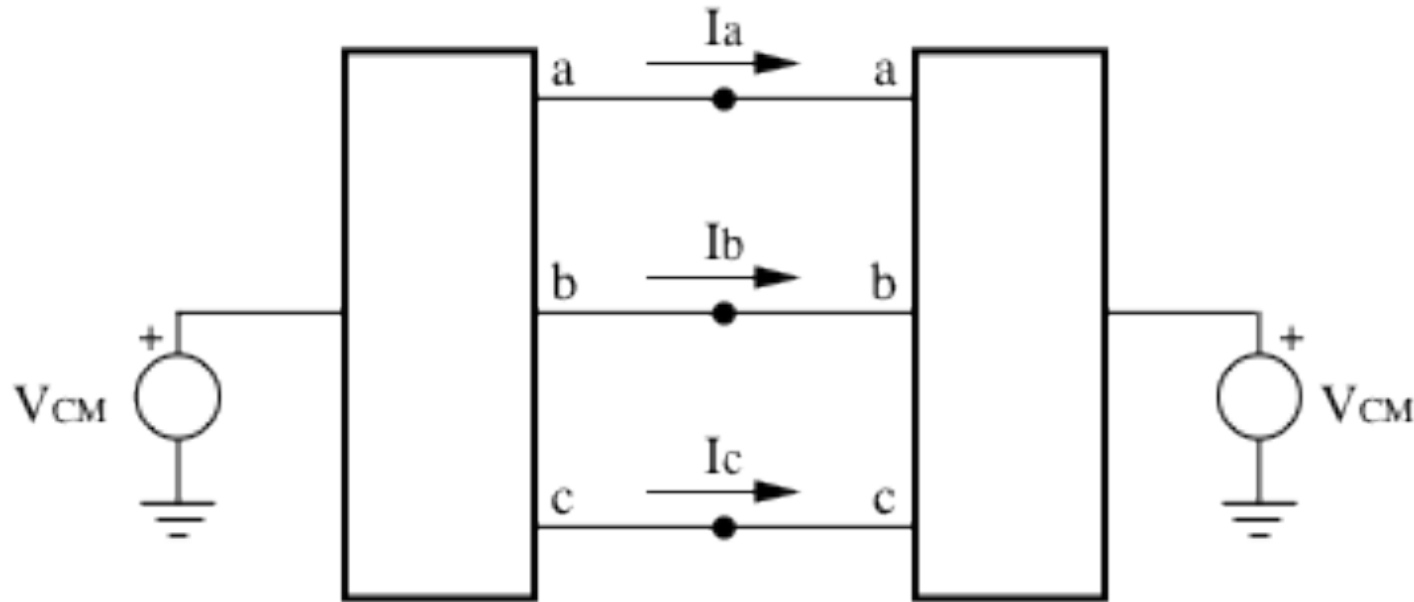


- If $V_1 = V_2 = V_{CM}$ (same input to both circuits)
- No current at connected points of symmetry
- Imagine mirror reversal: $I_a = -I_a \Rightarrow I_a = 0$

Common mode: Symmetric excitation

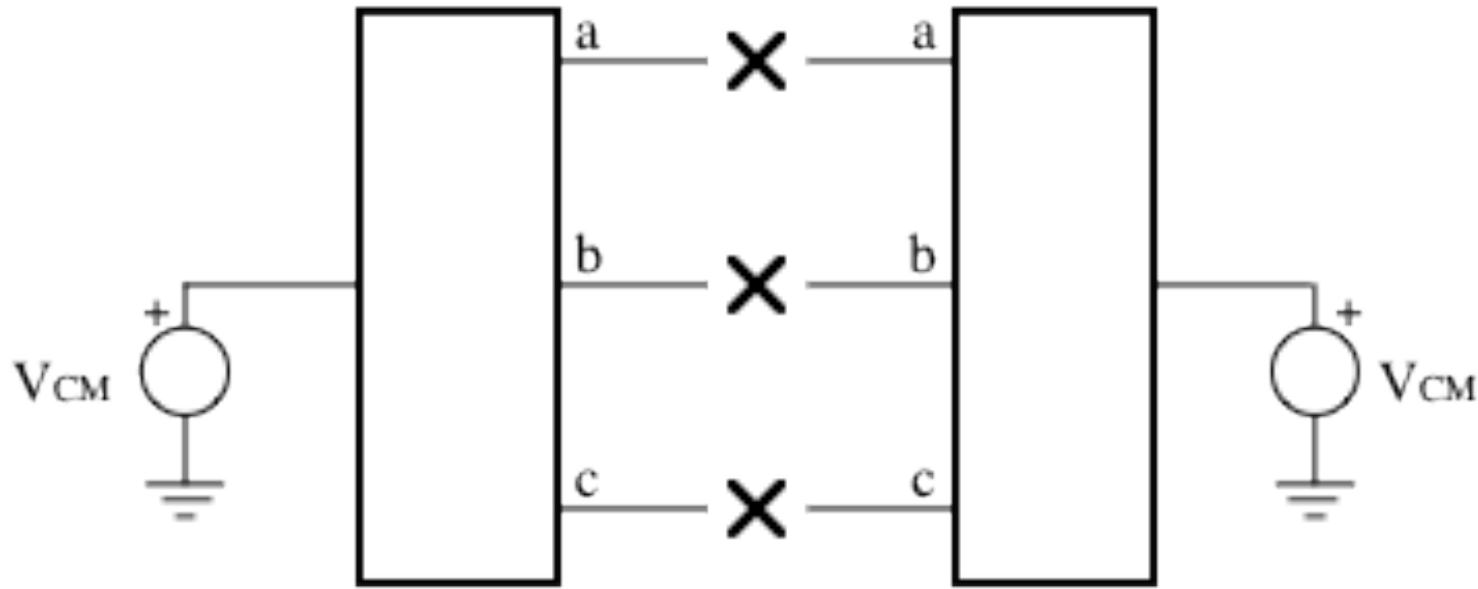


- We can open all leads between connected points of symmetry without affecting circuit operation
- Applies for any circuit (linear or nonlinear)

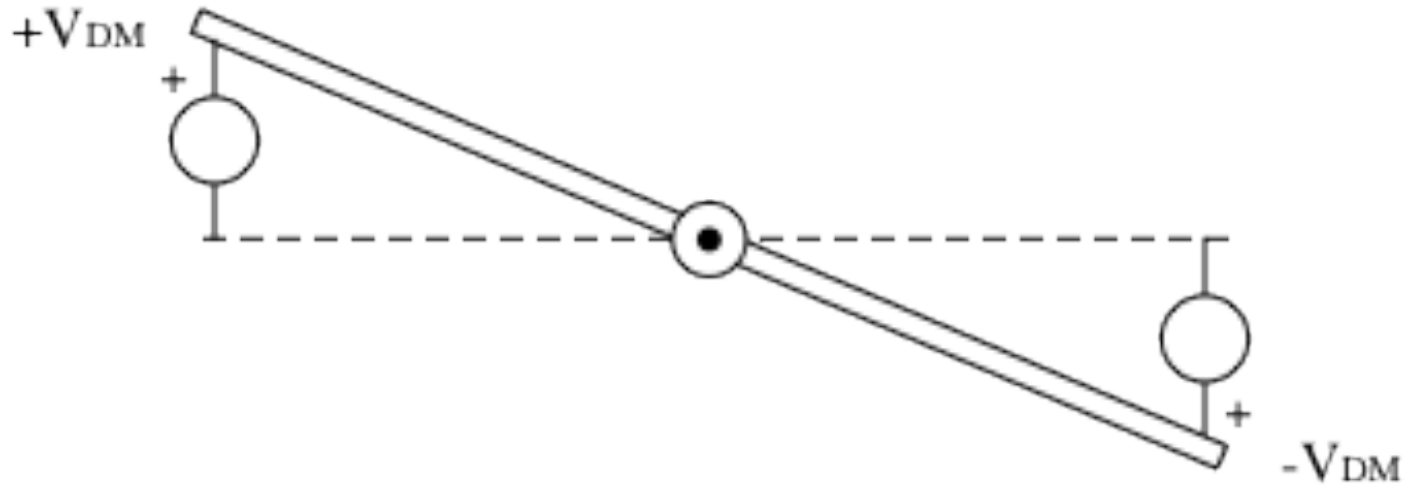Differential mode: Antisymmetric excitation



**If $V_1 = -V_2$: “See-Saw”:
Fixed voltage at connected points of symmetry**

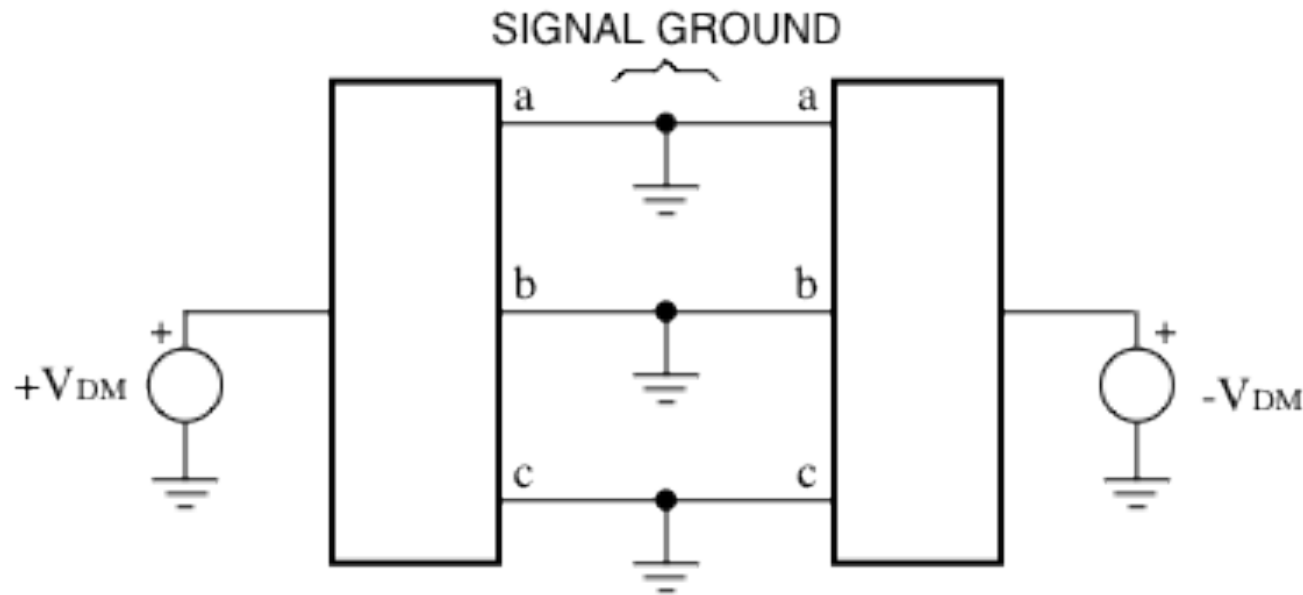Differential mode: Antisymmetric excitation




- All leads between connected points of symmetry can be tied to small signal ground without affecting circuit operation
- Requires linearity

Bartlett's Bisection Theorem

- **Applies to symmetric circuits**
- **Common mode (symmetric) excitation**
 - **Open connected points of symmetry**
- **Differential (antisymmetric) excitation**
 - **Connected points of symmetry tied to signal ground**
 - **Requires linearity**

Any two signals!

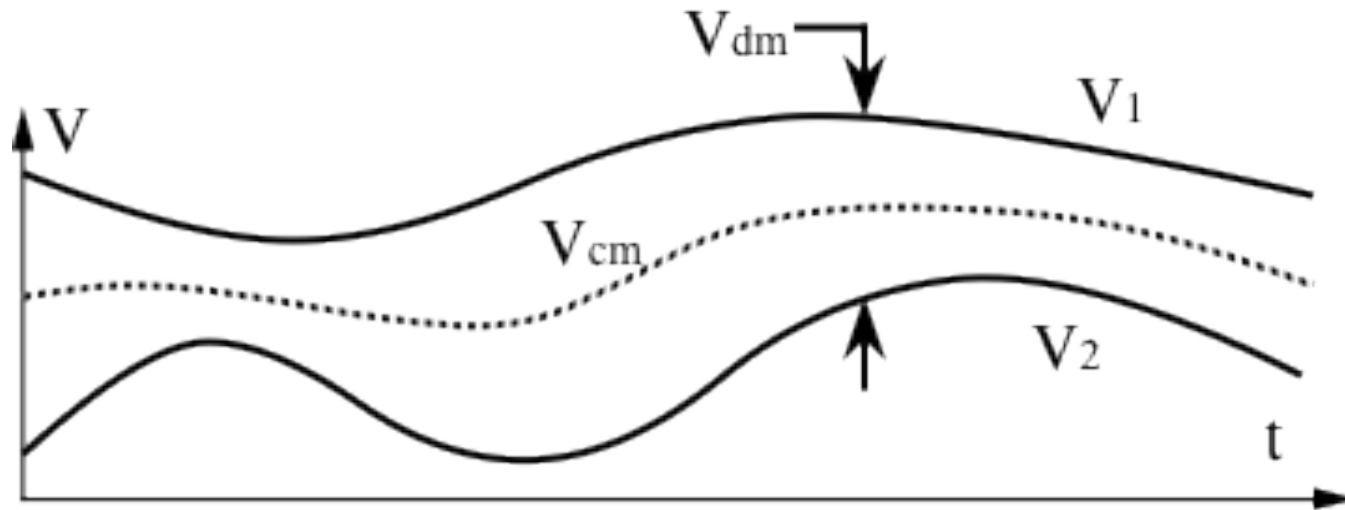

**Can be expressed as sum of
common mode, differential mode:**


Any two signals!

- **Define:** $V_{CM} = \frac{V_1 + V_2}{2}$

$$V_{dm} = V_1 - V_2$$

- **Can verify:** $V_1 = V_{CM} + \frac{V_{dm}}{2}$


$$V_2 = V_{CM} - \frac{V_{dm}}{2}$$

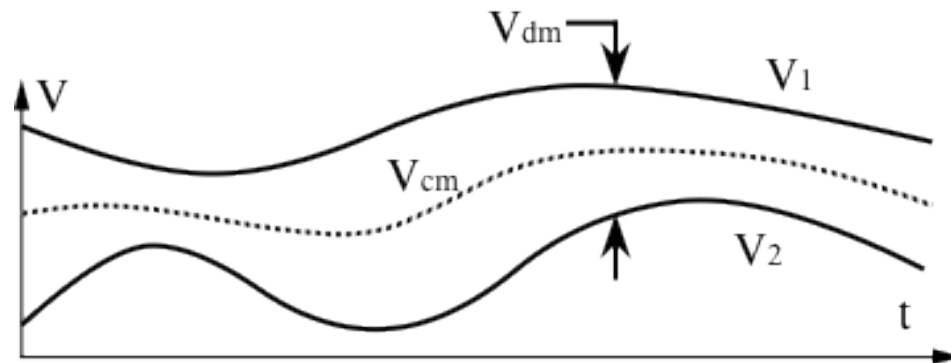


Half circuit analysis technique

- 1) Represent inputs in terms of V_{dm} , V_{CM}**
- 2) Redraw circuit to emphasize symmetry**
- 3) Use superposition to find output:**
 - DC bias: $V_1, V_2 = 0$ (all inputs suppressed)**
 - CM Response: keep v_{CM} , set $v_{dm} = 0$**
 - DM response: keep v_{dm} , set $v_{CM} = 0$**
 - Add results for total output**
- Split circuit using bisection theorem:**
 - Analyze each half separately**

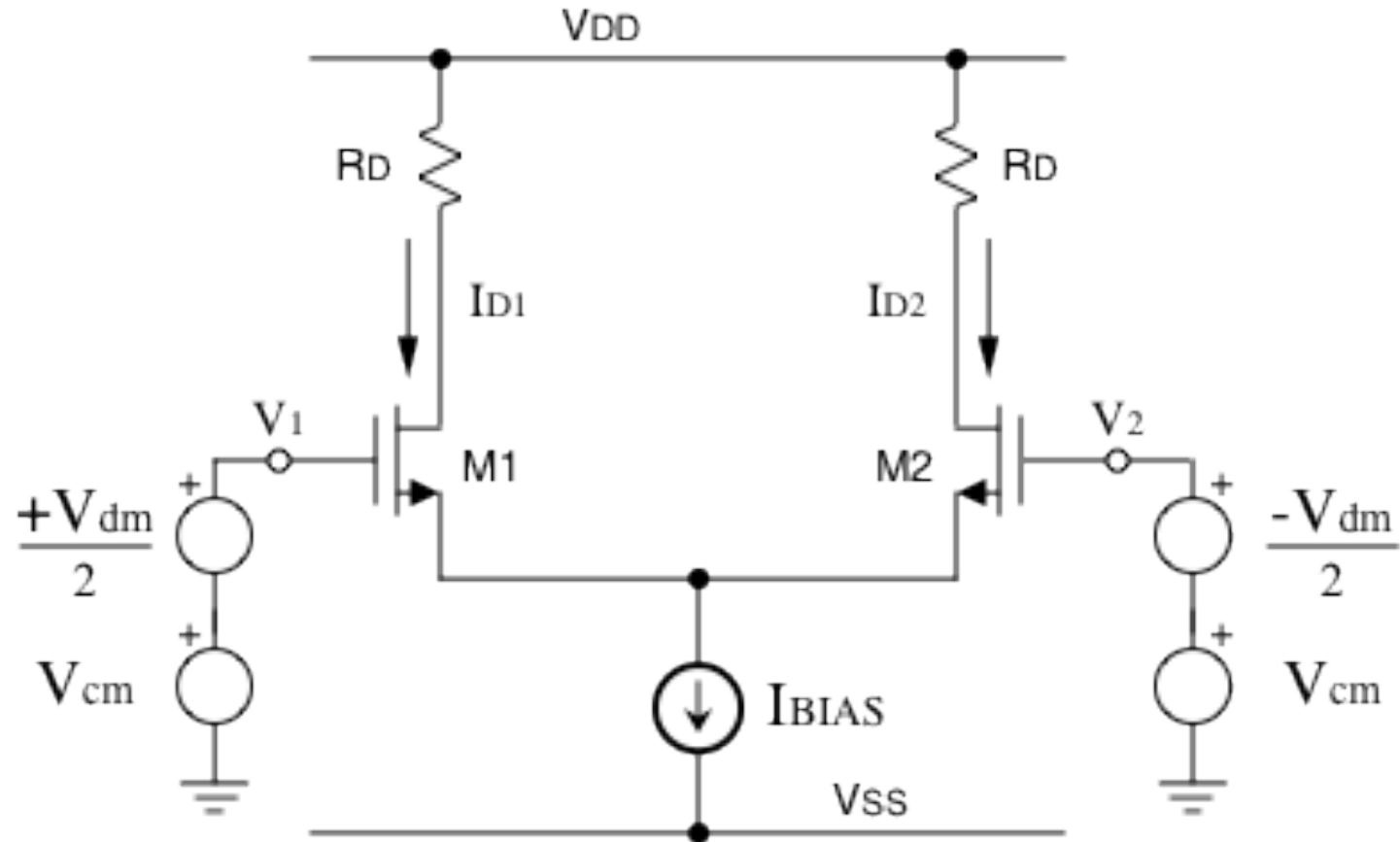1) Represent inputs in terms of V_{dm} , V_{cm}



2) Redraw to show symmetry

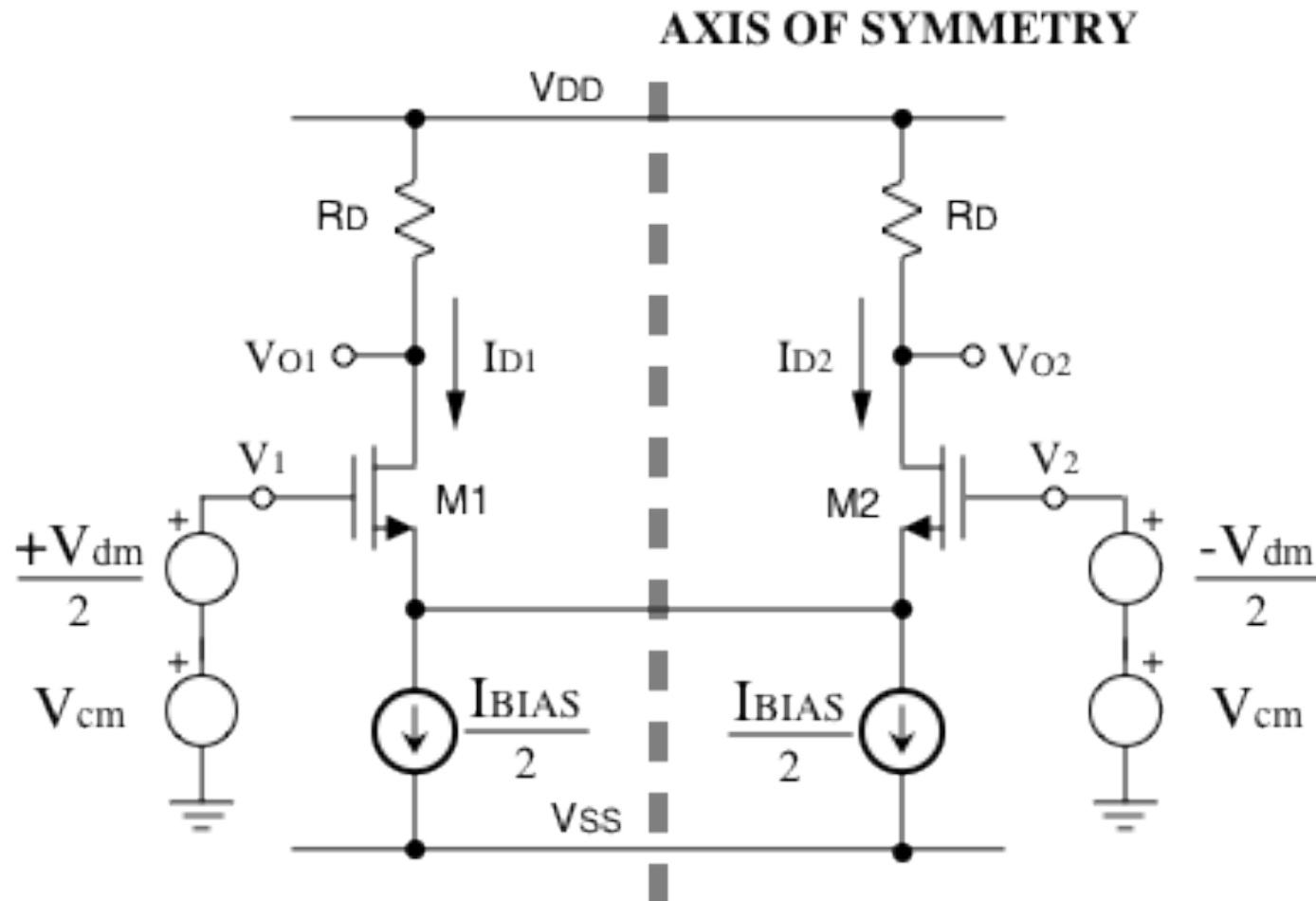


- I_{BIAS} equivalent: two $I_{BIAS}/2$ in parallel

DC bias: $V_1, V_2 = 0$ (all signal inputs suppressed)


$$V_{O1(DC)} = V_{DD} - \frac{I_{BIAS}}{2} R_D$$
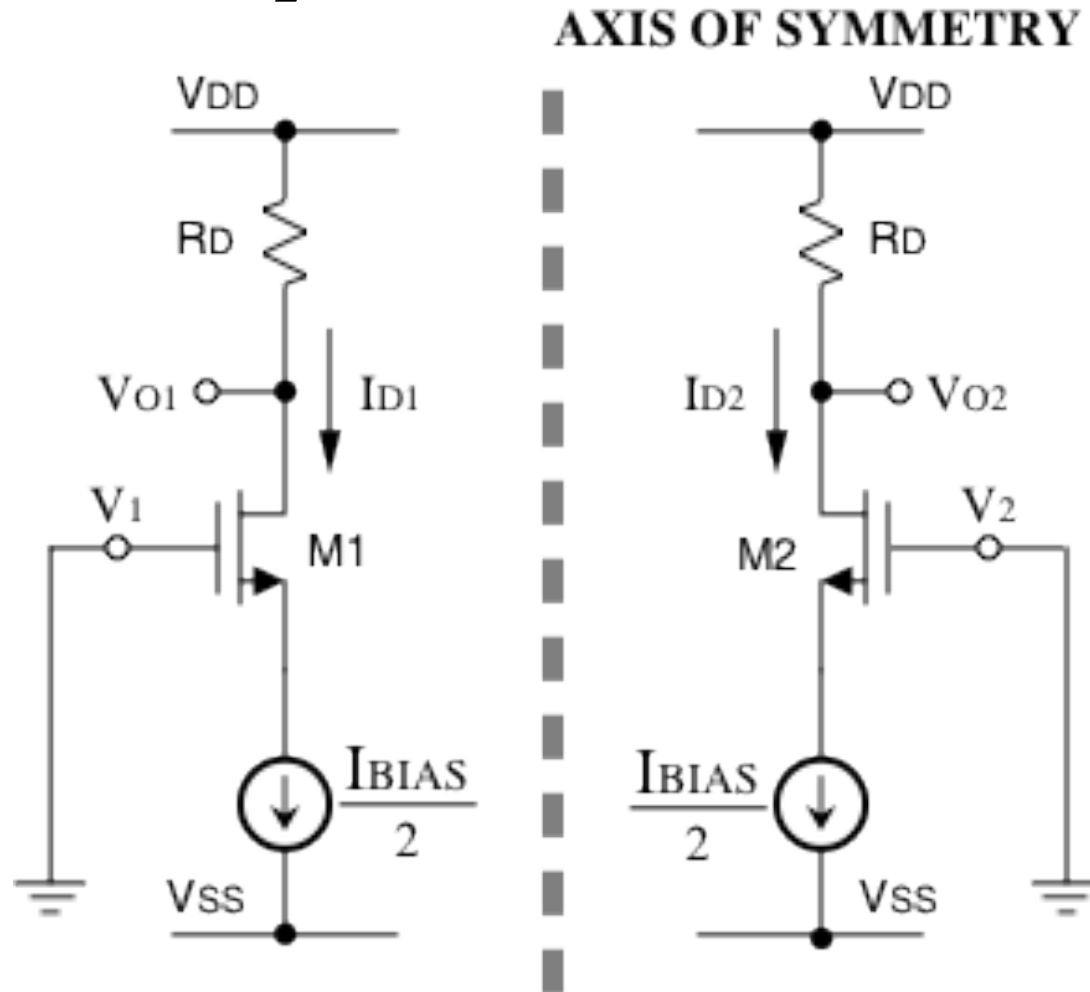
$$V_{O2(DC)} = V_{DD} - \frac{I_{BIAS}}{2} R_D$$




- **Symmetric excitation:**
open connected points of symmetry

Common Mode Response: $v_{dm} = 0$

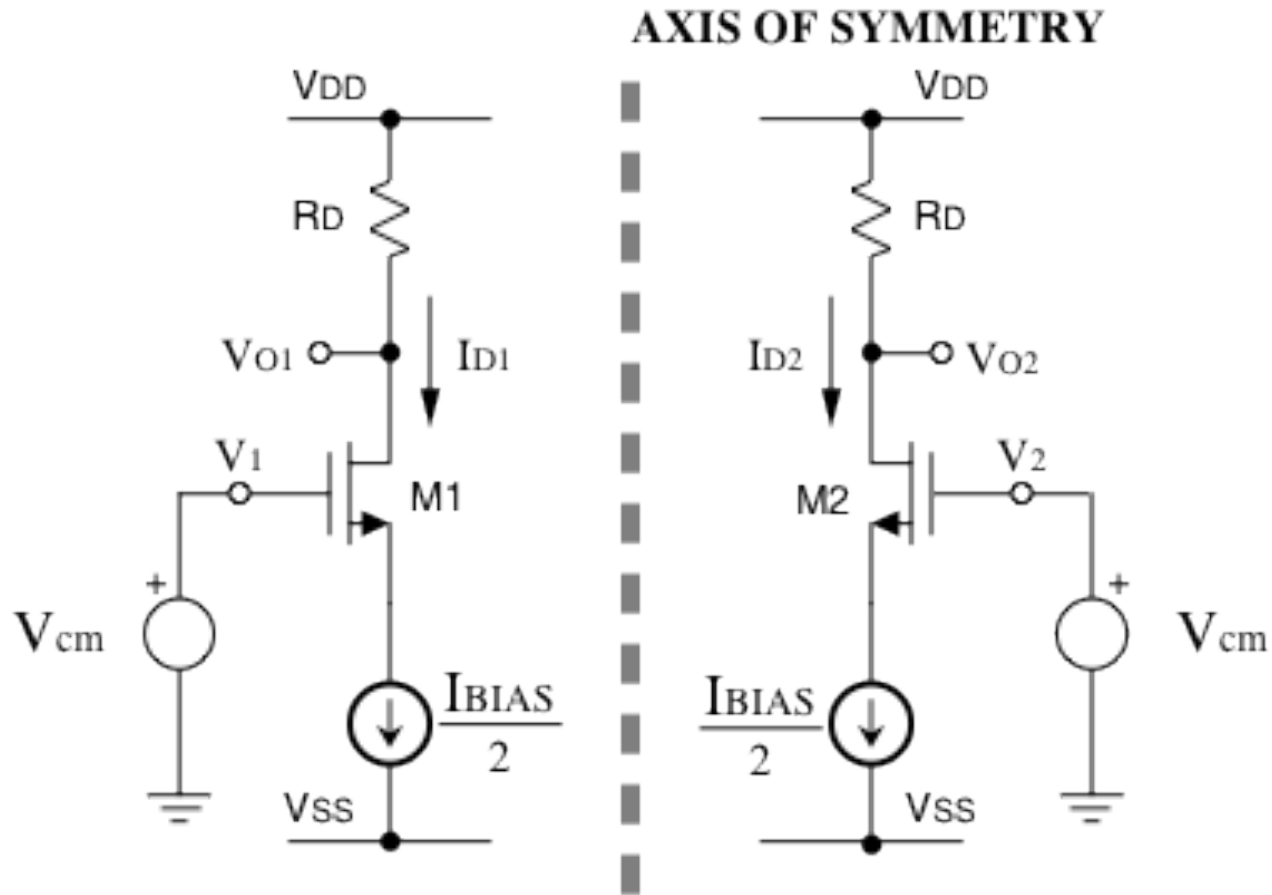

- Open connected points of symmetry


Note "supernode": $i_d = 0$

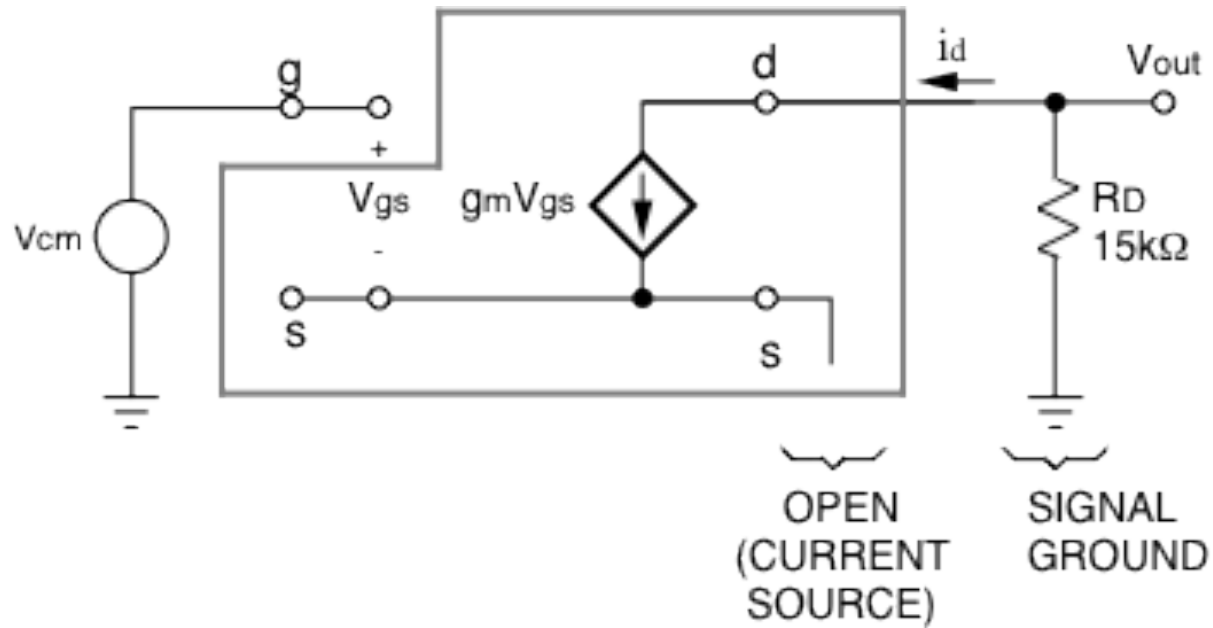

$$V_{o1(cm)} = -i_d R_D = 0$$


$$V_{o2(cm)} = 0$$

Differential mode response: $v_{cm} = 0$

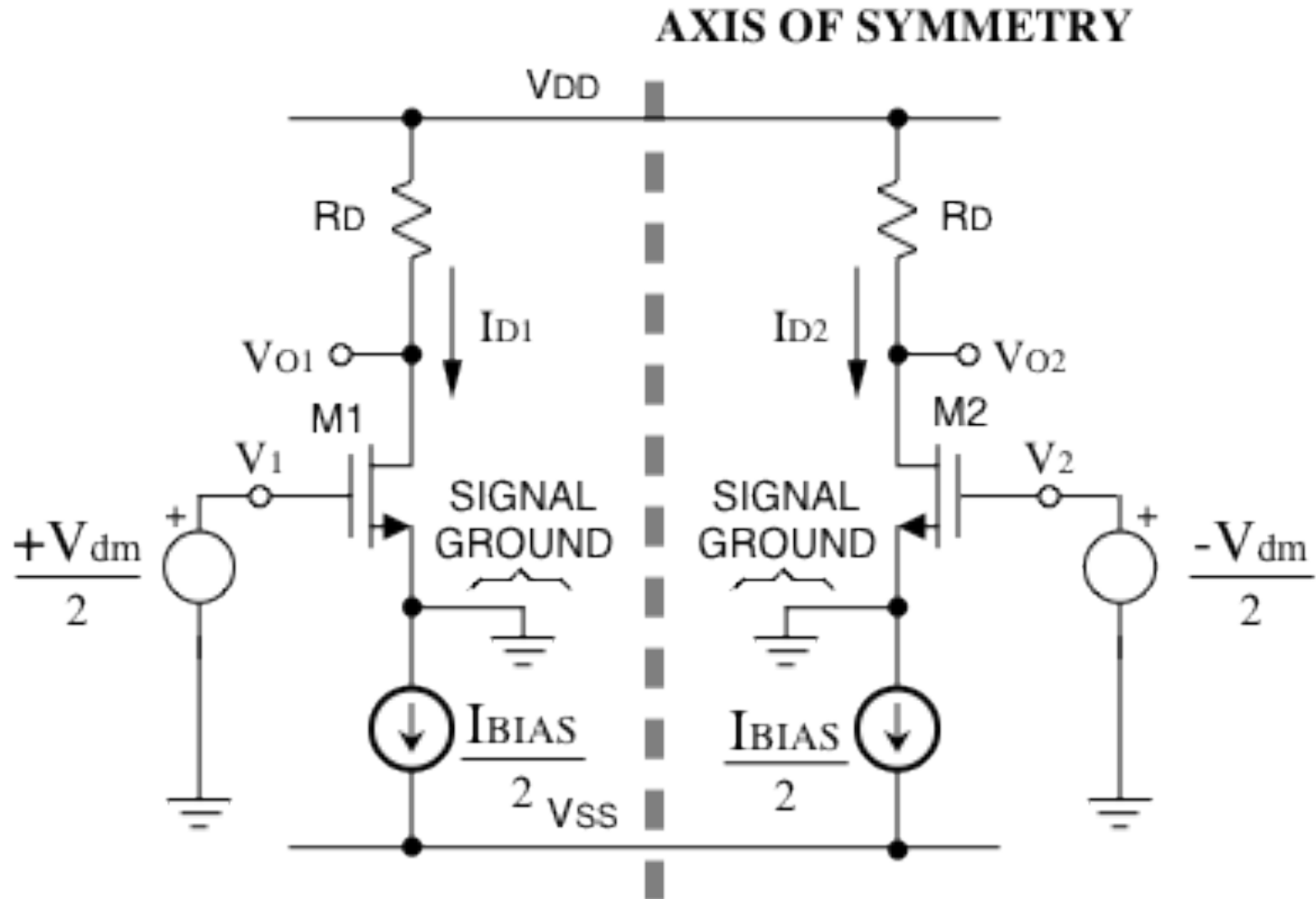

- Connected points of symmetry to signal ground

Small signal model of half-circuit

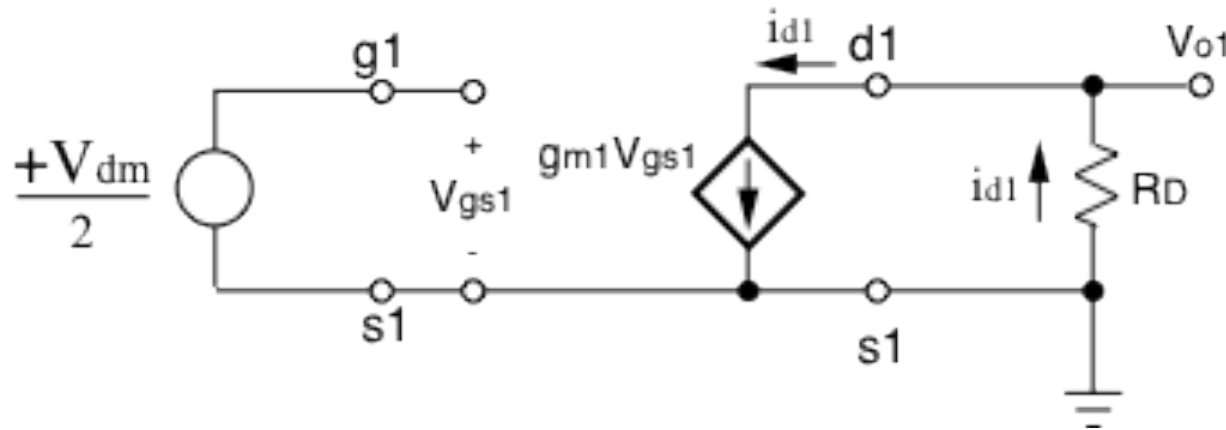

$$\underbrace{V_{o1(dm)}}_{OUTPUT} = -g_m R_D \underbrace{\frac{v_{dm}}{2}}_{INPUT}$$

$$\underbrace{V_{o2(dm)}}_{OUTPUT} = -g_m R_D \underbrace{\frac{-v_{dm}}{2}}_{INPUT}$$

- **Common source amplifier!**
- **Note:** $g_{m1} = g_{m2} = g_m$

Summary: Output “parts”

- **DC bias**

$$V_{O1(DC)} = V_{DD} - \frac{I_{BIAS}}{2} R_D \qquad V_{O2(DC)} = V_{DD} - \frac{I_{BIAS}}{2} R_D$$

- **Common mode**

$$V_{O1(cm)} = 0 \qquad V_{O2(cm)} = 0$$

- **Differential mode**

$$V_{O1(dm)} = \frac{-g_m R_D}{2} v_{dm} \qquad V_{O2(dm)} = \frac{g_m R_D}{2} v_{dm}$$

Summary: Total output sum of components

$$V_{O1} = \underbrace{V_{DD} - \frac{I_{BIAS}}{2} R_D}_{DCBIAS} + \underbrace{0}_{\check{CM}} + \underbrace{\frac{-g_m R_D}{2} v_{dm}}_{DIFFERENTIAL MODE}$$

$$V_{O2} = \underbrace{V_{DD} - \frac{I_{BIAS}}{2} R_D}_{DCBIAS} + \underbrace{0}_{\check{CM}} + \underbrace{\frac{g_m R_D}{2} v_{dm}}_{DIFFERENTIAL MODE}$$

Studio 7 Exercise

- $I_{BIAS} = 250\mu A, R_D = 20k\Omega$

- DCbias

$$V_{O1(DC)} = V_{DD} - \frac{I_{BIAS}}{2} R_D = +5V - \frac{250\mu A}{2} 20k\Omega = +2.5V$$

- Small signal: $g_m \approx 400\mu A/V$

$$g_{m1} R_D \approx (400\mu A/V)(20k\Omega) = 8$$


Differential gain

$$a_{v(diff)} = \frac{\overbrace{V_{o1(dm)} - V_{o2(dm)}}^{\text{DIFFERENTIAL OUTPUT}}}{\underbrace{v_{dm}}_{\text{DIFFERENTIAL INPUT}}}$$
$$a_{v(diff)} = \frac{-g_m R_D \frac{v_{dm}}{2} - g_m R_D \frac{v_{dm}}{2}}{v_{dm}}$$


$$a_{v(diff)} = -g_m R_D$$

- Same as common source amplifier
- Still low for resistive load!

Drain Currents

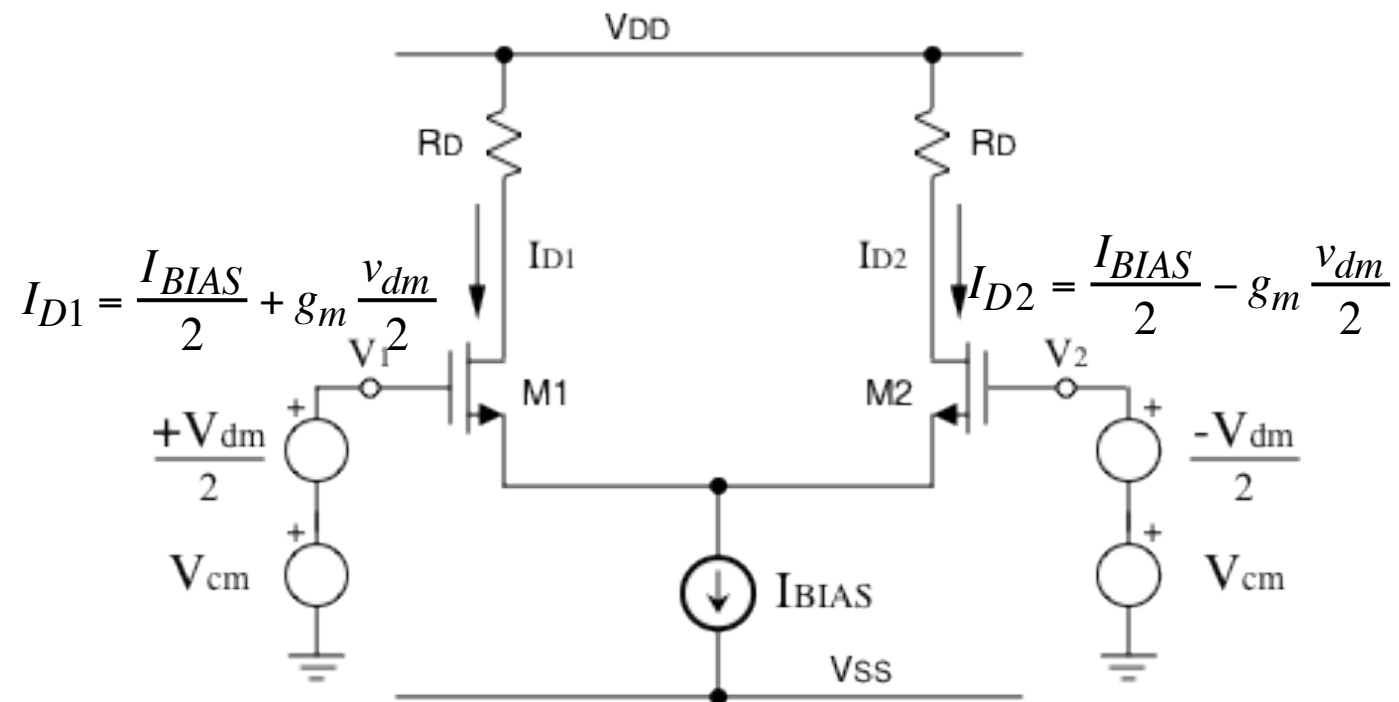

Drain Currents

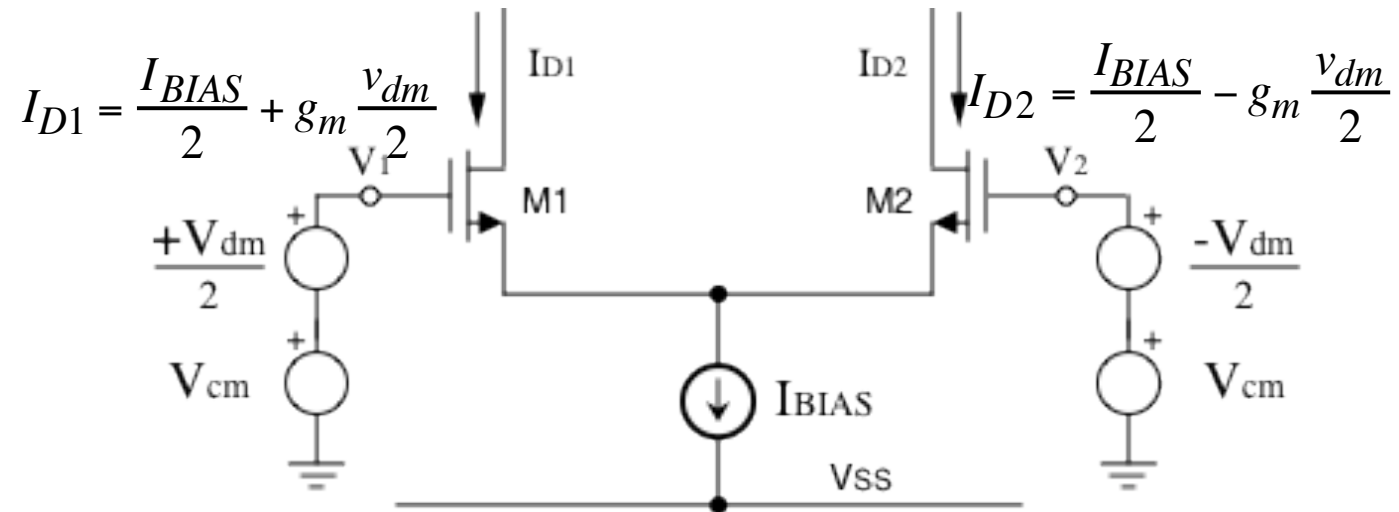

Mirror load

